
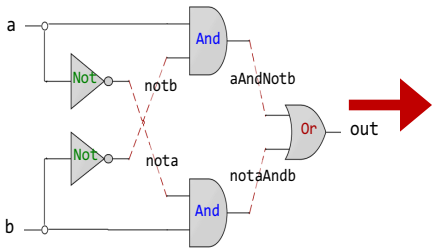


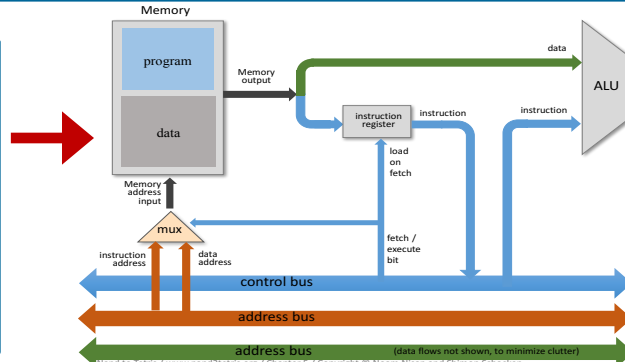

# Computer Organization & Assembly Language Programming



```
CHIP Xor {
  IN a, b;
  OUT out;
  PARTS:
  Not(in=a, out=nota);
  Not(in=b, out=notb);
  And(a=nota, b=b, out=w1);
  And(a=a, b=notb, out=w2);
  Or(a=w1, b=w2, out=out);
}
```



@R1  
D=M  
@temp  
M=D

```
0000000000000001
1111110000010000
0000000000010000
1110001100001000
```


## Lecture # 13

## Design of Counters

```
#include<stdio.h>
#include<stdlib.h>
int main(){
  printf("Learning is fun with Arif\n");
  exit(0);
}
```

```
global main
SECTION .data
  msg: db "Learning is fun with Arif", 0Ah, 0h
  len_msg: equ $ - msg
SECTION .text
main:
  mov rax,1
  mov rdi,1
  mov rsi,msg
  mov rdx,len_msg
  syscall
  mov rax,60
  mov rdi,0
  syscall
```
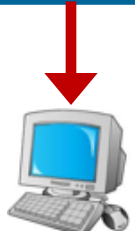
```
0: b8 01 00 00 00
5: bf 01 00 00 00
a: 48 be 00 00 00 00 00
11: 00 00 00
14: ba 1b 00 00 00
19: 0f 05
1b: b8 3c 00 00 00
20: bf 00 00 00 00
25: 0f 05
```



Slides of first half of the course are adapted from:  
<https://www.nand2tetris.org>  
 Download s/w tools required for first half of the course from the following link:  
<https://drive.google.com/file/d/0B9c0BdDjz6XpZUh3X2dPR1o0MUE/view>


**Instructor: Muhammad Arif Butt, Ph.D.**


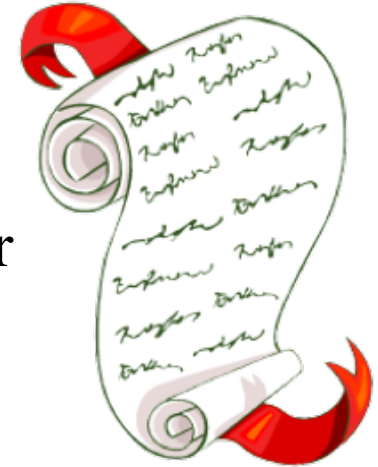
# Today's Agenda

---


- Overview of Hack Computer Components
- Overview of Counters
- Why do we need Counter for our Hack Computer
- Concept of Program Counter
- Counter Simulation
- Design and Implementation of PC for Hack Computer
- Demo on H/W Simulator





# Hack Computer System

## Computer System

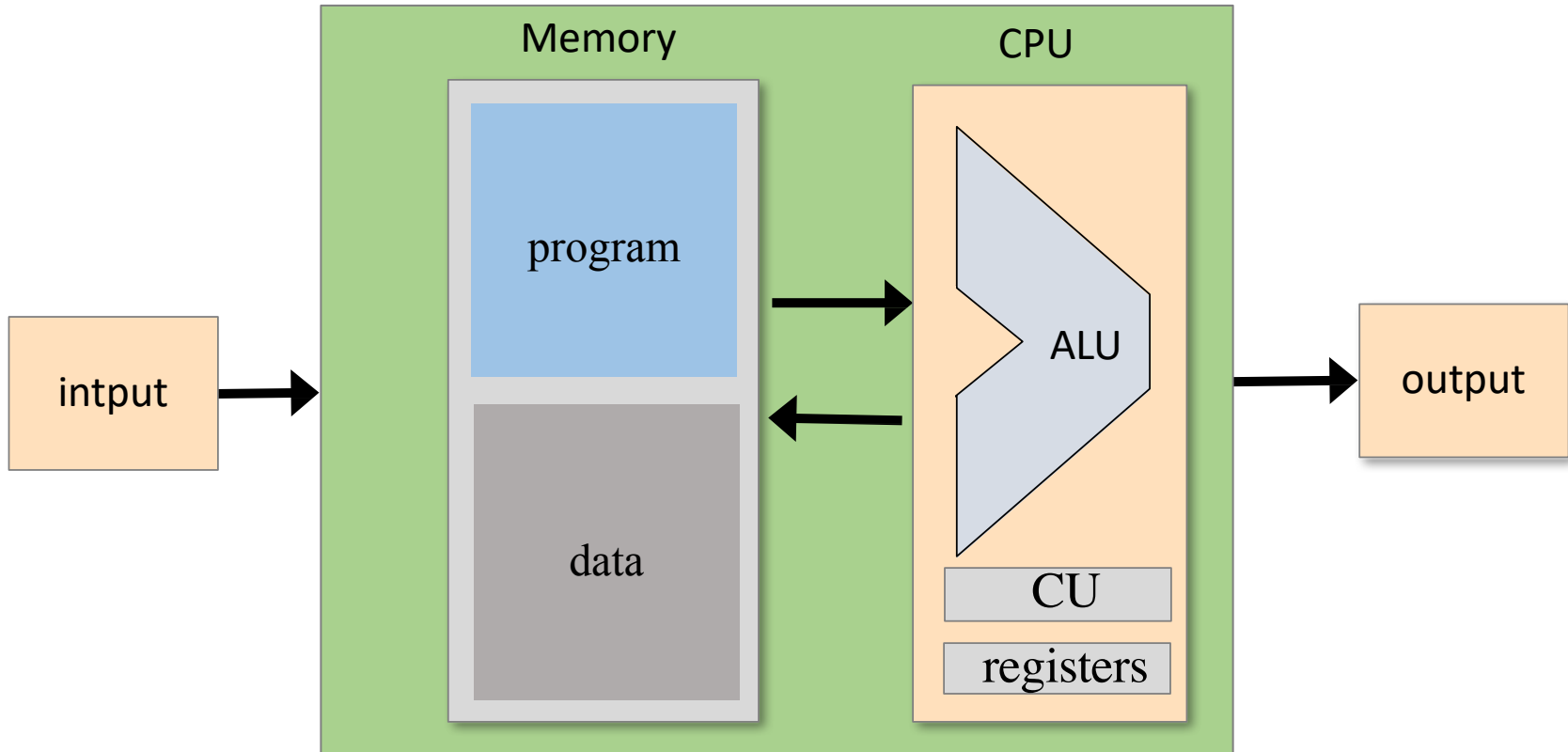



# Counters



# Overview of Counters

---

- A counter is a special type of register that goes through a pre-determined sequence of states upon the application of input pulses
- **Counters are used for:**
  - Counting the number of occurrences of an event
  - Keeping time or calculating amount of time between events
  - Baud rate generation
- **A w-bit counter consists of two main elements:**
  - A w-bit register to store a w-bit value
  - A combinational logic to
    - Compute the next value (according to a specific counting function)
    - Load a new value of user/programmer choice
    - Reset the counter to a default value
- **Examples:**
  - Simple Up/Down Binary Counters
  - BCD Counter(s)
  - Gray Code Counter
  - Ring Counter
  - Johnson Counter



# Why we Need Counter Chip for Hack CPU

---

- Consider a counter chip designed to contain the address of the instruction that the computer should fetch and execute next
- In most cases, the counter has to simply increment itself by 1 in each clock cycle, thus causing the computer to fetch the next instruction in the program
- In other cases, we may want the program to *jump to an instruction at memory address  $n$* , so the programmer want to set the counter to a value of  $n$ , rather than its default counting behavior with  $n+1$ ,  $n+2$ , and so forth
- Finally, the program's execution can be restarted anytime by resetting the counter to 0, assuming that the address of the program's first instruction
- In short, we need a loadable and resettable counter




# Program Counter Register

---

- Every computer has a special register called the Program Counter, normally called the PC, which keeps track of the instruction to be fetched and executed next
- The PC is designed to support three possible control operations:
  - **Reset:** Fetch the first instruction  $PC = 0$
  - **Next:** Fetch the next instruction  $PC++$
  - **Goto:** Fetch instruction at address **n**  $PC = n$



# Counter Abstraction

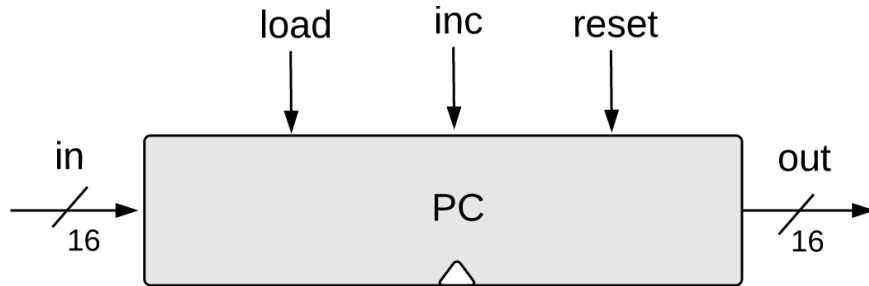

if reset[t] = 1 then

**PC = 0**

out[t+1] = 0

else if load[t] = 1 then

**PC = in**

out[t+1] = in[t]

else if inc[t] = 1 then

**PC++**


out[t+1] = out[t] + 1

else out[t+1] = out[t] //do nothing






# Counter Simulation

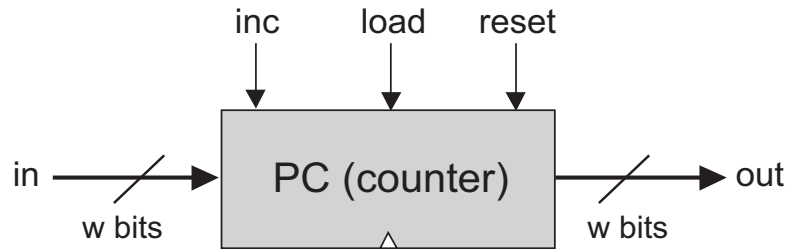

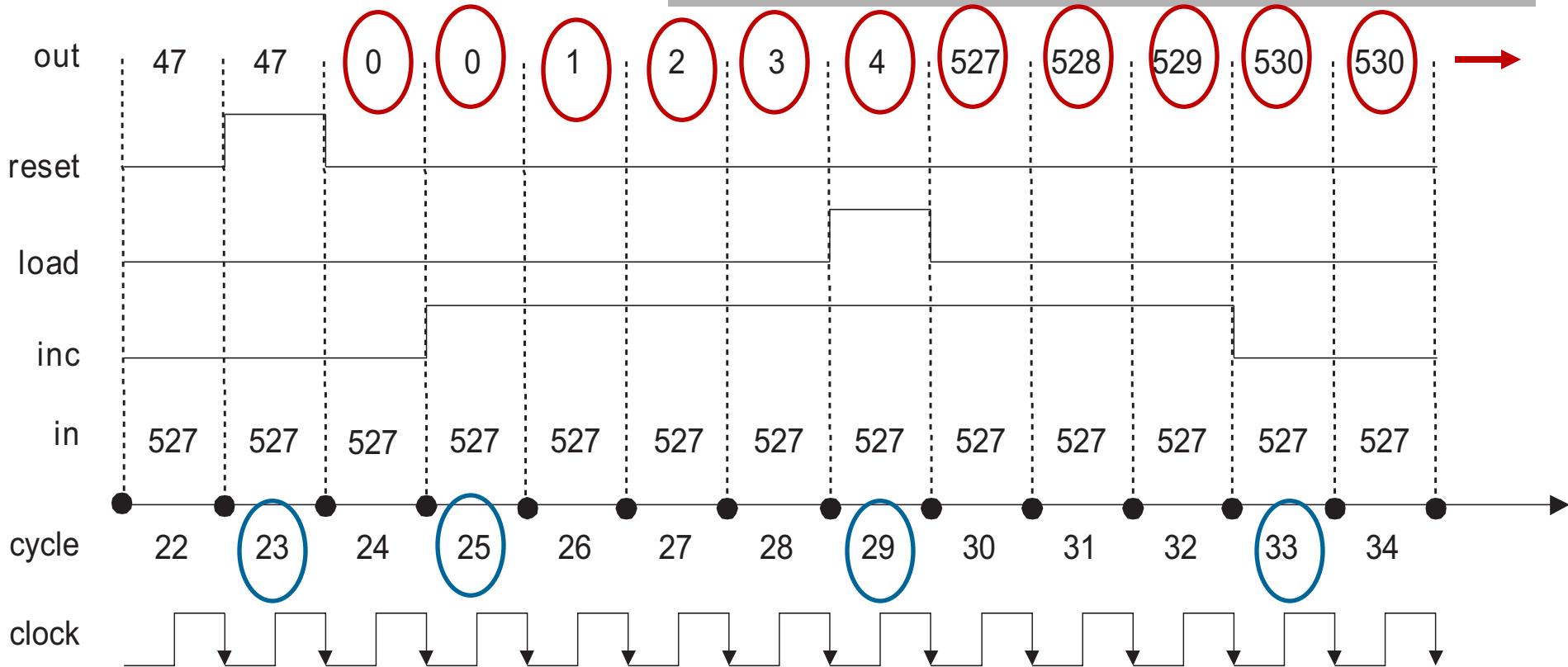
```
Chip name: PC // 16-bit counter
Inputs:   in[16], inc, load, reset
Outputs:  out[16]
Function:  If reset(t-1) then out(t)=0
           else if load(t-1) then out(t)=in(t-1)
           else if inc(t-1) then out(t)=out(t-1)+1
           else out(t)=out(t-1)
Comment:  "=" is 16-bit assignment.
           "+" is 16-bit arithmetic addition.
```





# 16 Bit Program Counter Implementation

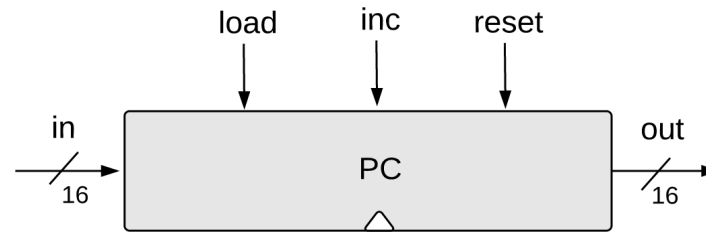

```
CHIP Register {
  IN in[16], load;
  OUT out[16];
  PARTS:
    Bit(in=in[0], load=load, out=out[0]);
    Bit(in=in[1], load=load, out=out[1]);
    Bit(in=in[2], load=load, out=out[2]);
    Bit(in=in[3], load=load, out=out[3]);
    . . . . .
    Bit(in=in[15], load=load, out=out[15]);
}
```


```
CHIP Bit {
  IN in, load;
  OUT out;
  PARTS:
    Mux(a=sendBack, b=in, sel=load, out=MuxOut);
    DFF(in=MuxOut, out=sendBack, out=out);
}
```

```
CHIP Incl6 {
  IN in[16];
  OUT out[16];
  PARTS:
    Add16(a=in, b[0]=true, out=out);
}
```

```
CHIP Add16 {
  IN a[16], b[16];
  OUT out[16];
  PARTS:
    HalfAdder(a=a[0], b=b[0], sum=out[0], carry=carry0);
    FullAdder(a=a[1], b=b[1], c=carry0, sum=out[1], carry=carry1);
    FullAdder(a=a[2], b=b[2], c=carry1, sum=out[2], carry=carry2);
    FullAdder(a=a[3], b=b[3], c=carry2, sum=out[3], carry=carry3);
    .....
    FullAdder(a=a[14], b=b[14], c=carry13, sum=out[14], carry=carry14);
    FullAdder(a=a[15], b=b[15], c=carry14, sum=out[15], carry=carry15);
}
```



# 16 Bit Program Counter Implementation

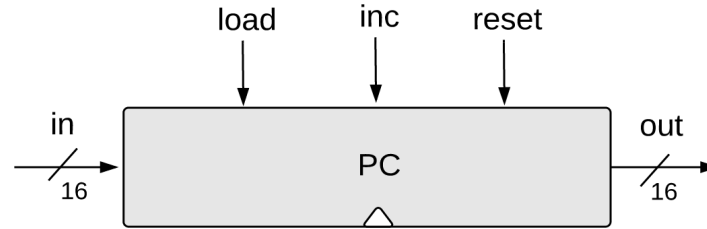

## PC.hdl

```
CHIP PC {  
  IN in[16], load, inc, reset;  
  OUT out[16];
```

```
  PARTS:
```

```
    Inc16(in=regContent, out=incremented);
```

```
  //if (inc == 1)
```

```
    Mux16(a=regContent, b=incremented, sel=inc, out=value1);
```

```
  //else if (load == 1)
```

```
    Mux16(a=value1, b=in, sel=load, out=value2);
```

```
  //else if (reset == 1)
```

```
    Mux16(a=value2, b=false, sel=reset, out=value3);
```

```
  //else
```

```
    Register(in=value3, load=true, out=regContent, out=out);
```

```
  CHIP Mux16 {  
    IN a[16], b[16], sel;  
    OUT out[16];  
    PARTS:  
      Mux(a=a[0], b=b[0], sel=sel, out=out[0]);  
      Mux(a=a[1], b=b[1], sel=sel, out=out[1]);  
      .  
      .  
      Mux(a=a[15], b=b[15], sel=sel, out=out[15]);  
  }
```



# Program Counter Demo

---





# Things To Do

- Perform testing of the chips designed in today's session on the h/w simulator. You can download the .hdl, .tst and .cmp files of above chips from the course bitbucket repository:

<https://bitbucket.org/arifpucit/coal-repo/>

- Interested students should also try to design, implement and simulate binary down counter, cascaded BCD counter, Gray Counter, Ring counter, and Johnson counter



**Coming to office hours does NOT mean you are academically week!**