

 


 

 Computer Organization & Assembly Language Programming



```
CHIP Xor {
  IN a, b;
  OUT out;
  PARTS:
  Not(in=a, out=nota);
  Not(in=b, out=notb);
  And(a=nota, b=b, out=w1);
  And(a=a, b=notb, out=w2);
  Or(a=w1, b=w2, out=out);
}
```



Lecture # 23

Data Path of Hack CPU - II

```
#include<stdio.h>
#include<stdlib.h>
int main(){
  printf("Learning is fun with Arif\n");
  exit(0);
}
```

```
global main
SECTION .data
  msg: db "Learning is fun with Arif", 0Ah, 0h
  len_msg: equ $ - msg
SECTION .text
main:
  mov rax,1
  mov rdi,1
  mov rsi,msg
  mov rdx,len_msg
  syscall
  mov rax,60
  mov rdi,0
  syscall
```

```
0: b8 01 00 00 00
5: bf 01 00 00 00
a: 48 be 00 00 00 00 00
11: 00 00 00
14: ba 1b 00 00 00
19: 0f 05
1b: b8 3c 00 00 00
20: bf 00 00 00 00
25: 0f 05
```

Slides of first half of the course are adapted from:
<https://www.nand2tetris.org>
 Download s/w tools required for first half of the course from the following link:
<https://drive.google.com/file/d/0B9c0BdDjz6XpZUh3X2dPR1o0MUE/view>


Instructor: Muhammad Arif Butt, Ph.D.






Today's Agenda

 - Review of Hack Computer Architecture
- Hack CPU Interface
- Hack CPU Implementation
- Input/output and Operations of Hack ALU
- Control Logic of Hack CPU






Recap: Hack Computer Architecture

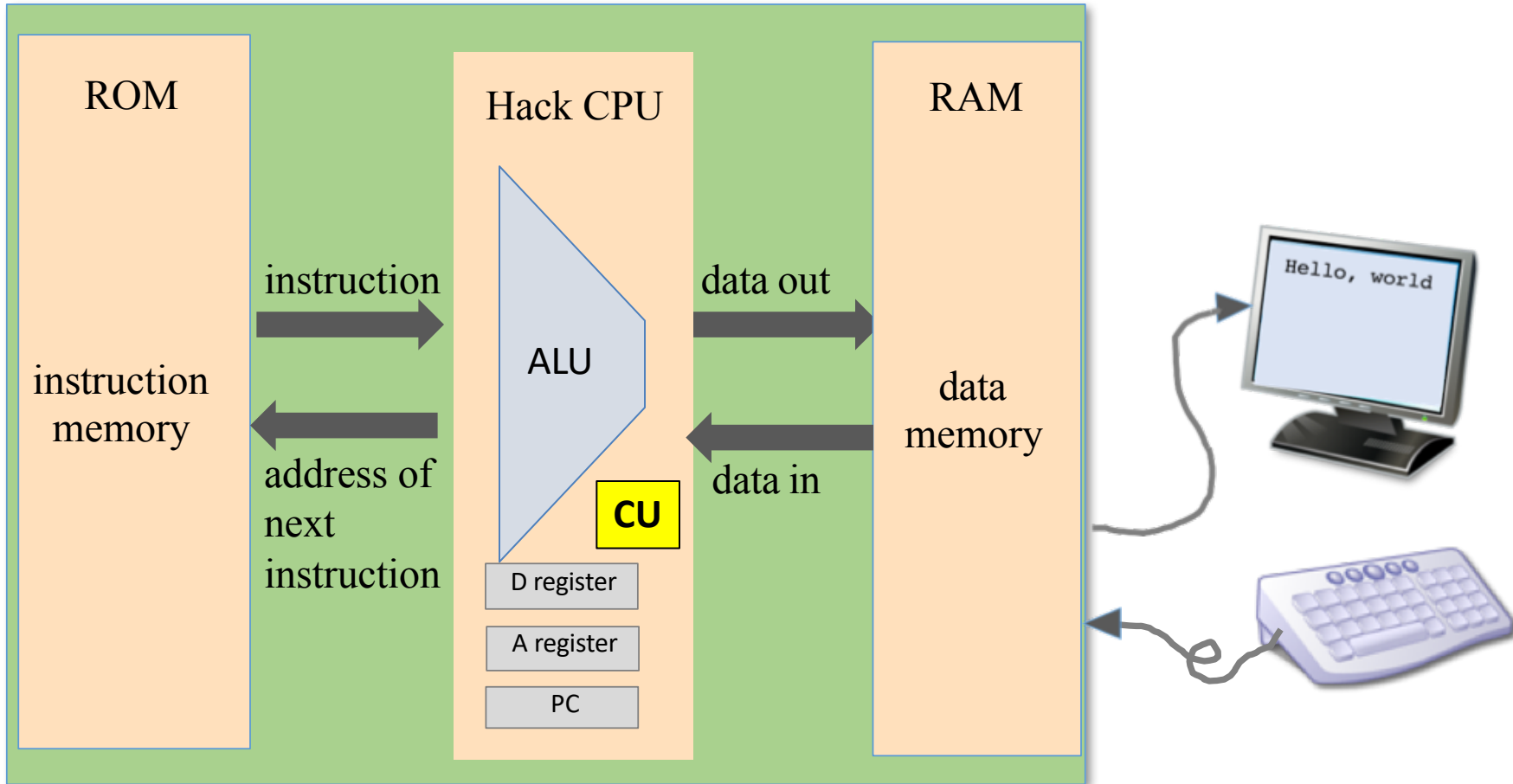




Hack CPU Interface

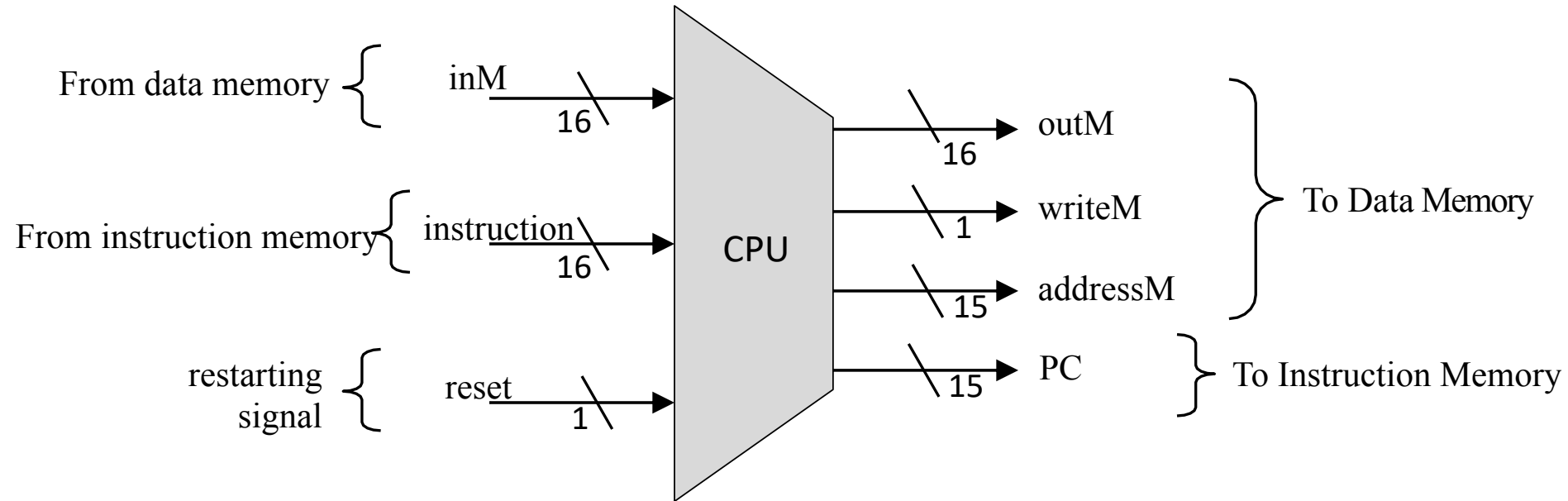


Inputs:

- Data Value
- Instruction
- Reset Bit

 




Hack CPU Interface

 

Outputs:

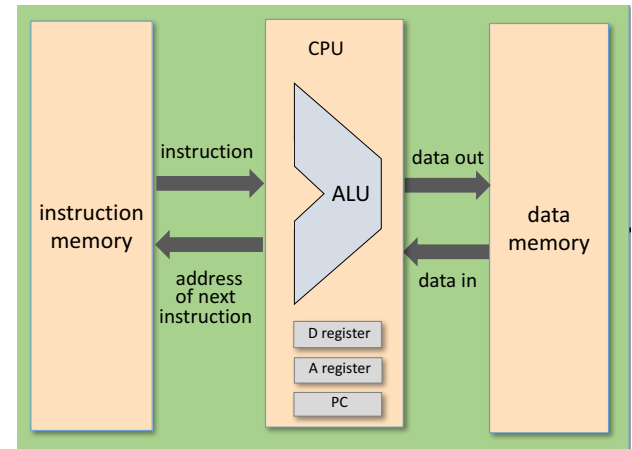
- Data Value
- Write to Memory? (yes/no)
- Memory Address
- Address of next instruction





Execution of Instructions by Hack CPU

Hack Instructions:

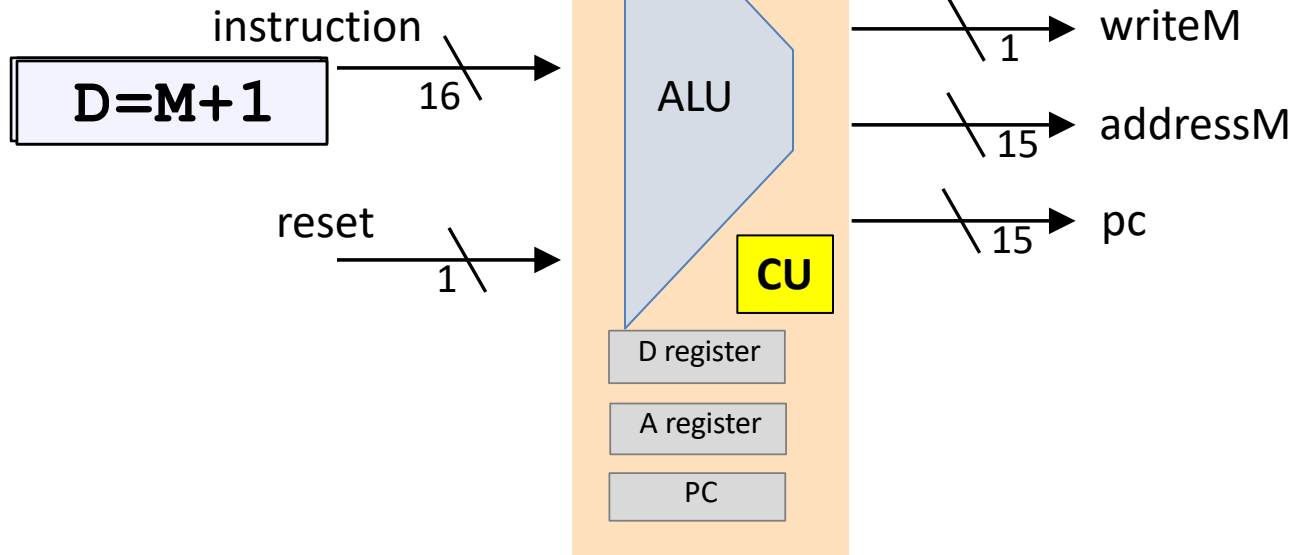



Execution of Instructions by Hack CPU

Reset Bit and PC:

If (reset == 1)

The 15 bit output **pc** emits 0, causing the program to restart

If (reset==0)

The CPU logic uses the instruction's jump bits and the ALU's output to decide if there should be a jump. For example:

```
@ 54
D - 1 ; JEQ
```


If (D-1==0)

PC is set to the value of the A-register

else


PC++

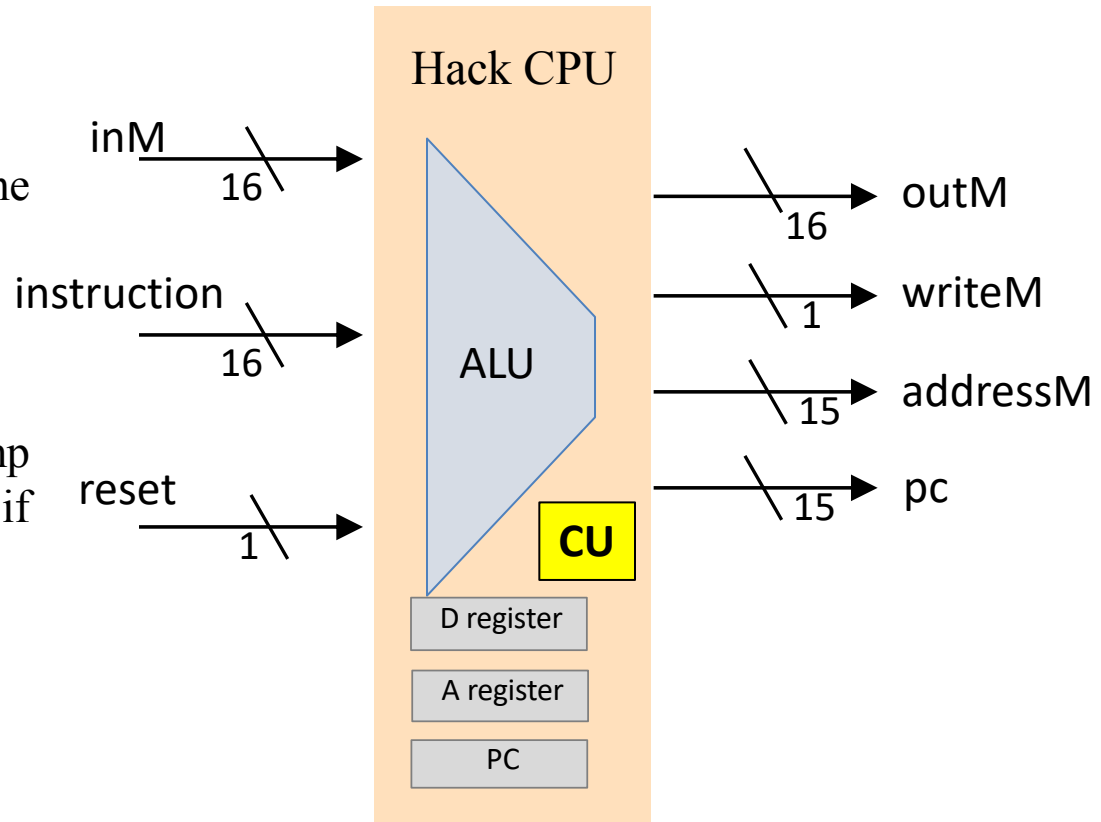The updated PC value is emitted by 15 bit output named **pc**






Hack CPU Implementation

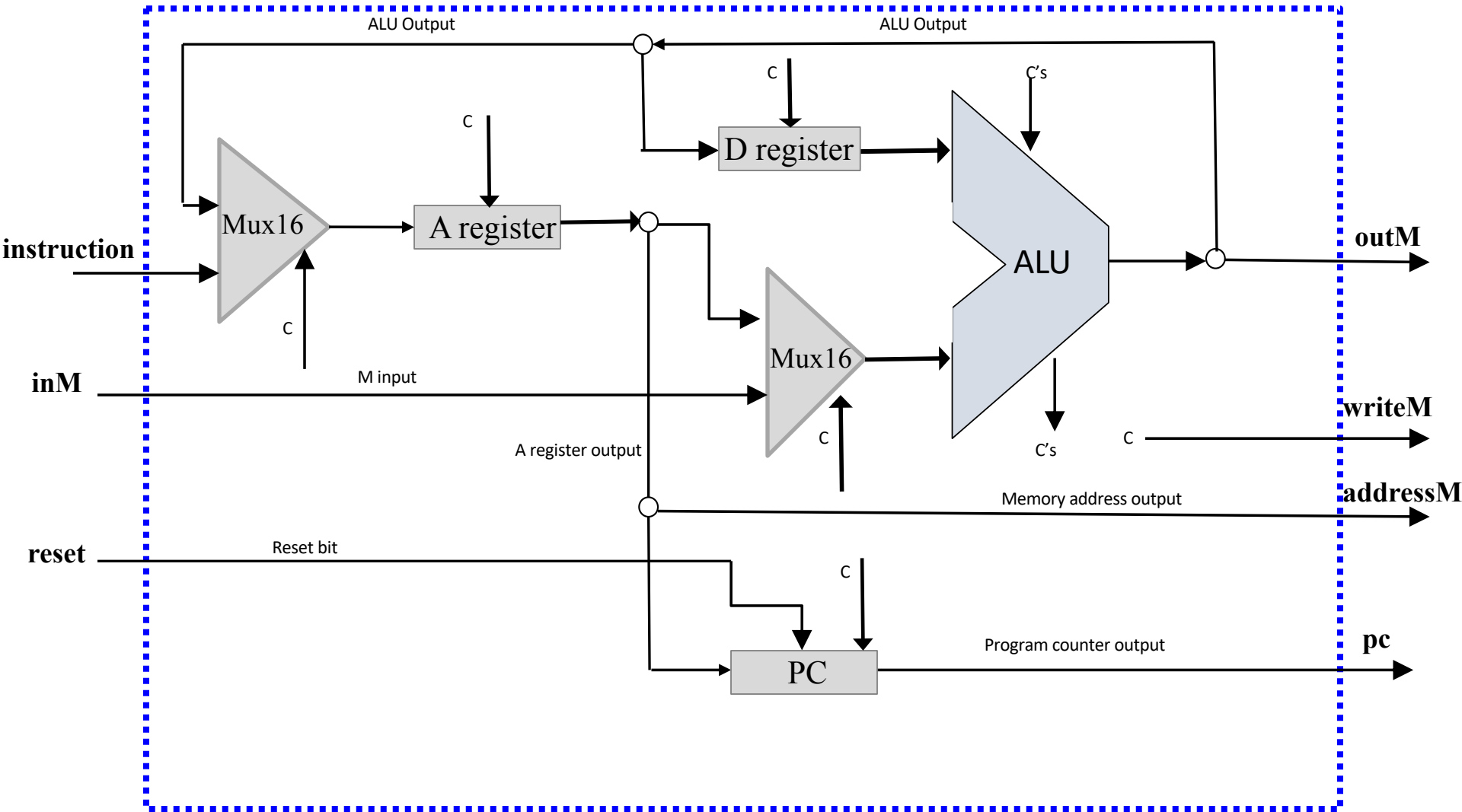

(each "C" symbol represents a control bit)




Instruction Handling

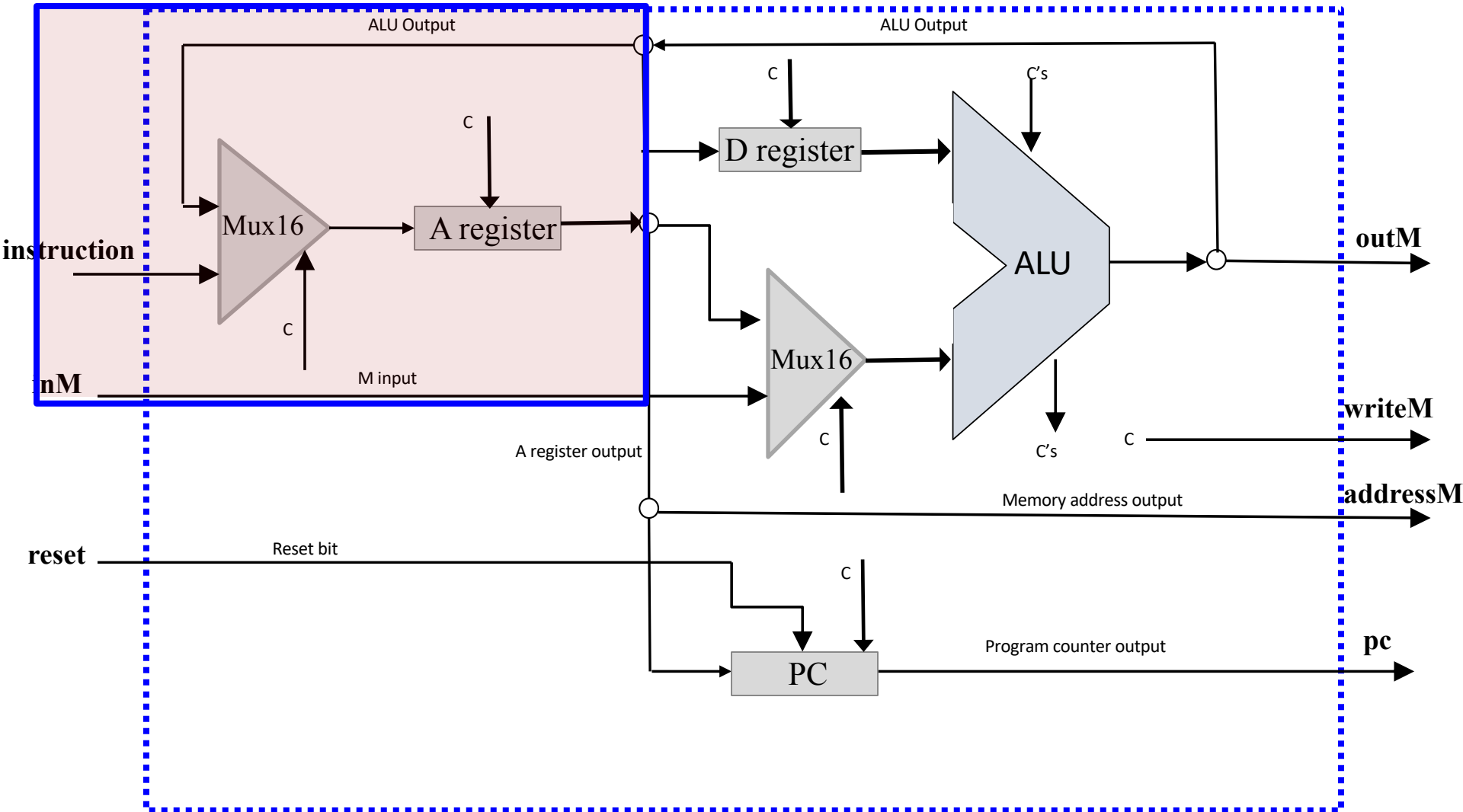



Handling A-Instruction

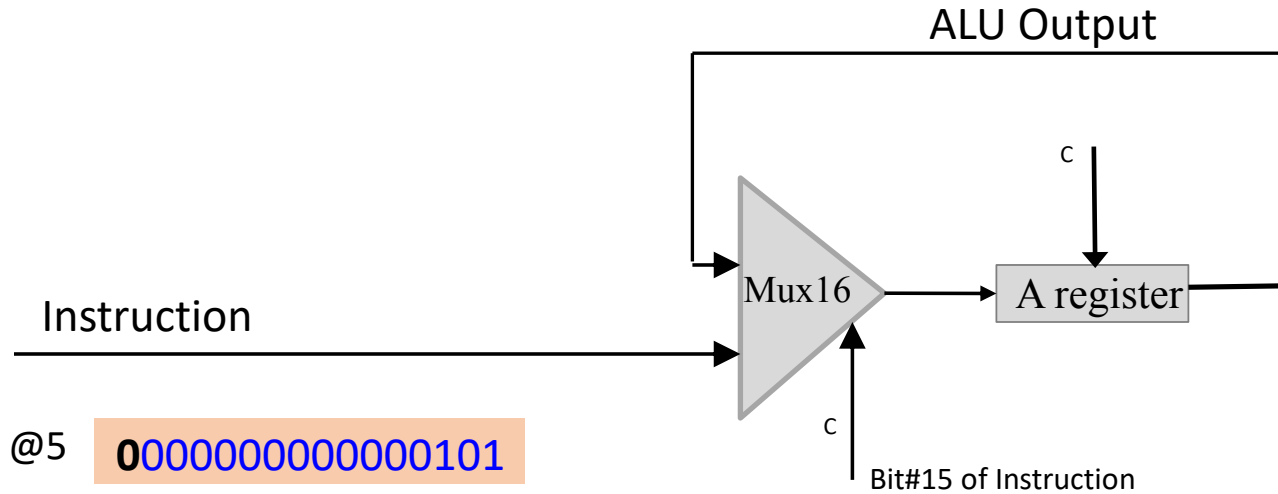

A-instruction

CPU handling of an A-instruction:


- Decodes the instruction into
 - op-code
 - 15-bit value
- Stores the 15 bit value in the A-register
- Outputs the value to ALU via Mux (not shown in this diagram)

Note:

- In case of A-instruction, the A-register get its input from the instruction part
- In case of C-instruction, the A-register get its input from the ALU output



Handling C-Instruction

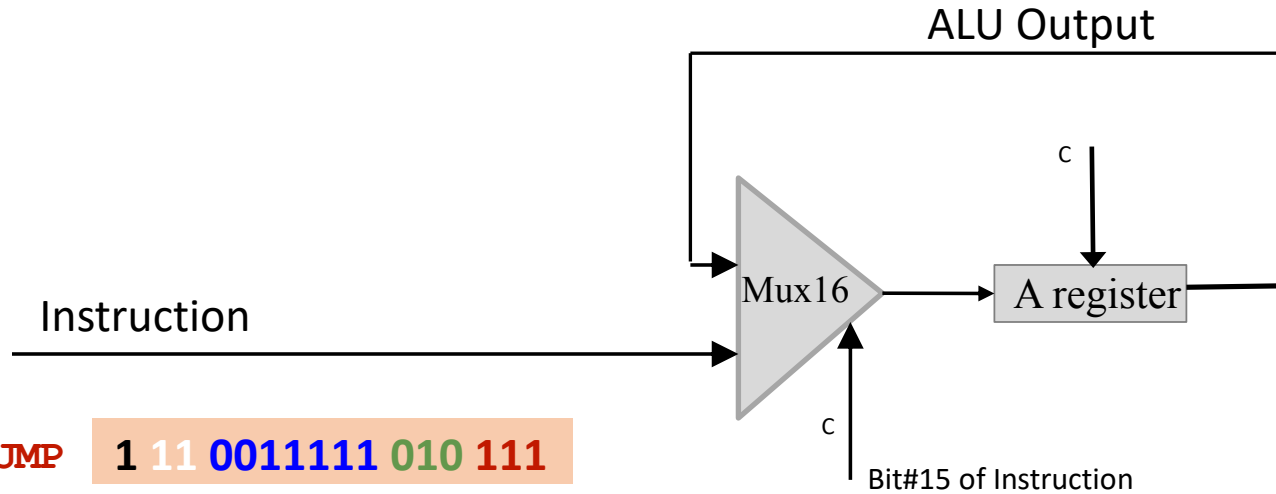

C-instruction


CPU handling of C-instruction:

`dest = comp ; jump`

- Decodes the instruction bits into:
 - Op-code
 - ALU control bits (D+1)
 - Destination load bits (D-Register)
 - Jump bits (Un-conditional jump)
- Routes these bits to their chip-part destinations
- The chip-parts (most notably, the ALU) execute the instruction




ALU Operation

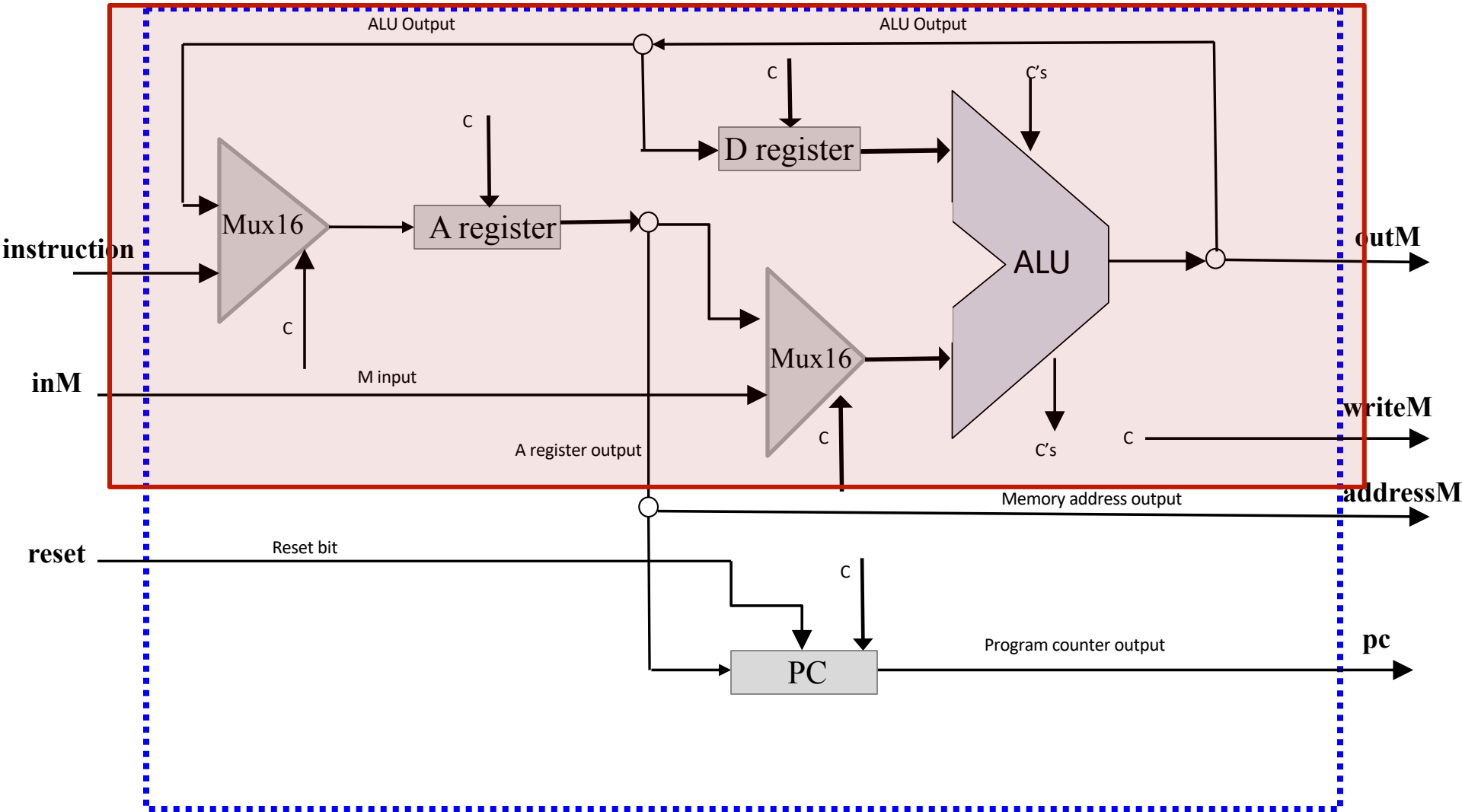



ALU Operation: Inputs

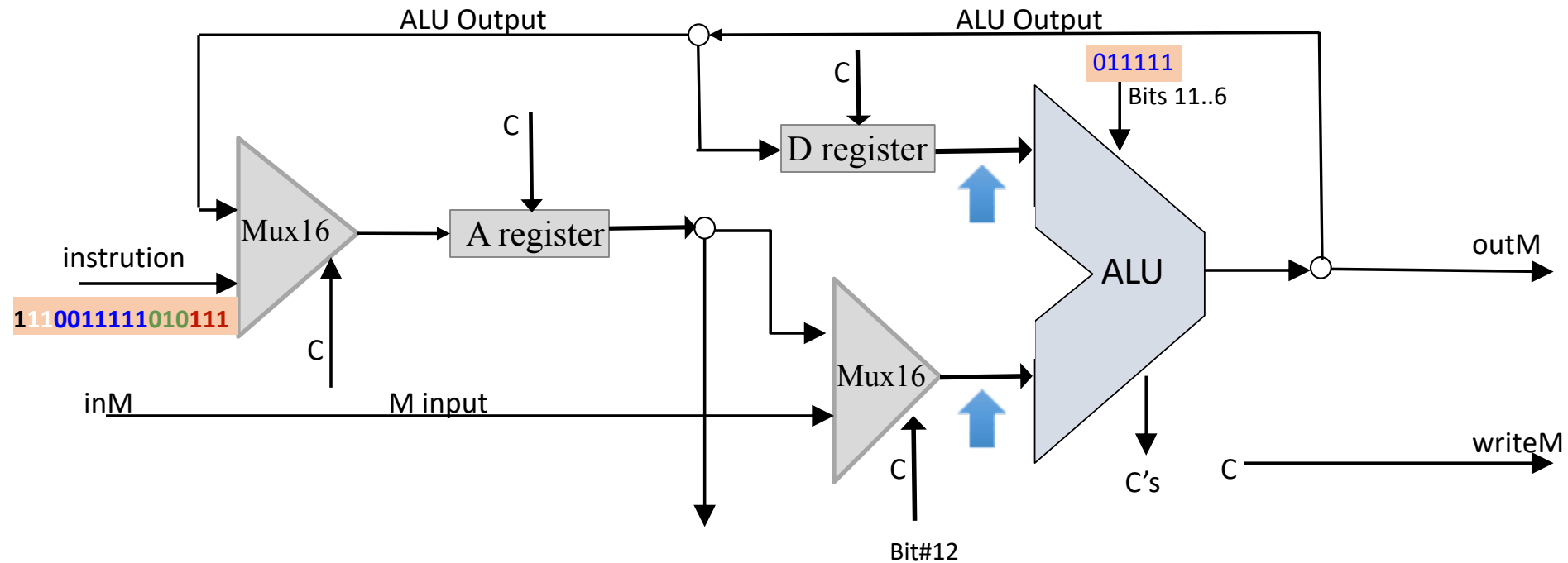

ALU data inputs:

- Input 1: From D-register
- Input 2: From A-register or M-register (decided by bit#12 of Instruction)


ALU control inputs:

- 6 x Control bits (from bits 6-11 of the instruction)

1 11 a cccccc ddd jjj



ALU Operation: Outputs

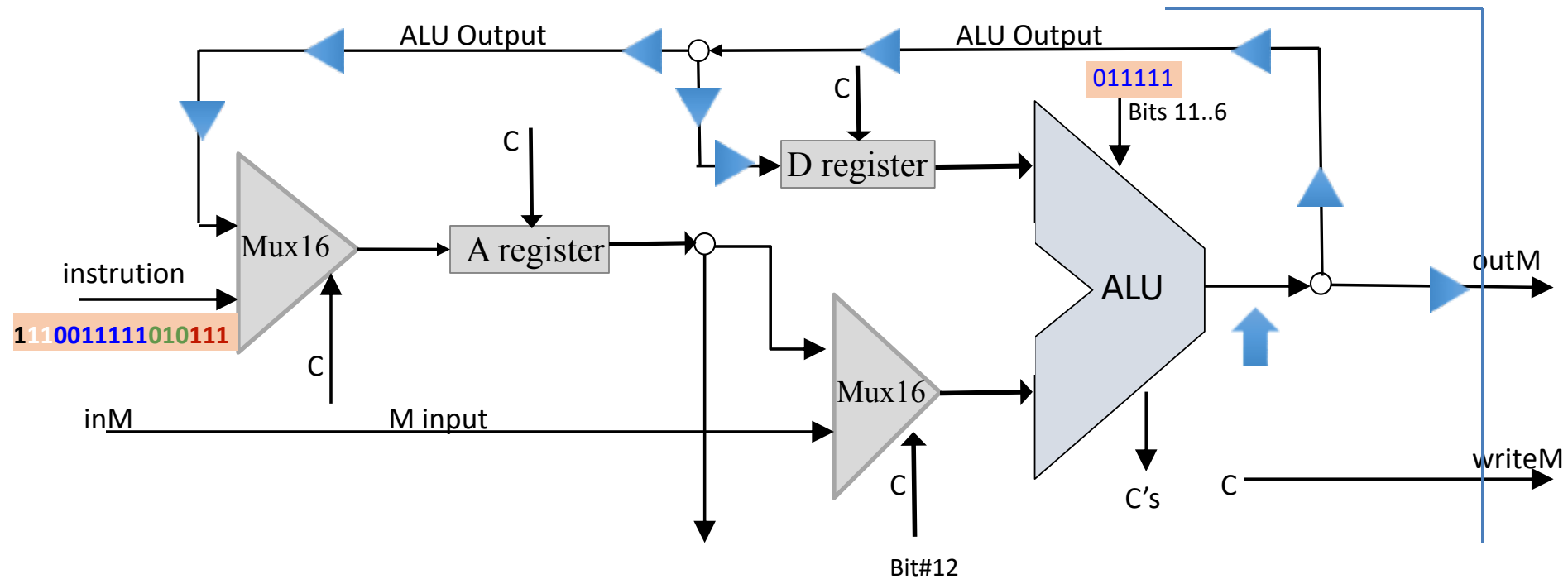


ALU data output:

- Result of ALU calculation, fed simultaneously to:
 - D-register, A-register, M-register (data memory)
- Which out of these three destinations actually commits to the ALU output is determined by the instruction's **destination bits** (010 means D-register)



ALU Operation: Control Outputs

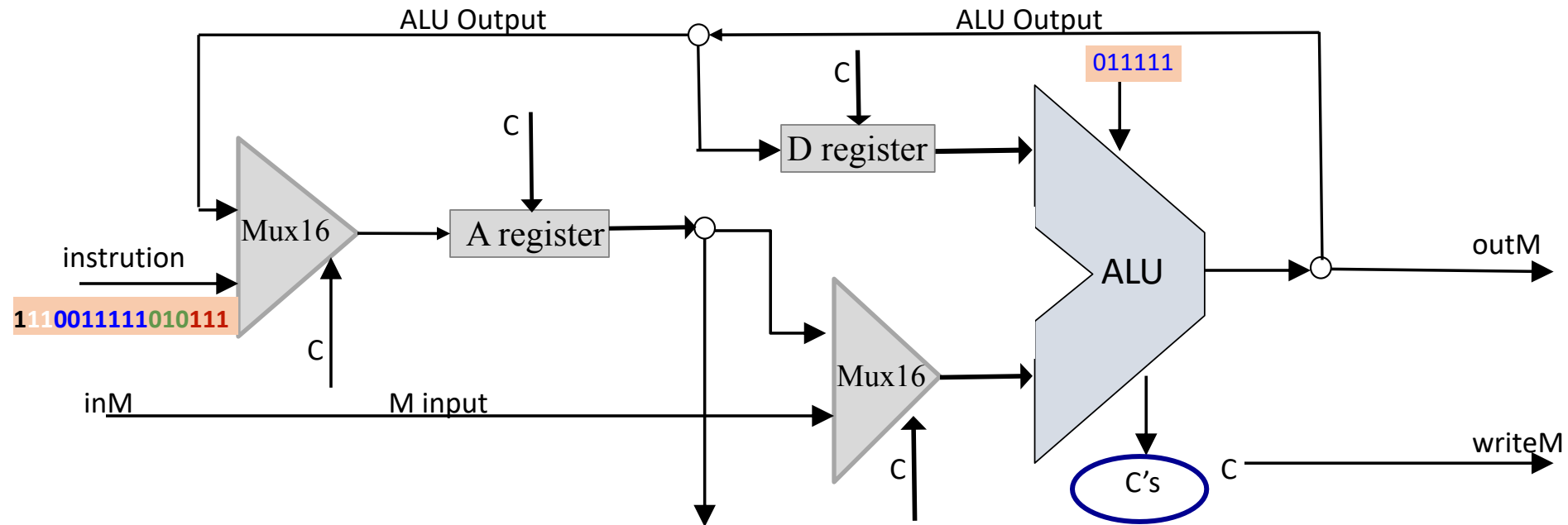


ALU control outputs:

- is the output negative? (`ng`)
- is the output zero? (`zr`)




Control Logic of CPU

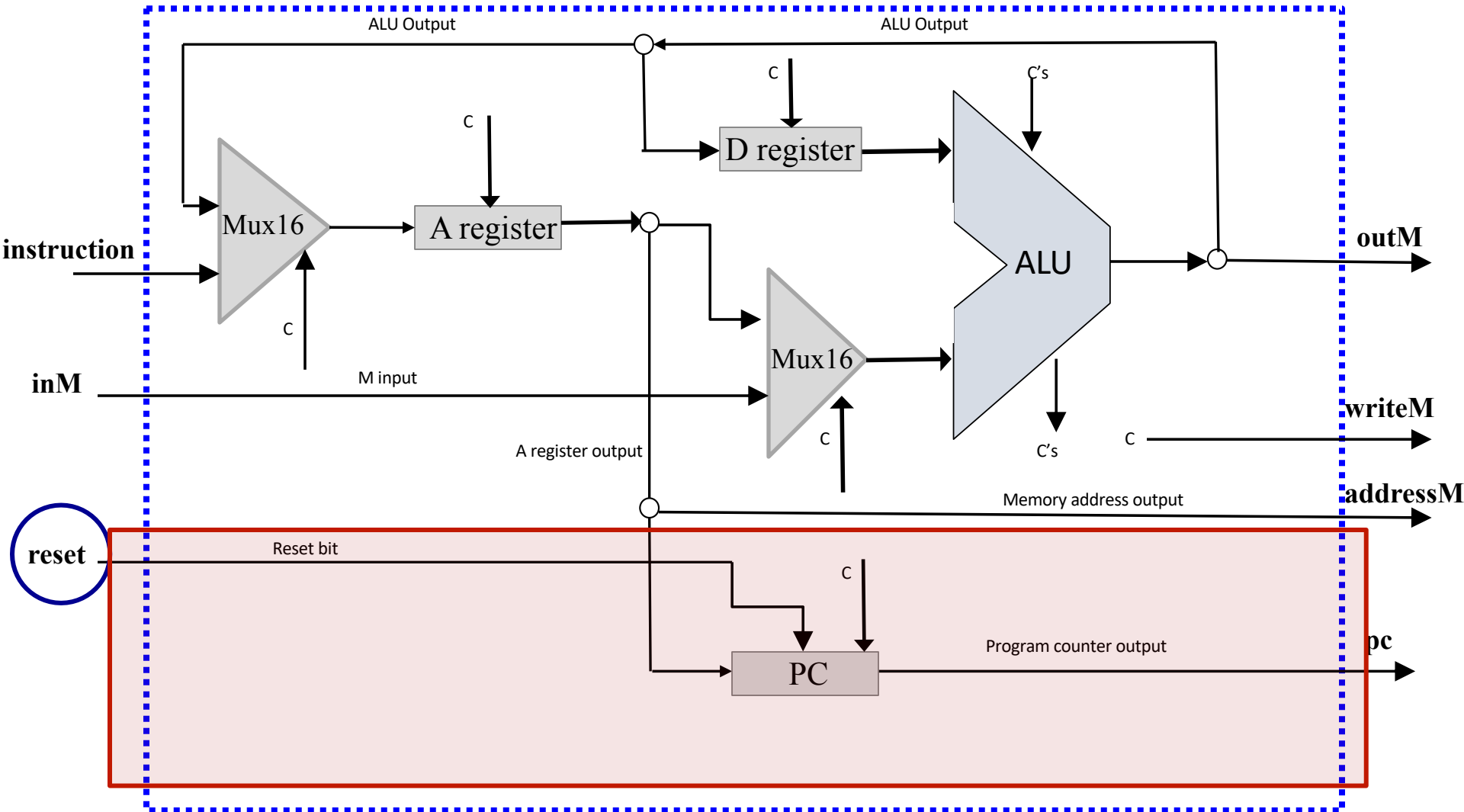

(each "C" symbol represents a control bit)




Possible Outside View of Hack Computer

 

- The computer is loaded with some program
- Pushing reset button causes the program to start running from beginning



Control Abstraction

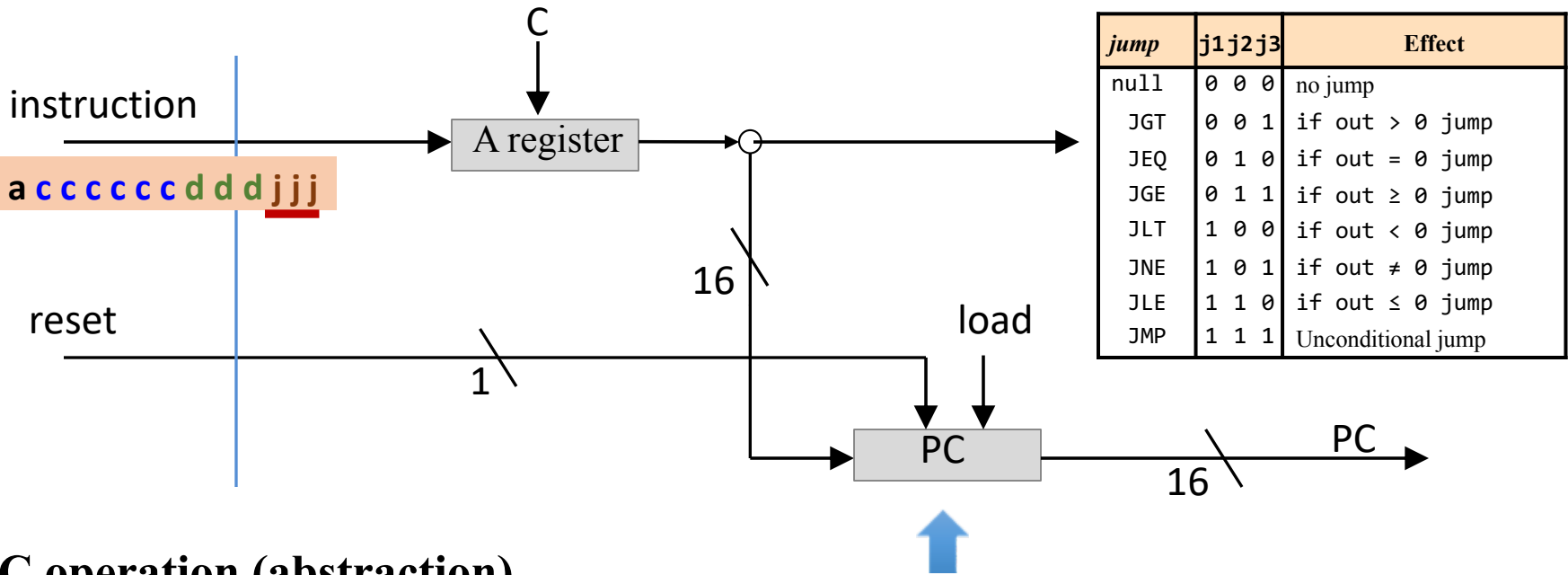


PC operation (abstraction)

- Emits the address of the next instruction
- restart PC=0
- no jump: PC++
- goto: PC=A
- conditional goto: if (condition) PC= A else PC++



Control Implementation

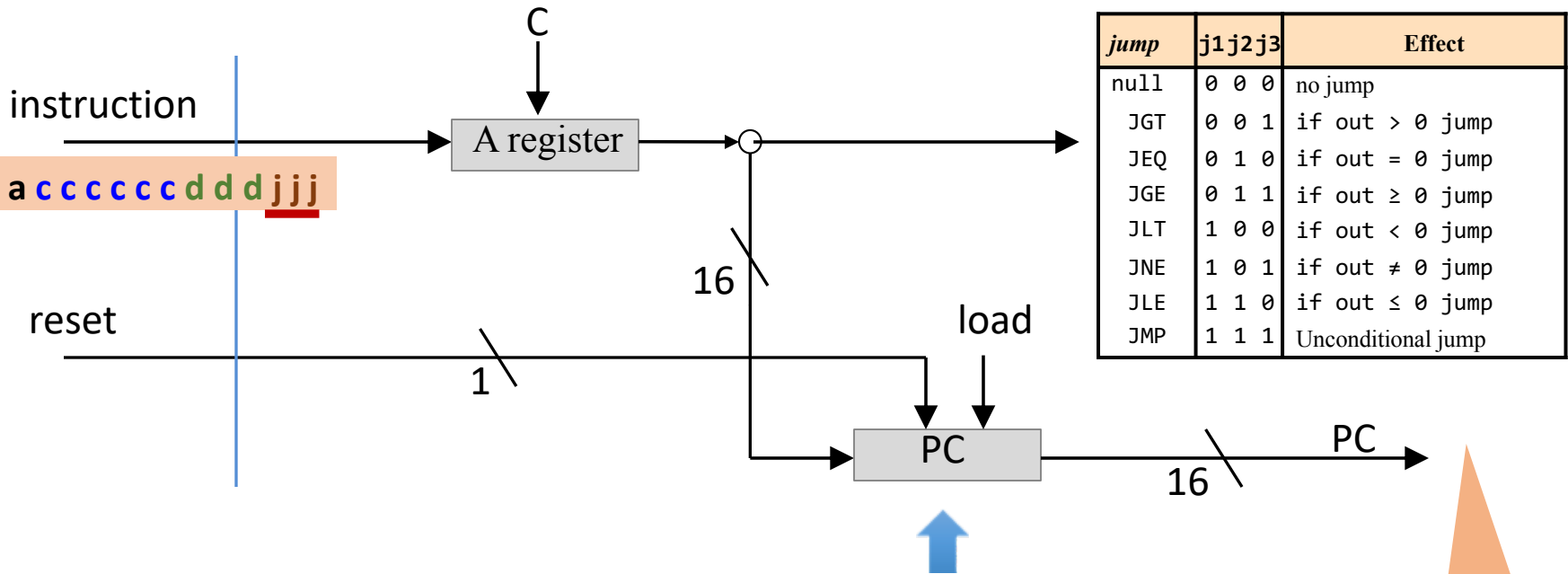

PC operation (implementation)

```
if (reset == 1)
```

```
    PC = 0
```

```
else
```

```
    load = f(jump bits, ALU control outputs (zr,ng))
```


```
    if (load == 1)    PC = A    // jump
```

```
    else            PC++      // next instruction
```

address of next instruction



Hack CPU Implementation

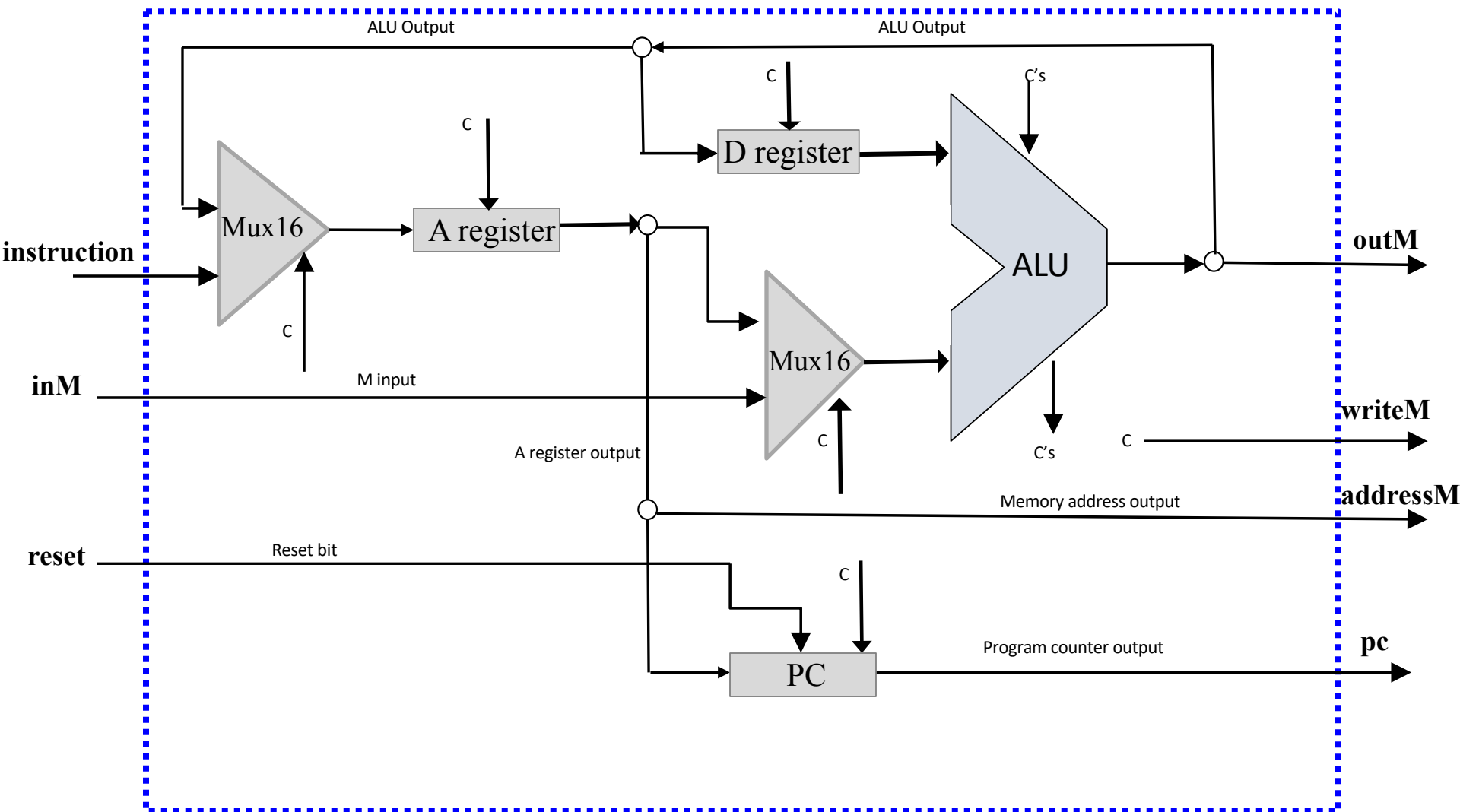

That's It! All that remains is to actually build it 😊



Things To Do

