
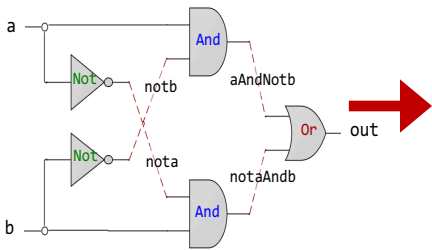


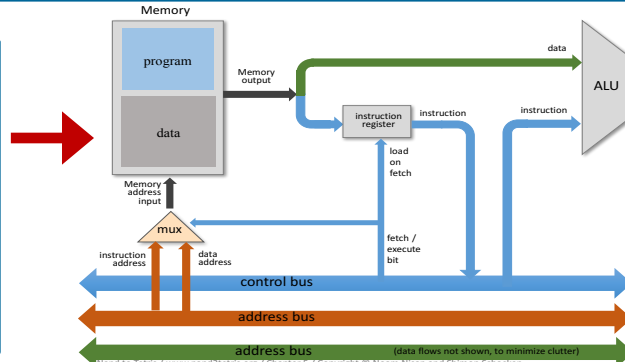


Computer Organization & Assembly Language Programming



```
CHIP Xor {
  IN a, b;
  OUT out;
  PARTS:
  Not(in=a, out=nota);
  Not(in=b, out=notb);
  And(a=nota, b=b, out=w1);
  And(a=a, b=notb, out=w2);
  Or(a=w1, b=w2, out=out);
}
```



```
@R1
D=M
@temp
M=D
```

 


Lecture # 24

Design of Hack Computer

```
#include<stdio.h>
#include<stdlib.h>
int main(){
  printf("Learning is fun with Arif\n");
  exit(0);
}
```
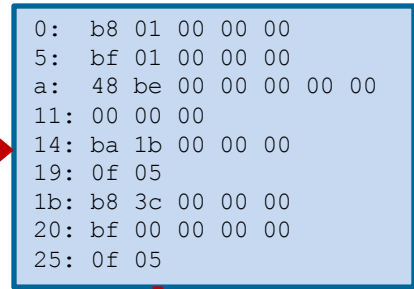
```
global main
SECTION .data
  msg: db "Learning is fun with Arif", 0Ah, 0h
  len_msg: equ $ - msg
SECTION .text
main:
  mov rax,1
  mov rdi,1
  mov rsi,msg
  mov rdx,len_msg
  syscall
  mov rax,60
  mov rdi,0
  syscall
```



Slides of first half of the course are adapted from:
<https://www.nand2tetris.org>
 Download s/w tools required for first half of the course from the following link:
<https://drive.google.com/file/d/0B9c0BdDjz6XpZUh3X2dPR1o0MUE/view>


Instructor: Muhammad Arif Butt, Ph.D.






Today's Agenda

 - Recap of Hack Computer Architecture
- Implementation of Hack CPU Chip (**CPU.hdl**)
- Implementation of Hack Memory Chip (**Memory.hdl**)
 - RAM16 chip (**RAM16K.hdl**)
 - Screen chip (**Screen.hdl**)
 - Keyboard chip (**Keyboard.hdl**)
- Implementation of Hack ROM Chip (**ROM32K.hdl**)
- Implementation of Hack Computer Chip (**Computer.hdl**)





Recap: Hack Computer Architecture

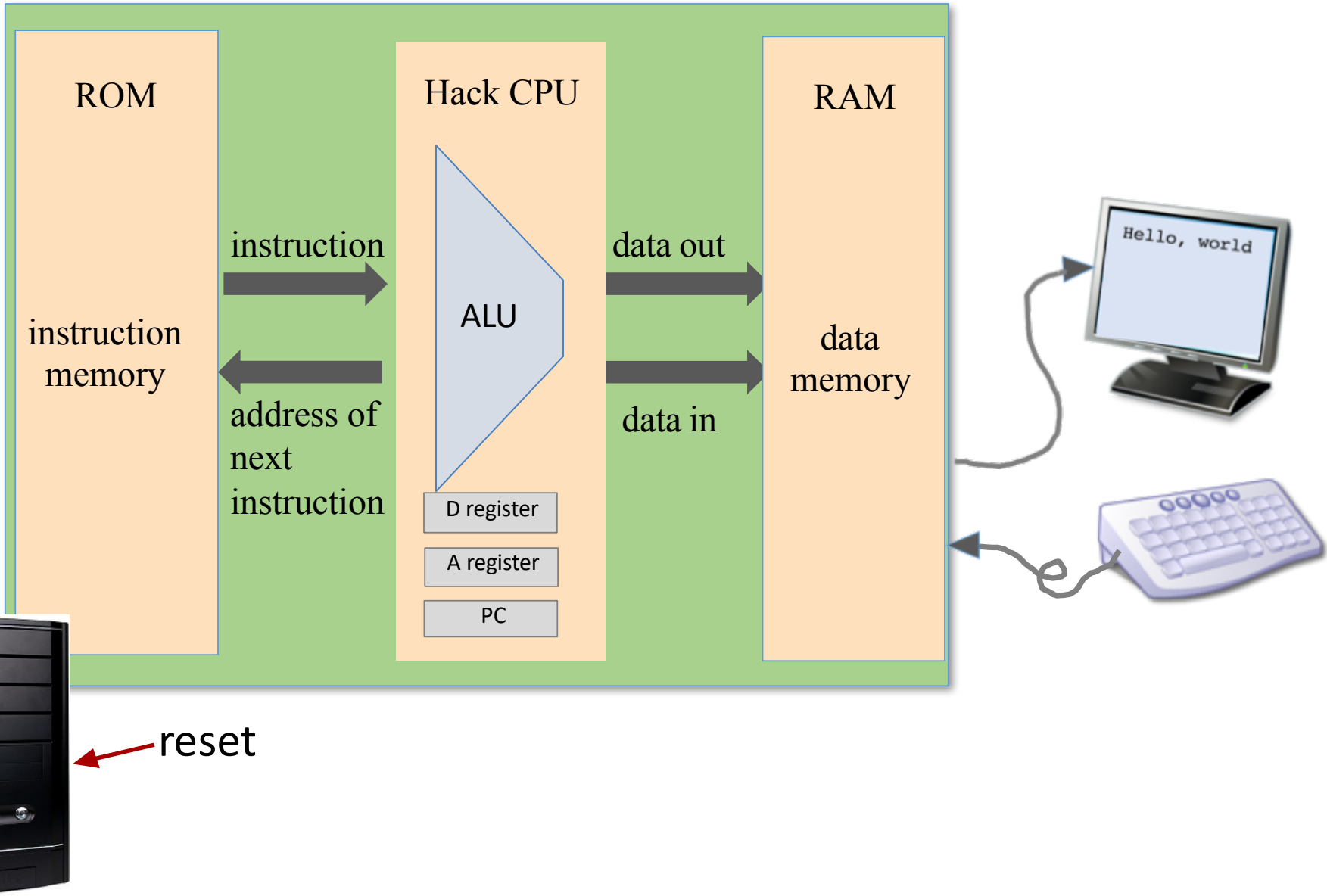




Implementation of Hack CPU Chip



Recap: Hack CPU Interface

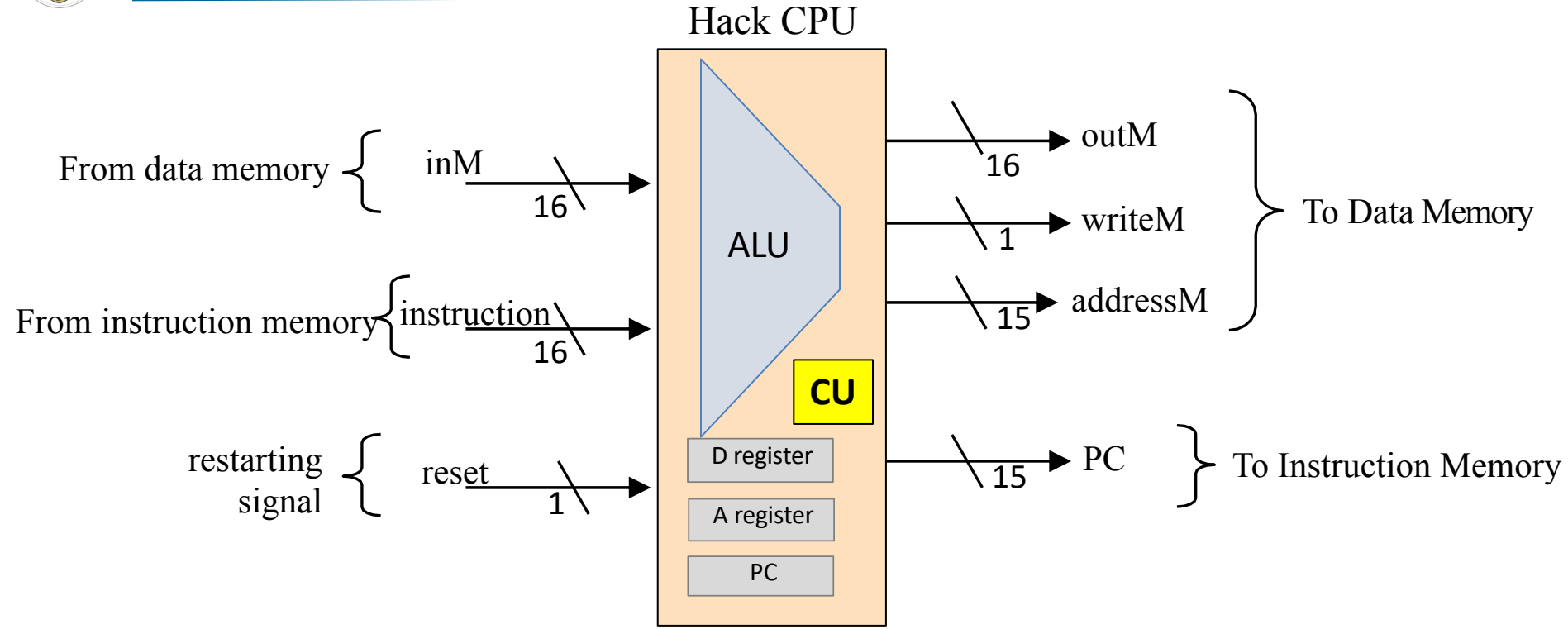

Inputs:


- Data Value
- Instruction
- Reset Bit

Outputs:

- Data Value
- Write to Memory? (yes/no)
- Memory Address
- Address of next instruction




Chip Parts of Hack CPU and their Control

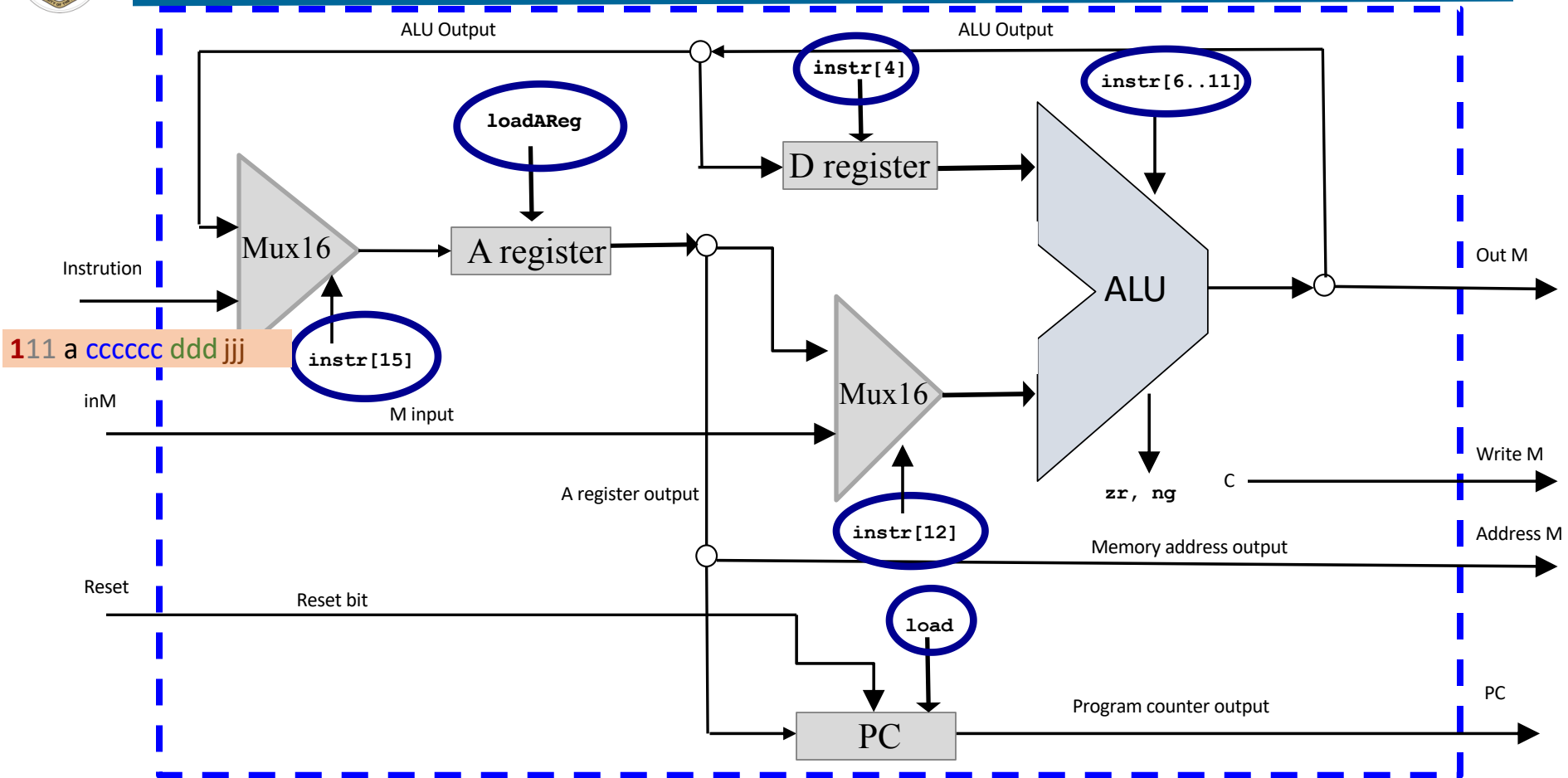




Select Input of First Mux16 Chip

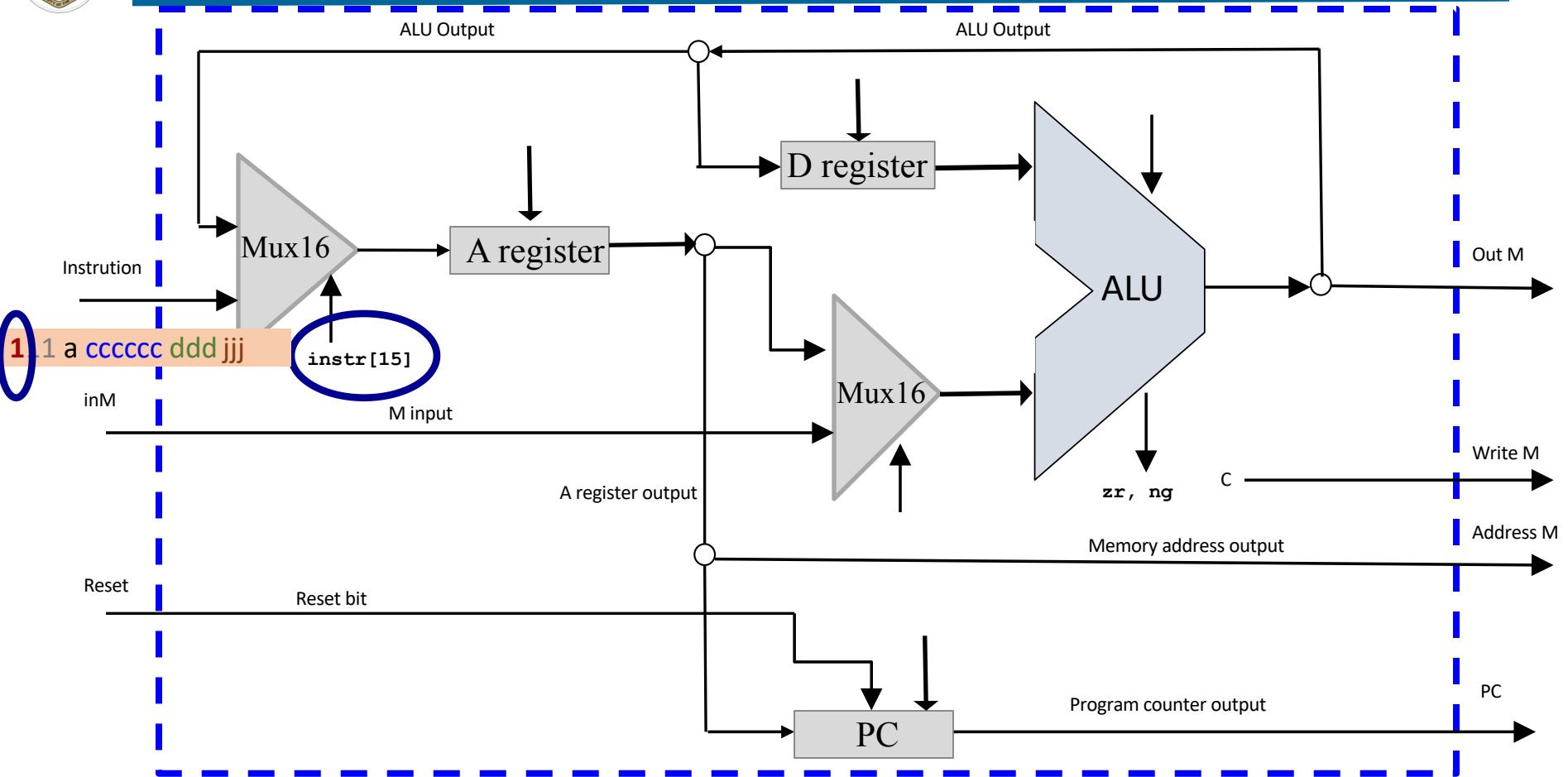




Select Input of Second Mux16 Chip

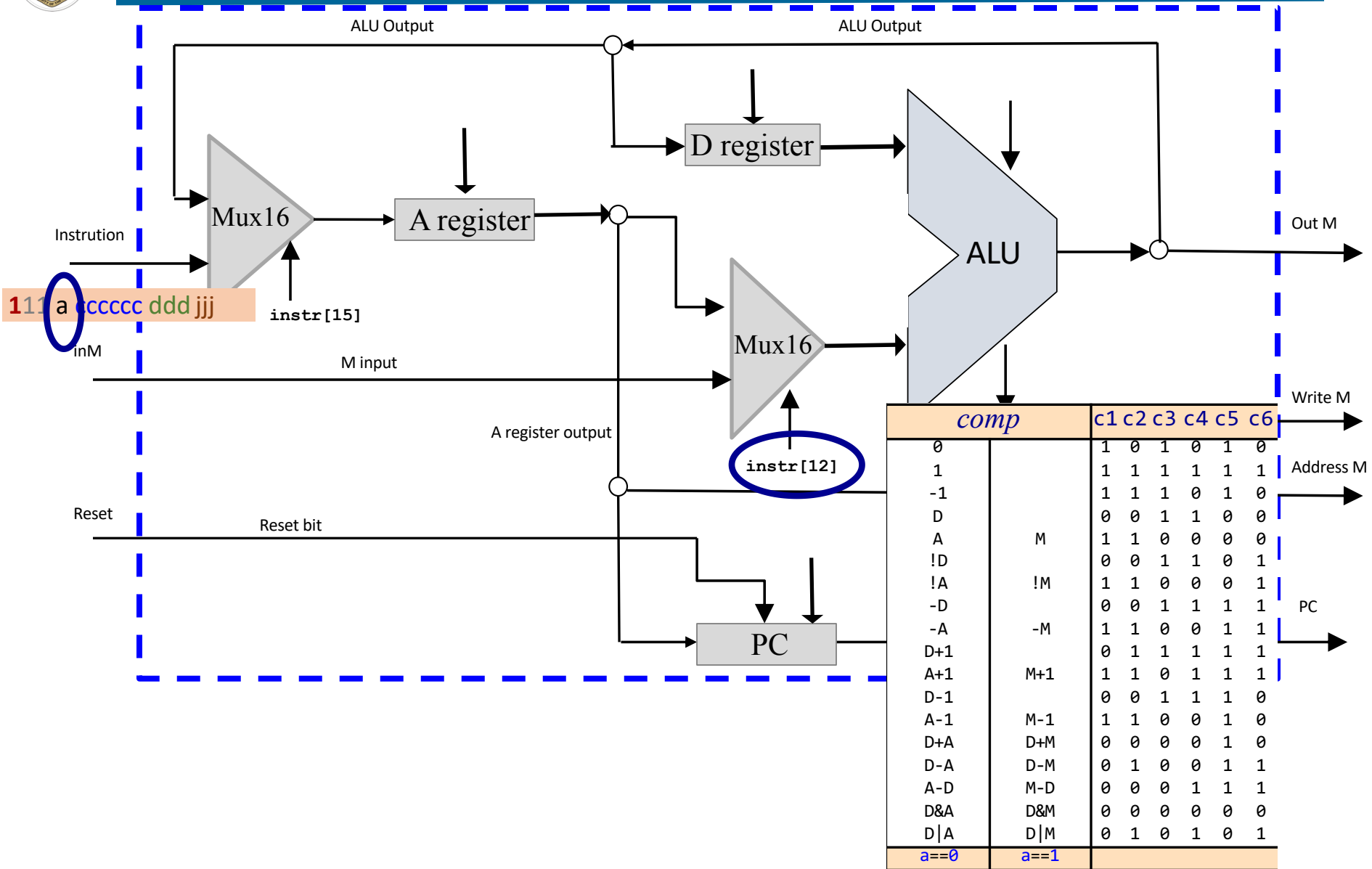




Load Input of A-Register Chip

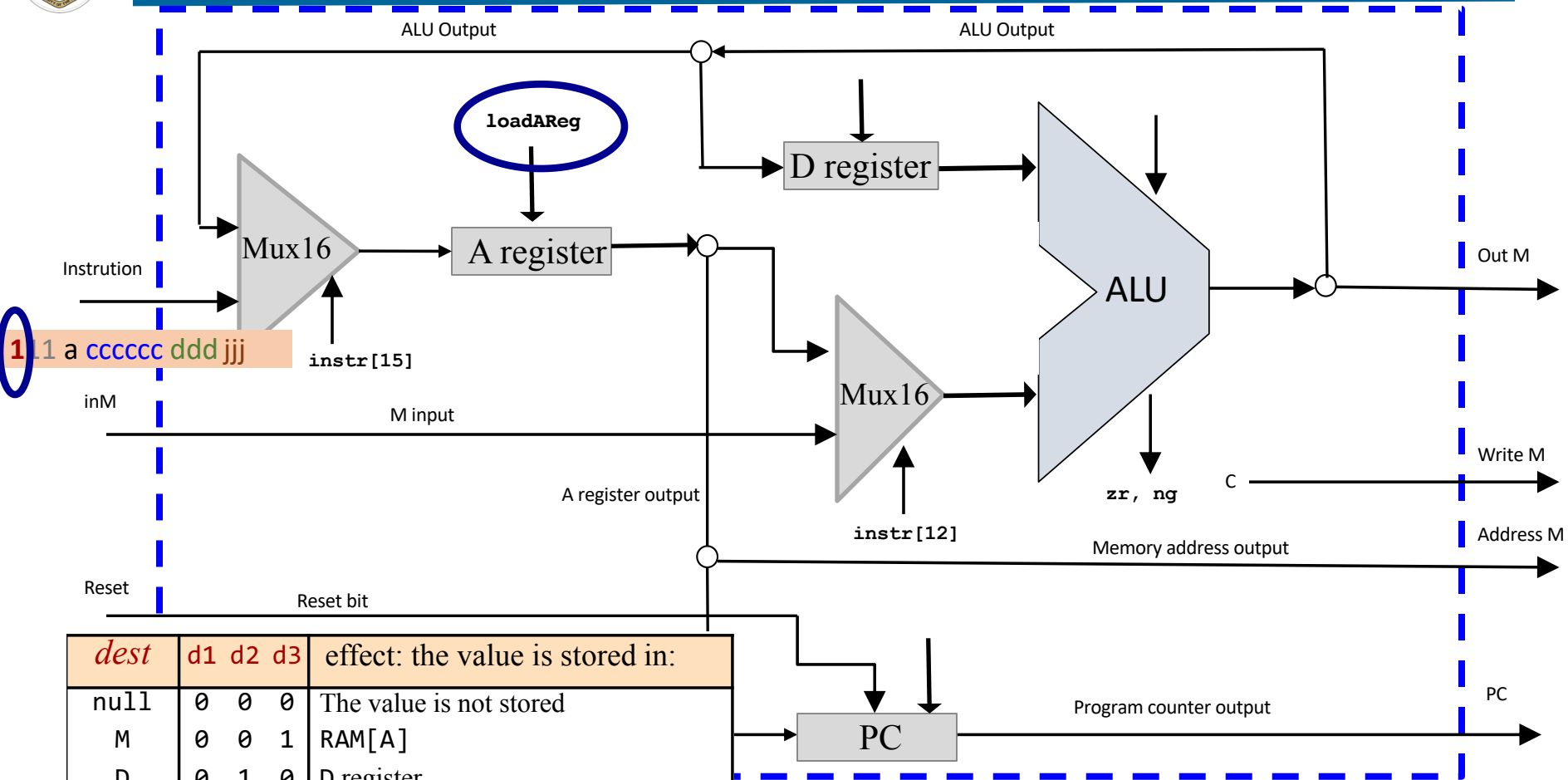

<i>dest</i>	d1	d2	d3	effect: the value is stored in:
null	0	0	0	The value is not stored
M	0	0	1	RAM[A]
D	0	1	0	D register
MD	0	1	1	RAM[A] and D register
A	1	0	0	A register
AM	1	0	1	A register and RAM[A]
AD	1	1	0	A register and D register
AMD	1	1	1	A register, RAM[A], and D register




Load Input of D-Register Chip

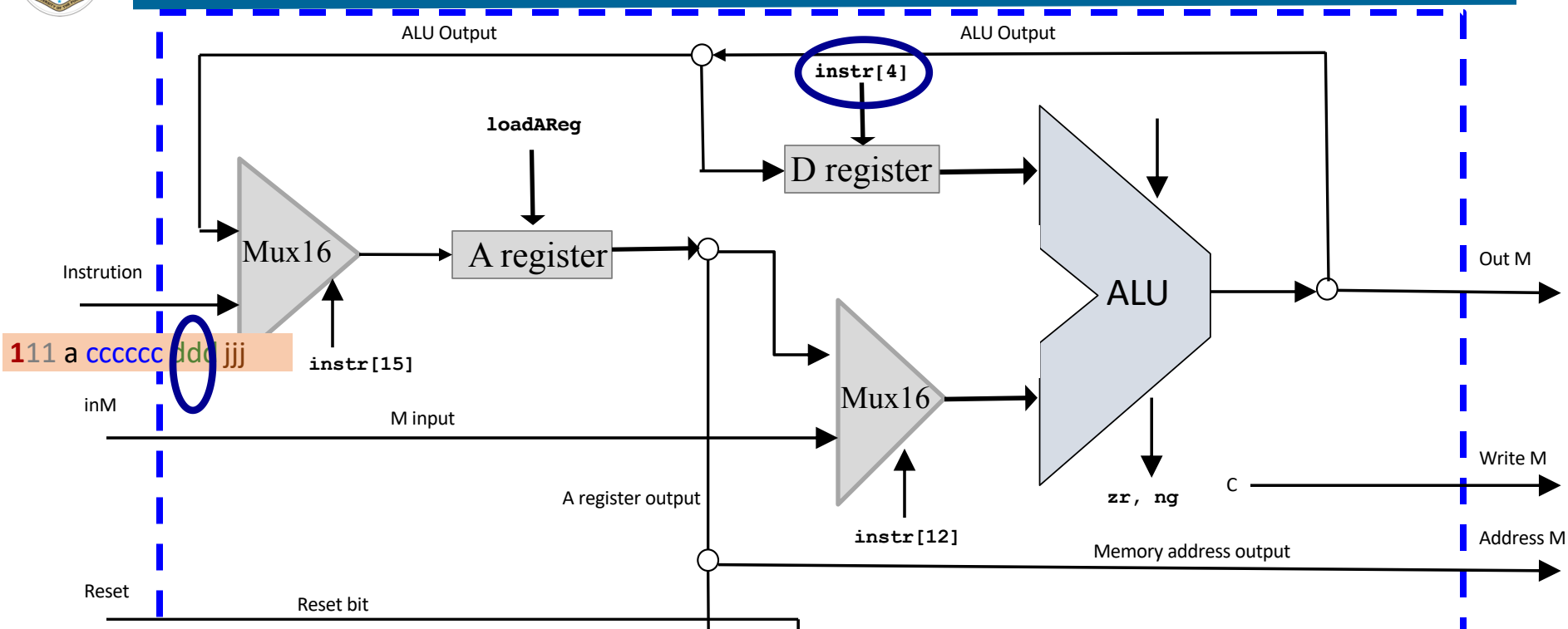

<i>dest</i>	<i>d1</i>	<i>d2</i>	<i>d3</i>	effect: the value is stored in:
null	0	0	0	The value is not stored
M	0	0	1	RAM[A]
D	0	1	0	D register
MD	0	1	1	RAM[A] and D register
A	1	0	0	A register
AM	1	0	1	A register and RAM[A]
AD	1	1	0	A register and D register
AMD	1	1	1	A register, RAM[A], and D register



Load Input of PC-Register

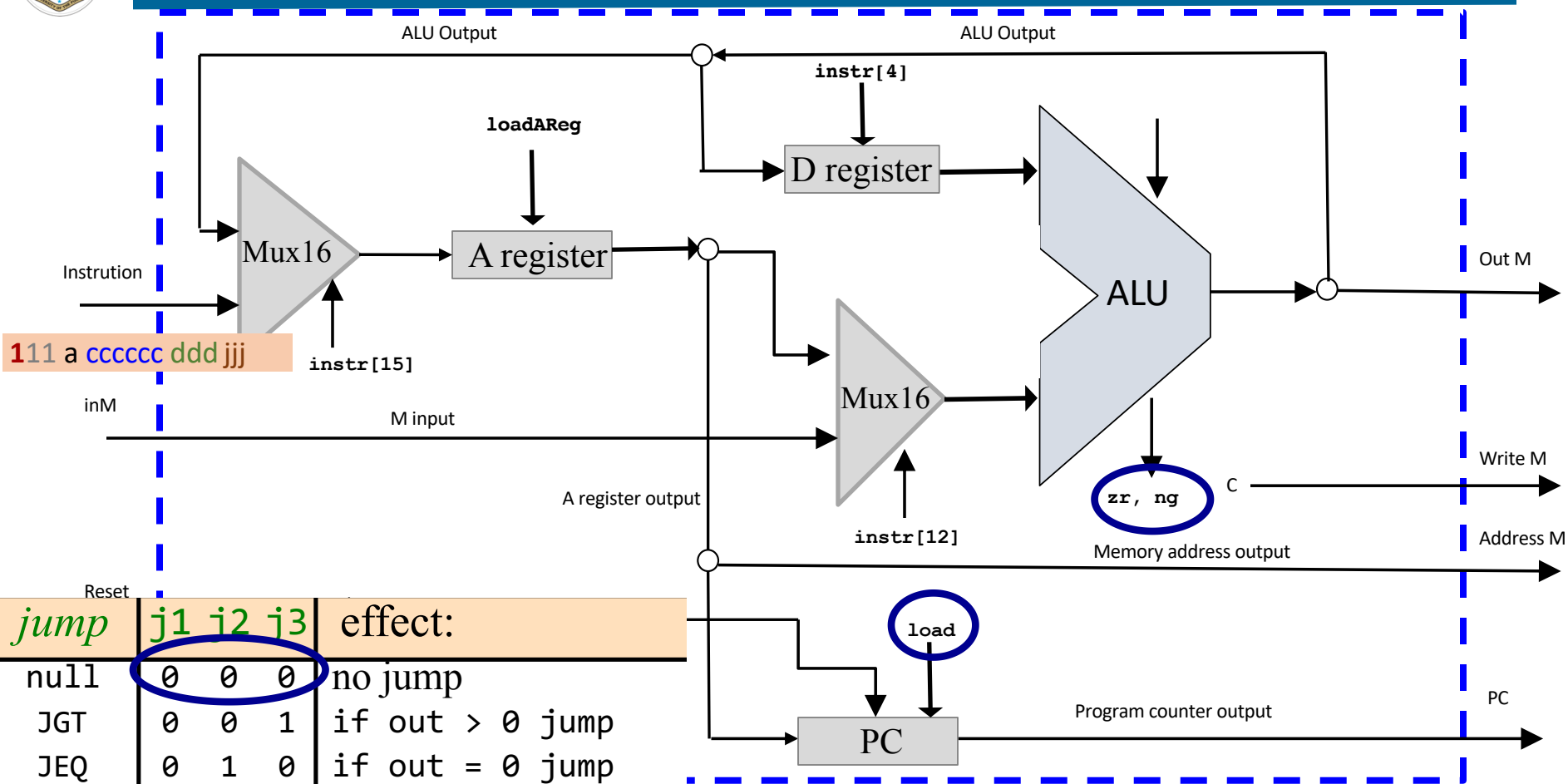


<i>jump</i>	<i>j1</i>	<i>i2</i>	<i>j3</i>	effect:
null	0	0	0	no jump
JGT	0	0	1	if out > 0 jump
JEQ	0	1	0	if out = 0 jump
JGE	0	1	1	if out ≥ 0 jump
JLT	1	0	0	if out < 0 jump
JNE	1	0	1	if out ≠ 0 jump
JLE	1	1	0	if out ≤ 0 jump
JMP	1	1	1	Unconditional jump

$load = f(\text{jump bits}, \text{zr/ng bits})$
 if (load == 1)
 $PC = A$



Control Input of ALU Chip

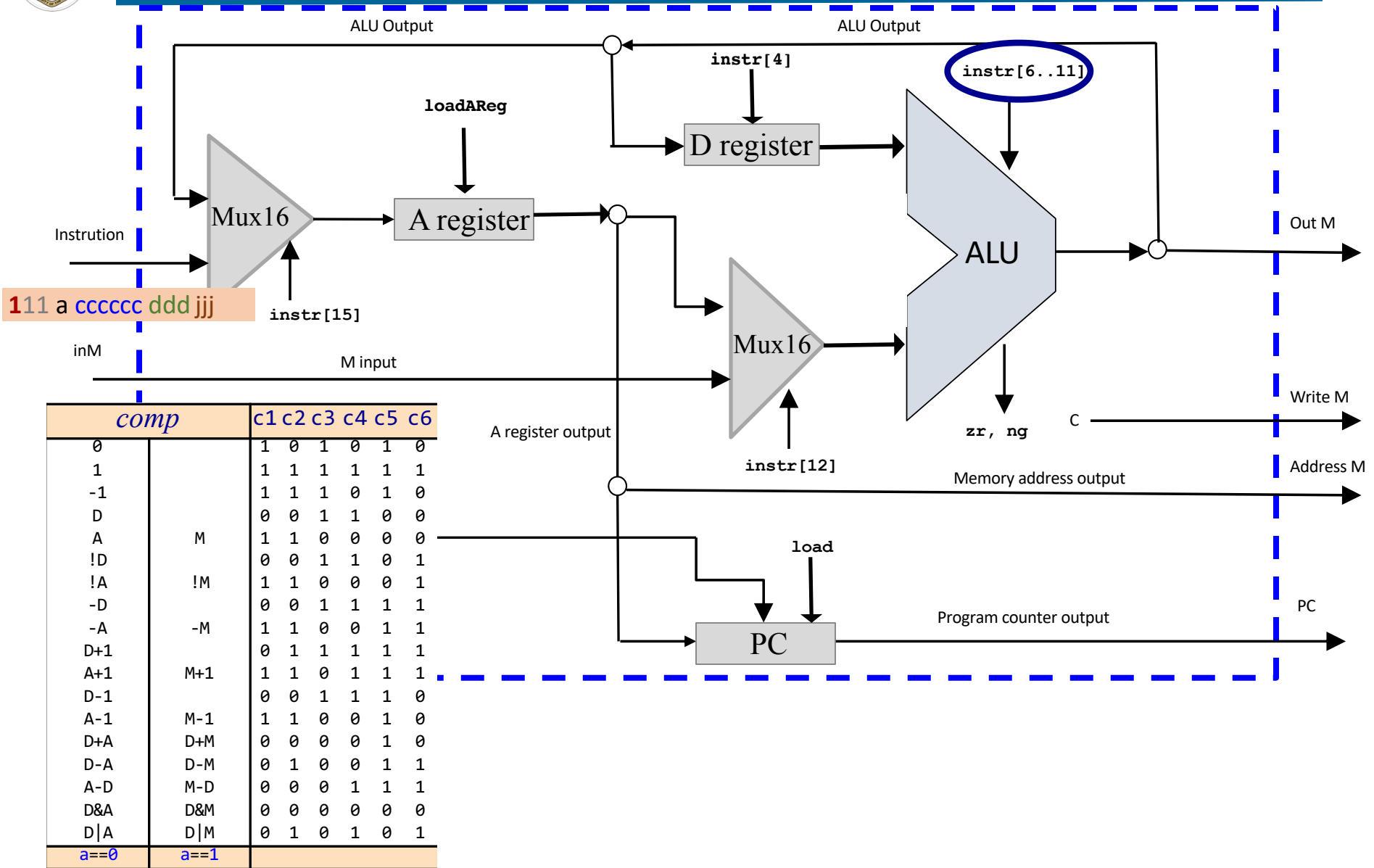



CPU Implementation

```
/** CPU.hdl
```

The Hack CPU (Central Processing unit), consisting of an ALU, two registers named A and D, and a program counter named PC. The CPU is designed to fetch and execute instructions written in the Hack machine language. In particular, functions as follows:

Executes the inputted instruction according to the Hack machine language specification. The D and A in the language specification refer to CPU-resident registers, while M refers to the external memory location addressed by A, i.e. to Memory[A]. The inM input holds the value of this location. If the current instruction needs to write a value to M, the value is placed in outM, the address of the target location is placed in the addressM output, and the writeM control bit is asserted. (When writeM==0, any value may appear in outM). The outM and writeM outputs are combinational: they are affected instantaneously by the execution of the current instruction. The addressM and pc outputs are clocked: although they are affected by the execution of the current instruction, they commit to their new values only in the next time step. If reset==1 then the CPU jumps to address 0 (i.e. pc is set to 0 in next time step) rather than to the address resulting from executing the current instruction.

```
*/
```


```
CHIP CPU {
```

```
    IN inM[16],          // M value input (M = contents of RAM[A])
        instruction[16], // Instruction for execution
        reset;          // Signals whether to re-start the current
                        // program (reset==1) or continue executing
                        // the current program (reset==0).
```

```
    OUT outM[16],       // M value output
        writeM,         // Write to M?
        addressM[15],  // Address in data memory (of M)
        pc[15];        // address of next instruction
```

```
    PARTS:
```
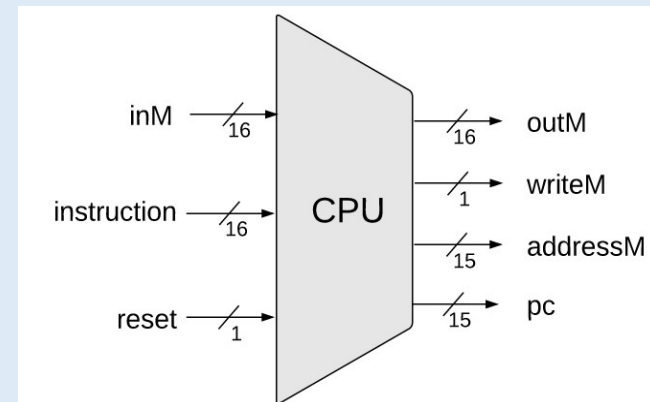
```
    // Chip implementation code on next slide
```





CPU Implementation

CPU.hdl (cont...)

PARTS:

```
Not(in=instruction[15],out=Ainst);
Not(in=Ainst,out=Cinst);
Mux16(a=instruction, b=ALUout, sel=Cinst, out=ARegBefore);
And(a=instruction[5], b=Cinst, out=d1); // instruction[5] = d1 if it's a C instruction
Or(a=d1, b=Ainst, out=storeAReg);
ARegister(in=ARegBefore, load=storeAReg, out=A, out[0..14]=addressM);
Mux16(a=A, b=inM, sel=instruction[12], out=MOrA); // instruction[12] = a
And(a=instruction[4], b=Cinst, out=d2); // instruction[4] = d2 if it's a C instruction
DRegister(in=ALUout, load=d2, out=D);


ALU(x=D, y=MOrA, zx=instruction[11], nx=instruction[10], zy=instruction[9],
    ny=instruction[8], f=instruction[7], no=instruction[6], out=ALUout, out=outM, zr=zr, ng=ng);

And(a=instruction[3], b=Cinst, out=writeM); // instruction[2] = d3 if it's a C instruction
Not(in=zr, out=notzr);
Not(in=ng, out=notng);
And(a=notzr, b=notng, out=pos);
And(a=instruction[2], b=ng, out=jneg);
And(a=instruction[1], b=zr, out=jzer);
And(a=instruction[0], b=pos, out=jpos);
Or(a=jneg, b=jzer, out=jzerneg);
Or(a=jzerneg, b=jpos, out=jumpIfCinst);
And(a=jumpIfCinst, b=Cinst, out=jump);

PC(in=A, load=jump, inc=true, reset=reset, out[0..14]=pc);
}
```



The Hack Computer

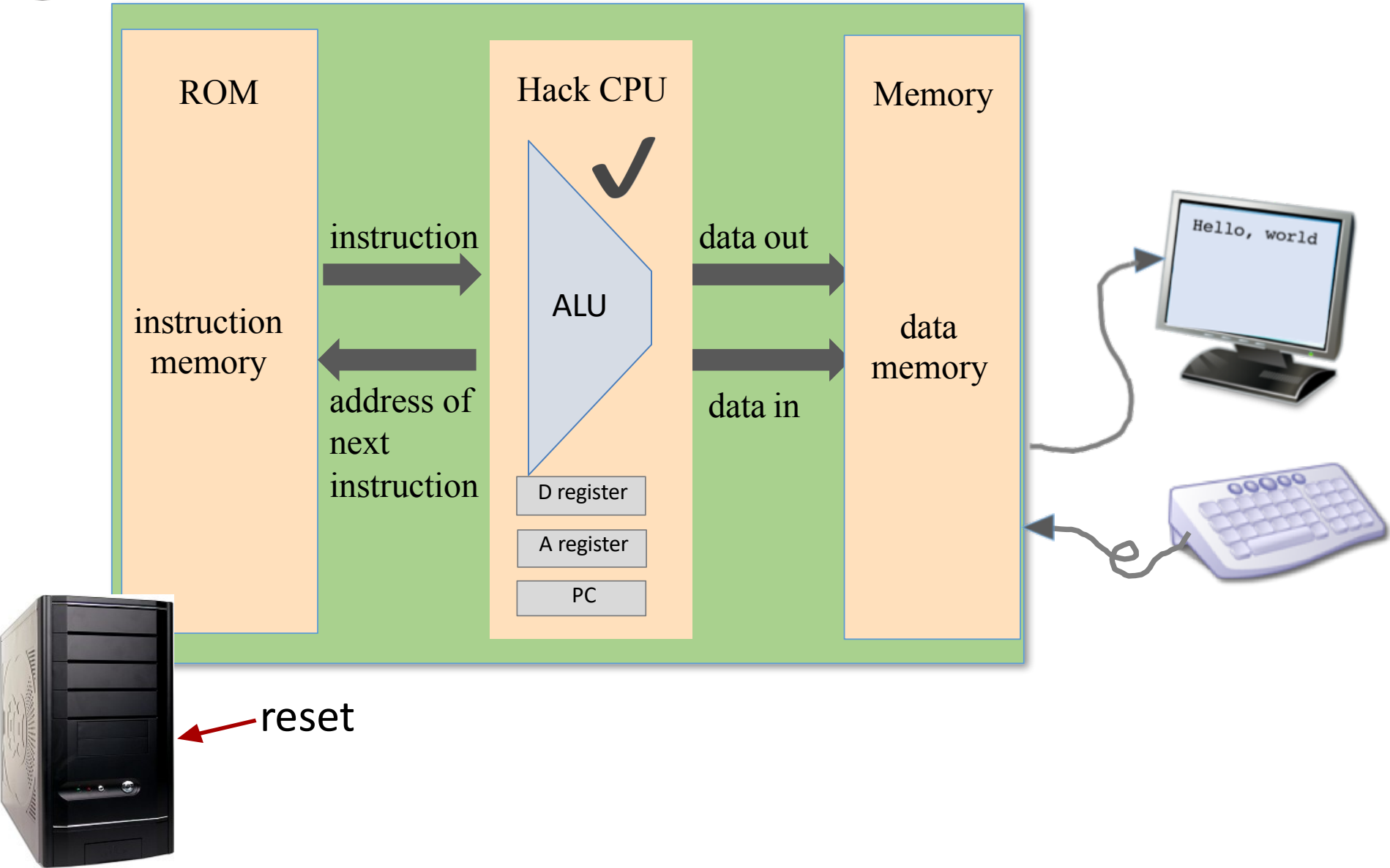




Implementation of Hack Memory Chip





Memory Chip

 

- **RAM/Data Memory:** 16 bit, 16K RAM Chip (address 0 to 16383)
- **Screen Memory Map:** 16 bit, 8K memory Chip with a raster display side effect (16384 to 24575)
- **Keyboard Memory Map:** 16 bit register with a keyboard side effect (address 24576)



RAM16 Chip Implementation

 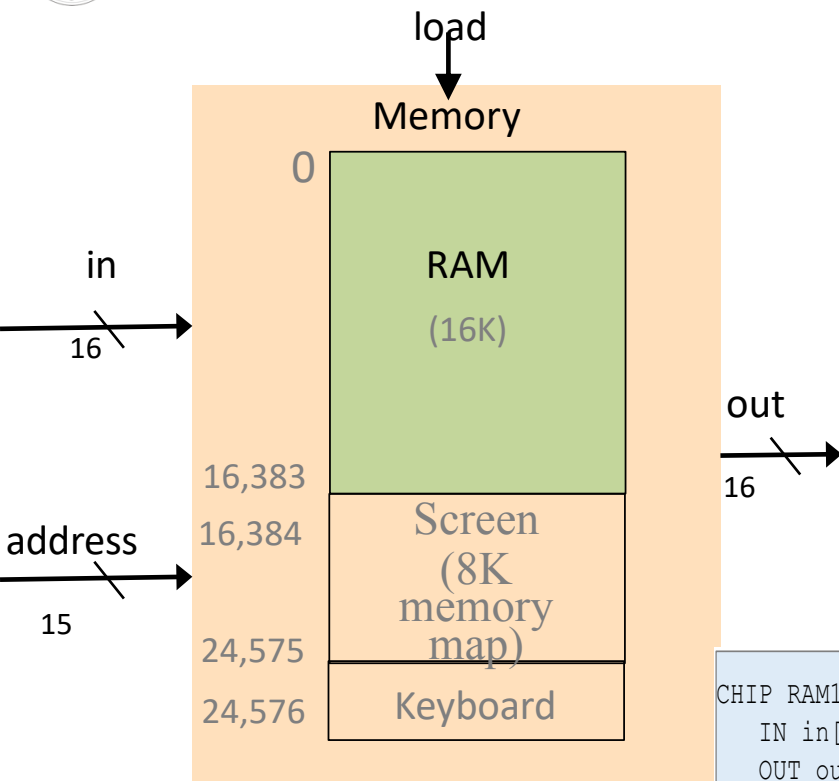

```
CHIP RAM16K {
  IN in[16], load, address[14];
  OUT out[16];
  PARTS:
  DMux4Way(in=load, sel=address[12..13], a=load0, b=load1, c=load2, d=load3);


  RAM4K(in=in, load=load0, address=address[0..11], out=out0);
  RAM4K(in=in, load=load1, address=address[0..11], out=out1);
  RAM4K(in=in, load=load2, address=address[0..11], out=out2);
  RAM4K(in=in, load=load3, address=address[0..11], out=out3);

  Mux4Way16(a=out0, b=out1, c=out2, d=out3, sel=address[12..13], out=out);
}
```



Screen Built-in Chip

Memory

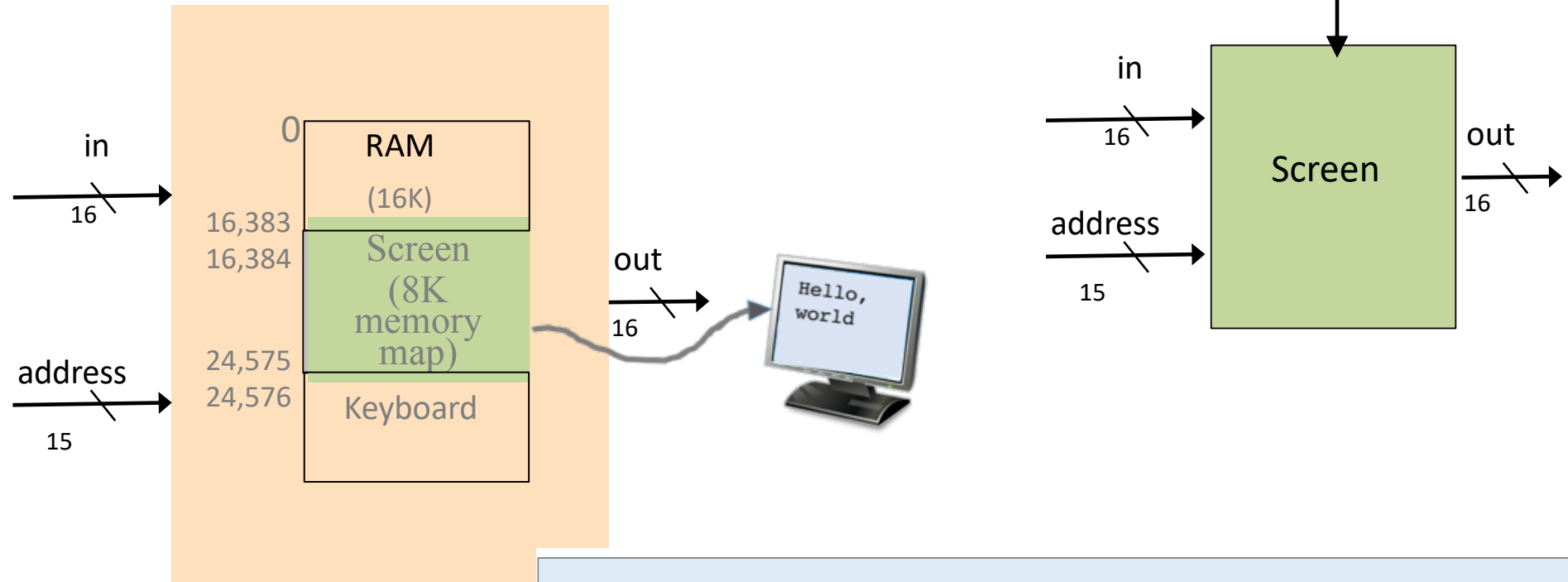


```
CHIP Screen {  
    IN in[16],    // what to write  
    load,        // write-enable bit  
    address[13]; // where to read/write  
    OUT out[16]; // Screen value at the given address  
    BUILTIN Screen;  
    CLOCKED in, load;  
}
```



Keyboard Built-in Chip


Memory

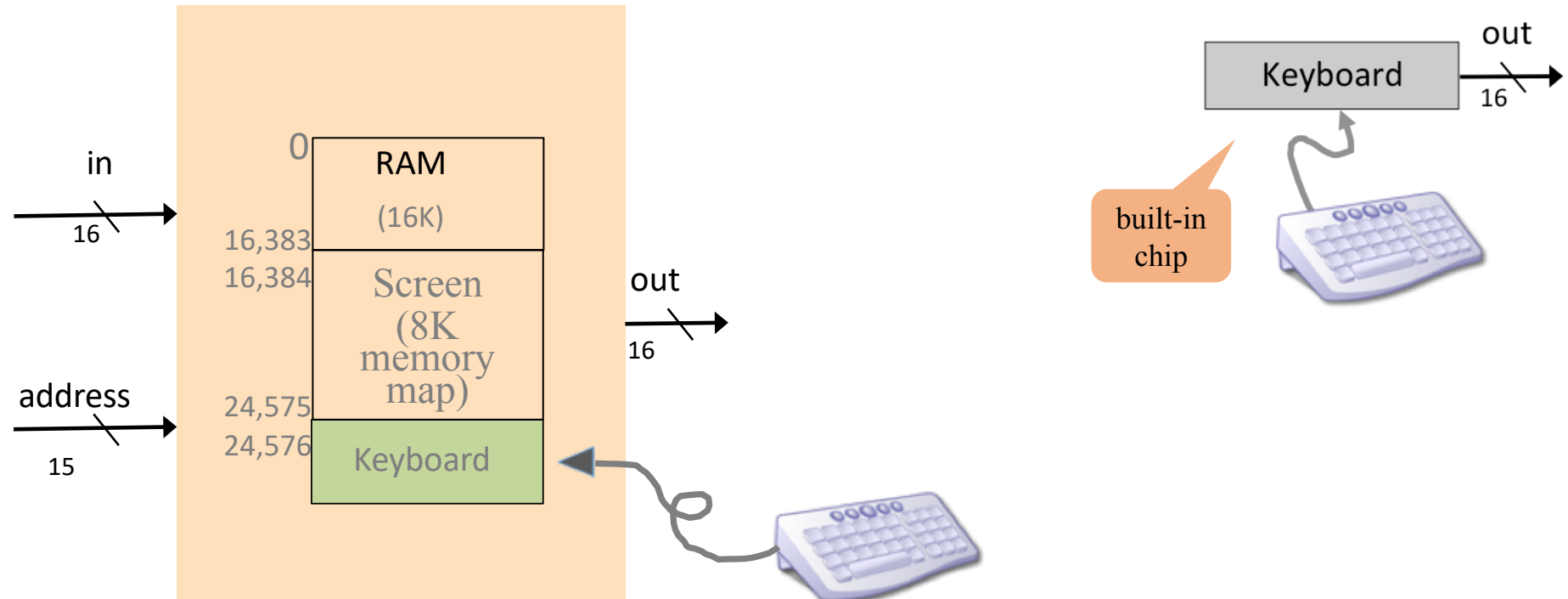

```
CHIP Keyboard {  
  
    OUT out[16]; // The ASCII code of the pressed key,  
                // or 0 if no key is currently pressed,  
                // or one the special codes  
    BUILTIN Keyboard;  
}
```



Memory Chip Implementation

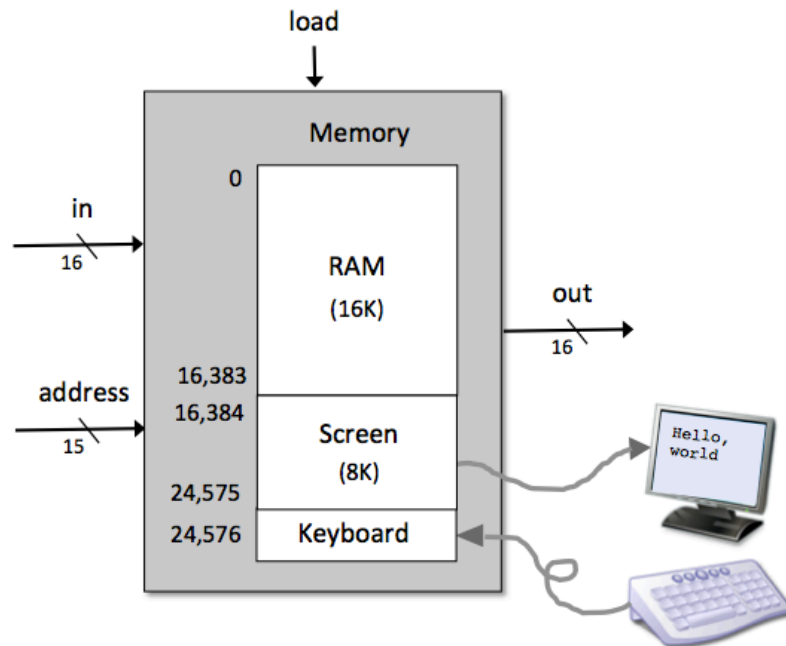


Memory.hdl

```
CHIP Memory {
  IN in[16], load, address[15];
  OUT out[16];
  PARTS:
    DMux(in=load, sel=address[14], a=loadRam, b=loadScreen);
    RAM16K(in=in, address=address[0..13], load=loadRam, out=outRam);
    Screen(in=in, address=address[0..12], load=loadScreen, out=outScreen);
    Keyboard(out=outKeyboard);
    Mux4Way16(a=outRam, b=outRam, c=outScreen, d=outKeyboard, sel=address[13..14],
out=out);
}
```



The Hack Computer

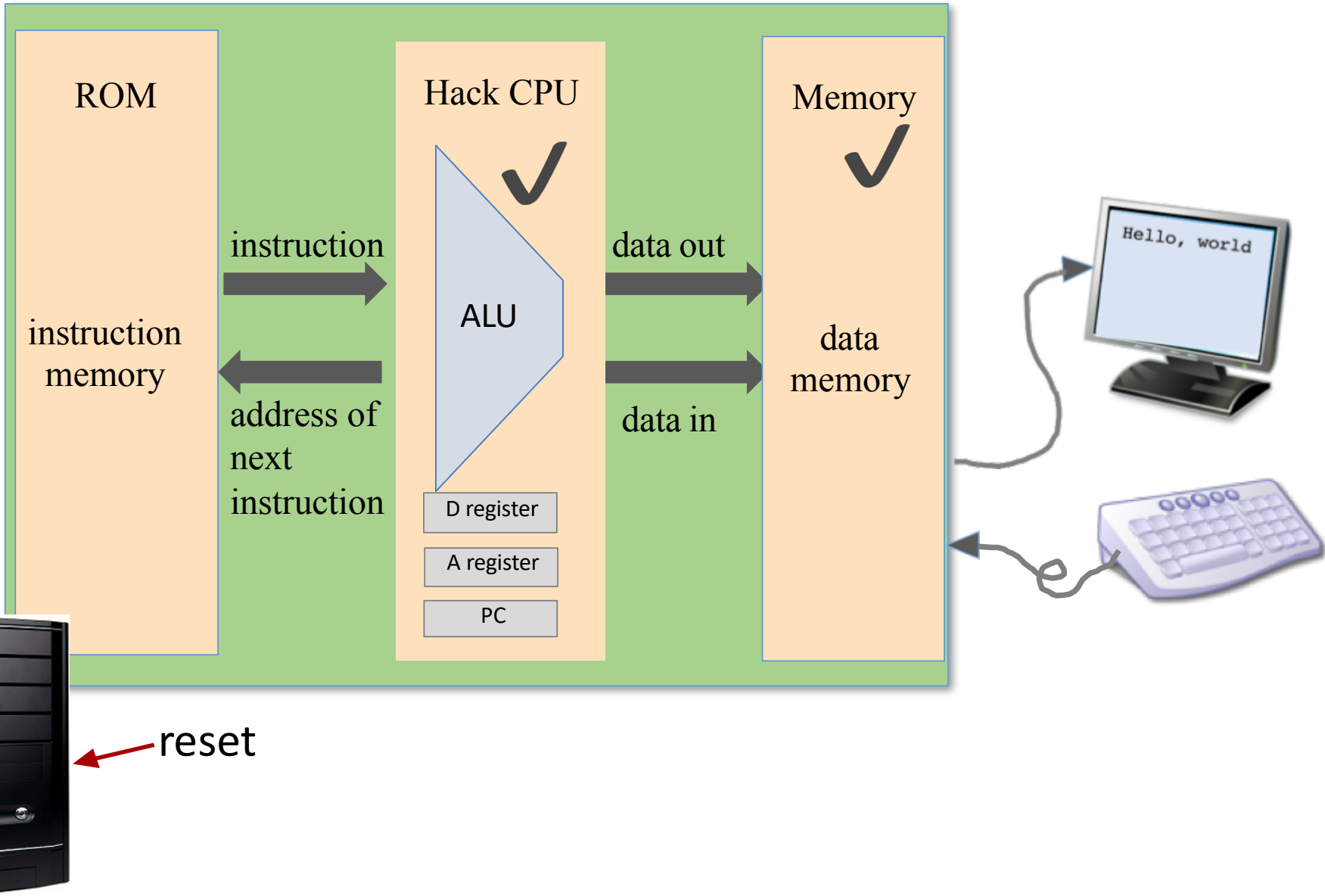





Implementation of Hack Instruction Memory Chip



Instruction Memory

Hack Program
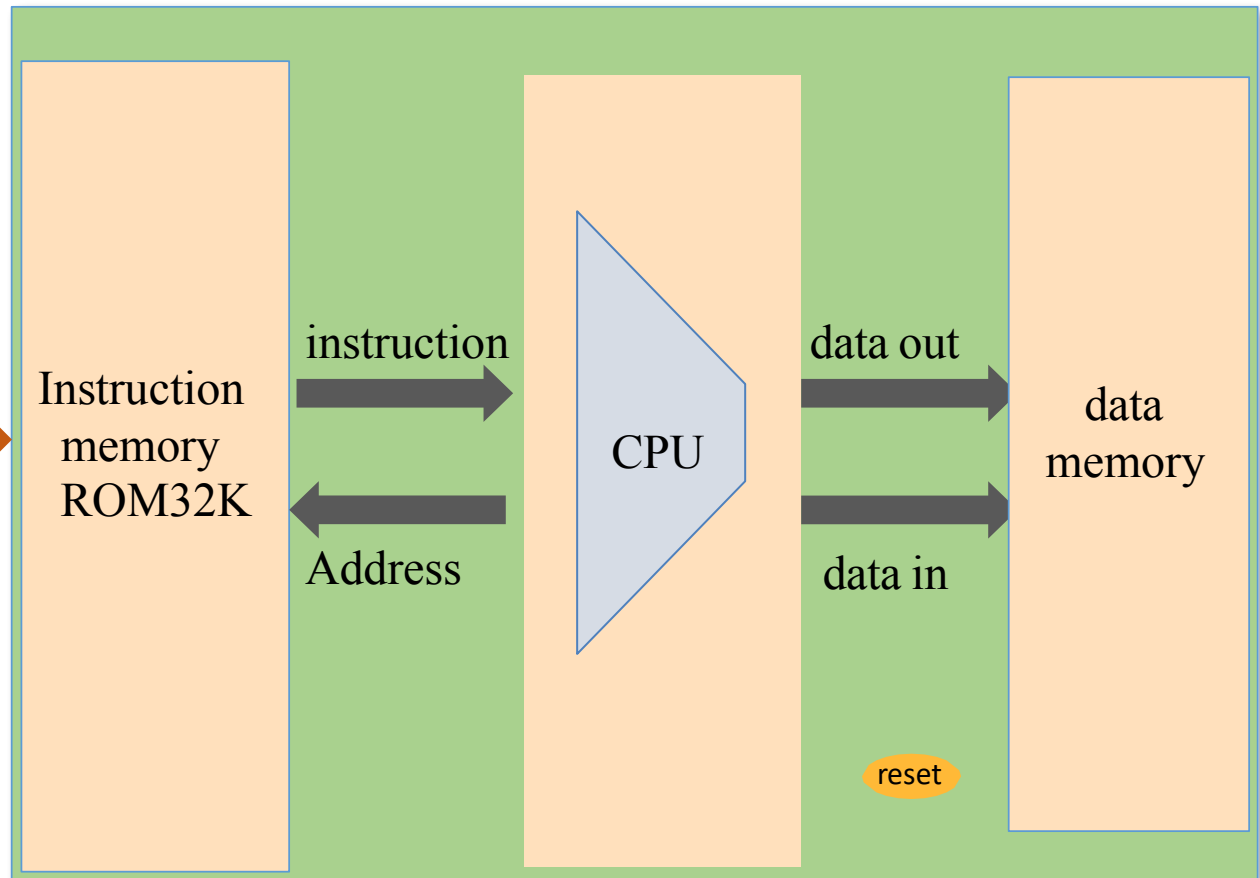 
```
00000000000001101
1110101001010101
0000000000000001
1110101001101011
0000001100110101
1110010111011111
*
*
*
1111001001100111
```



To run a program on the Hack computer:

- Load the program into the Instruction Memory
- Press “reset”
- The program starts running





How do you load a program into the Instruction Memory?



Loading a Program in Instruction Memory

Hack Program
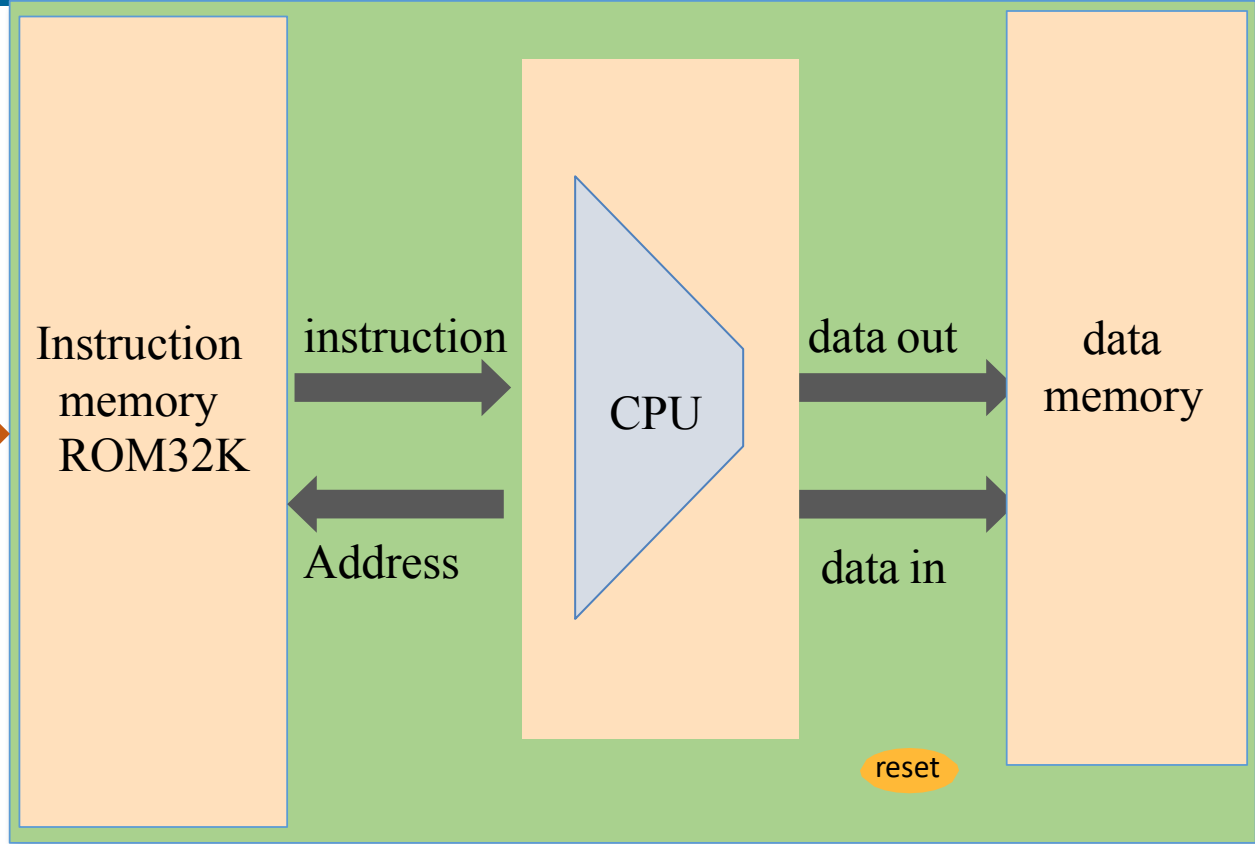 
```
00000000000001101
1110101001010101
0000000000000001
1110101001101011
0000001100110101
1110010111011111
*
*
*
1111001001100111
```




- **Hardware Implementation:** We use a specialized hardware normally called the programmers, which burn/write the hack machine code into a EEPROM chip. We then plug that EEPROM into our computer. Press the reset button and our program starts running. To run another program repeat process (game cartridges for game consoles)
- **Hardware Simulation:** Programs are stored in text files; Program loading is emulated by the built-in ROM chip. The simulator's software features a load-program service



ROM32K Built-in Chip

ROM32K.hdl
 
```
CHIP ROM32K {  
    IN address[15];  
    OUT out[16];  
    BUILTIN ROM32K;  
}
```




- The Hack instruction memory is implemented as a built-in ROM32K chip, which is actually a read-only, 16-bit, 32K RAM chip with program loading side-effect. The chip always outputs the value stored at the memory location specified by address (next instruction to be executed)
- The built-in chip implementation (written in Java) has a GUI side-effect, showing an array-like component that displays the ROM's contents
- The ROM32K chip is supposed to be pre-loaded with a machine language program. However, once the built-in chip implementation is loaded inside the hardware simulator, it allows the user to load Hack machine program from a text file (We will soon see a demo)



Implementation of Hack Computer Chip




Hack Computer Abstraction

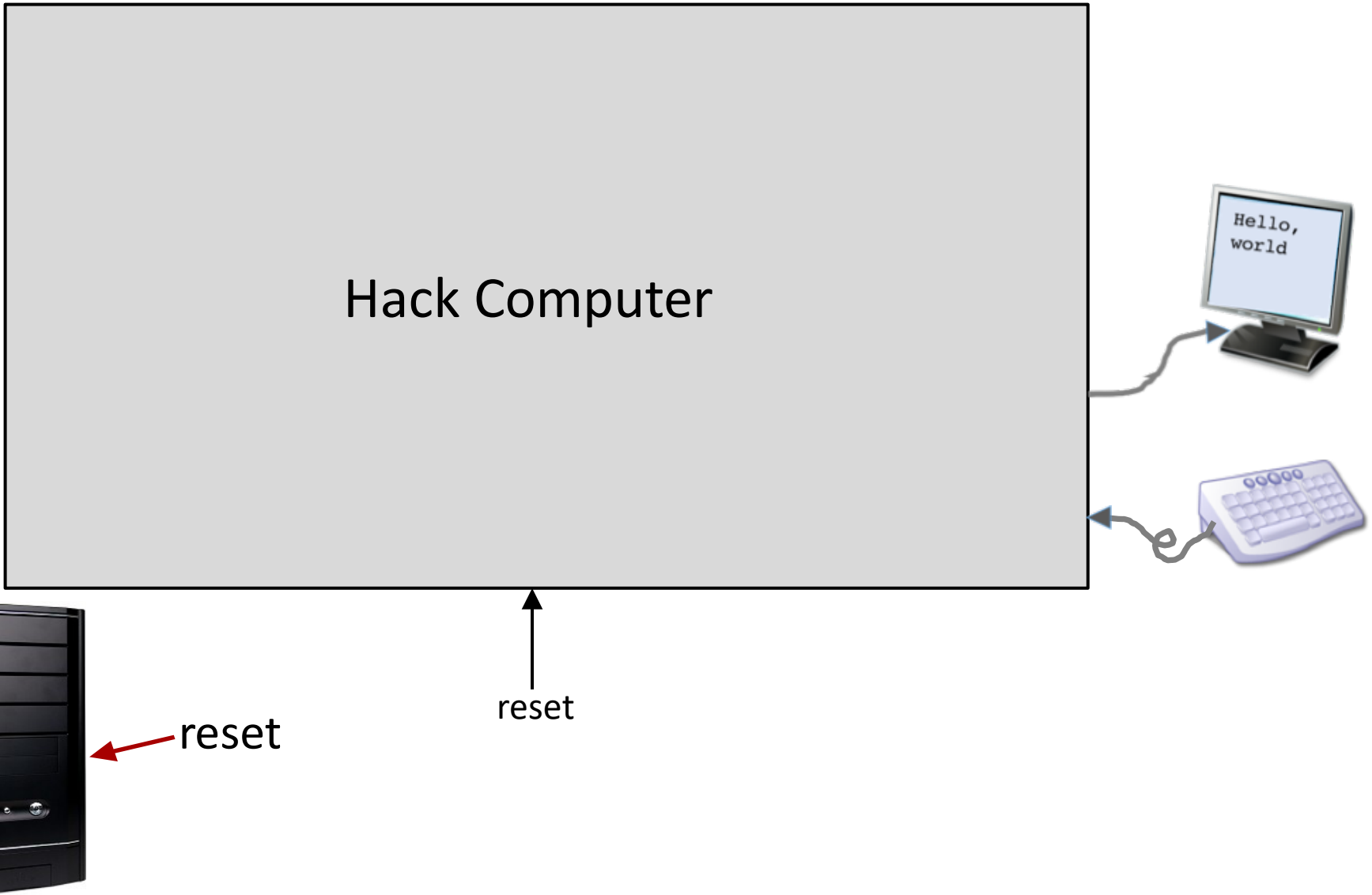



Hack Computer Implementation

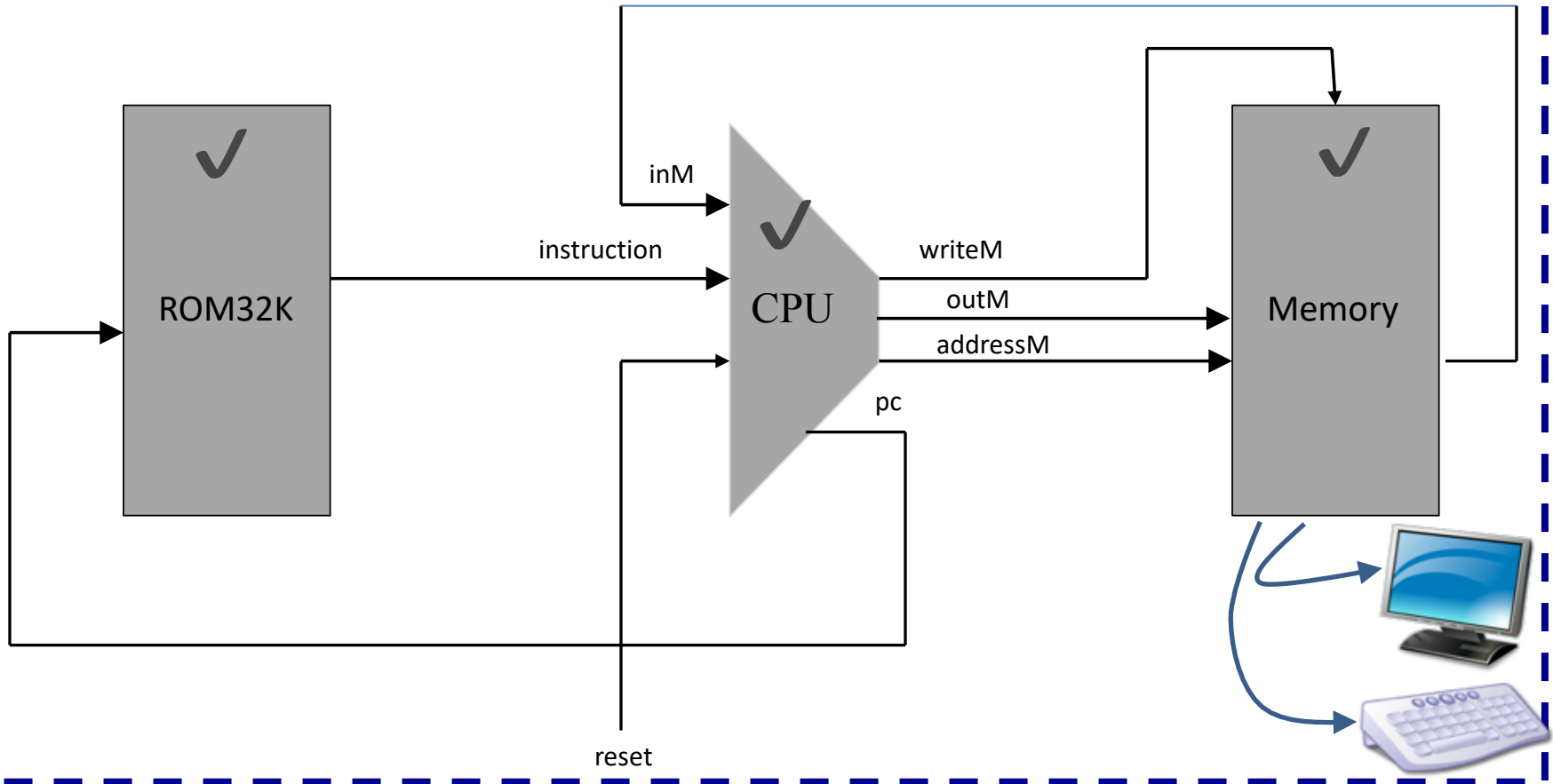




Hack Computer Chip

Computer.hdl

```
/**
 * The HACK computer, including CPU, ROM and RAM.
 * When reset is 0, the program stored in the computer's ROM executes.
 * When reset is 1, the execution of the program restarts.
 * Thus, to start a program's execution, reset must be pushed "up" (1)
 * and "down" (0). From this point onward the user is at the mercy of
 * the software. In particular, depending on the program's code, the
 * screen may show some output and the user may be able to interact
 * with the computer via the keyboard.
 */
```
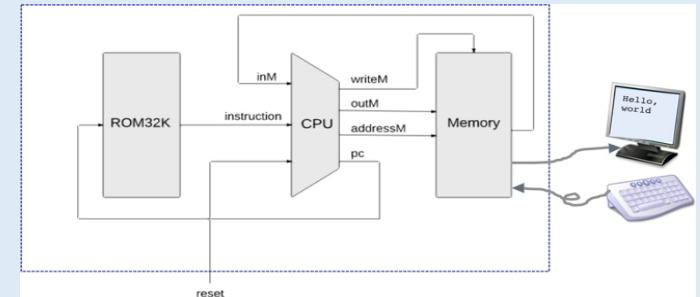
```
CHIP Computer {
  IN reset;
  PARTS:
    ROM32K(address=pc, out=instruction);
    CPU(inM=memoryOut, instruction=instruction, reset=reset, outM=outM,
writeM=writeM, addressM=addressM, pc=pc);
    Memory(in=outM, load=writeM, address=addressM, out=memoryOut);
}
```



Simplicity at its peak 😊



Running Assembly Programs in Hack Computer





Things To Do

