

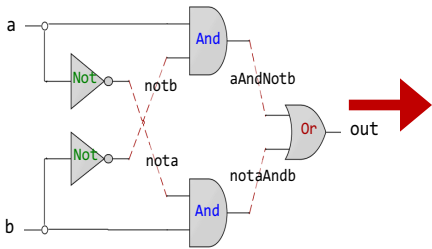


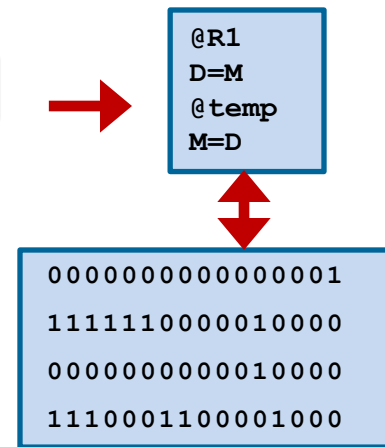

Digital Logic Design

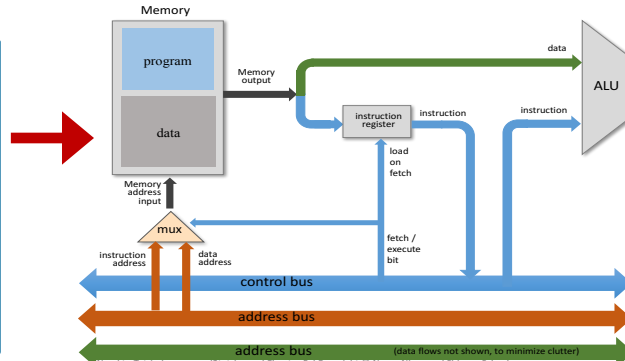

```
CHIP Xor {
  IN a, b;
  OUT out;
  PARTS:
    Not(in=a, out=nota);
    Not(in=b, out=notb);
    And(a=nota, b=b, out=w1);
    And(a=a, b=notb, out=w2);
    Or(a=w1, b=w2, out=out);
}
```



Lecture # 09-10

HDL for Arithmetic Circuits


```
#include<stdio.h>
#include<stdlib.h>
int main(){
  printf("Learning is fun with Arif\n");
  exit(0);
}
```

```
global main
SECTION .data
  msg: db "Learning is fun with Arif", 0Ah, 0h
  len_msg: equ $ - msg
SECTION .text
main:
  mov rax,1
  mov rdi,1
  mov rsi,msg
  mov rdx,len_msg
  syscall
  mov rax,60
  mov rdi,0
  syscall
```

0:	b8 01 00 00 00
5:	bf 01 00 00 00
a:	48 be 00 00 00 00 00
11:	00 00 00
14:	ba 1b 00 00 00
19:	0f 05
1b:	b8 3c 00 00 00
20:	bf 00 00 00 00
25:	0f 05

Slides of first half of the course are adapted from:
<https://www.nand2tetriz.org>
 Download s/w tools required for first half of the course from the following link:
<https://drive.google.com/file/d/0B9c0BdDz6XpZUh3X2dPR1o0MUE/view>

Instructor: Muhammad Arif Butt, Ph.D.

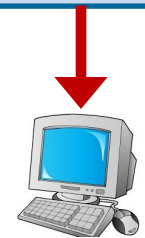



Today's Agenda


- Designing Combinational Circuits
- Writing HDL for Combinational Arithmetic Circuits like
 - Half Adder
 - Full Adder
 - Full Subtractor
 - 16 bit Binary Adder (Add16 chip)
 - 16 bit Incrementor (Inc16 chip)
 - BCD Adder
 - Half Subtractor
 - Full Subtractor
 - Binary Subtractor
 - Binary Adder/Subtractor
- Demo of above chips on H/W Simulator





Combinational Circuits

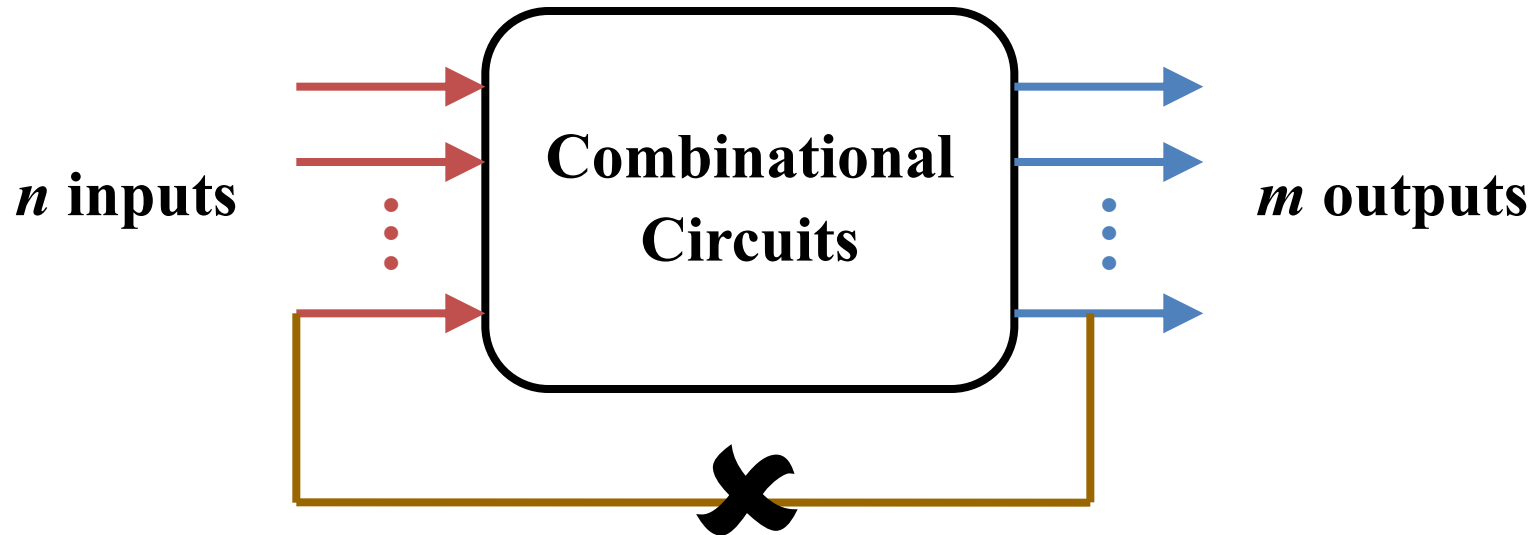- Output is function of input only
i.e. no feedback



When **input** changes, **output** may change (after a delay)



Designing Combinational Circuits

Design a majority circuit, which is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise



Designing Combinational Circuits

Design a circuit that converts each of its BCD inputs to corresponding Excess-3 Code







Designing Combinational Circuits

BCD-to-Excess 3 Converter


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

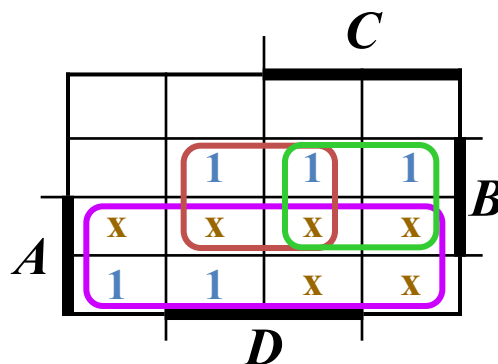


$$w = A + BC + BD$$

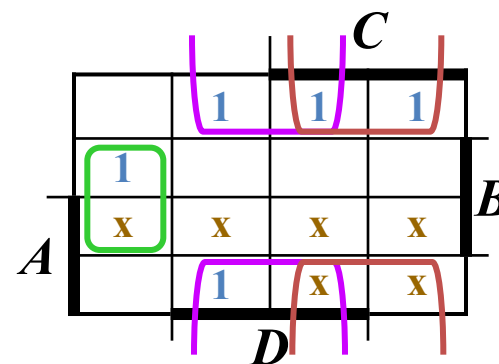

$$x = B'C + B'D + BC'D'$$

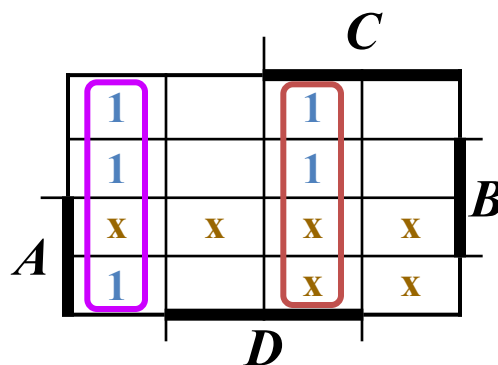

$$y = C'D' + CD$$

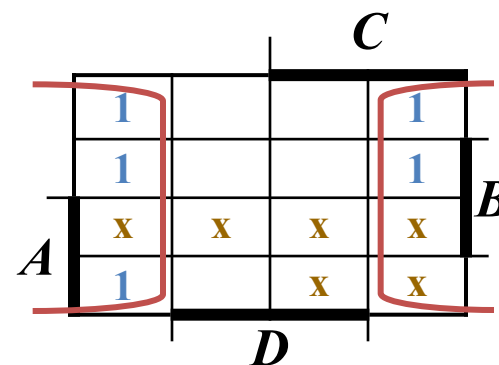


$$z = D'$$



Designing Combinational Circuits

- BCD-to-Excess 3 Converter

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

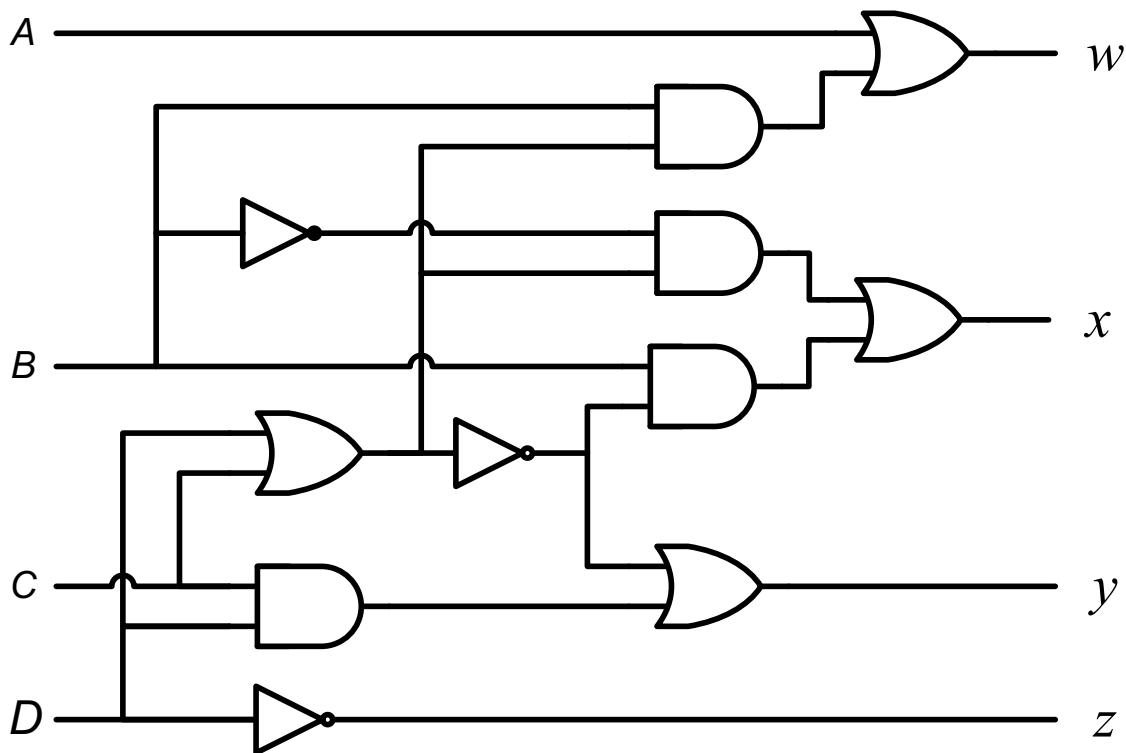

$$w = A + B(C+D)$$

$$y = (C+D)' + CD$$

$$x = B'(C+D) + B(C+D)'$$

$$z = D'$$



Designing Combinational Circuits

A circuit that converts each of its 3-bit binary number to its corresponding 2's complement



Arithmetic Logic Unit

- To design a proper Arithmetic Logic Unit, we first need to design some combinational chips that can perform some basic arithmetic operations. Later we can integrate those chips to build the complete ALU
- Let us now design and code some chips that perform some basic arithmetic operations using the already created chips so far

- HalfAdder
- FullAdder
- Add16
- Inc16
- ALU

A family of combinational chips, from simple adders to an Arithmetic Logic Unit.



Boolean Arithmetic

• Addition

implement

• Subtraction

get for free

• Comparison (<, >, =)

get for free

• Multiplication

postpone to software

• Division


postpone to software

- Half adder: adds two bits
- Full adder: adds three bits
- Binary Adder: adds two integers
- Incrementer: adds one to an integer



Half Adder

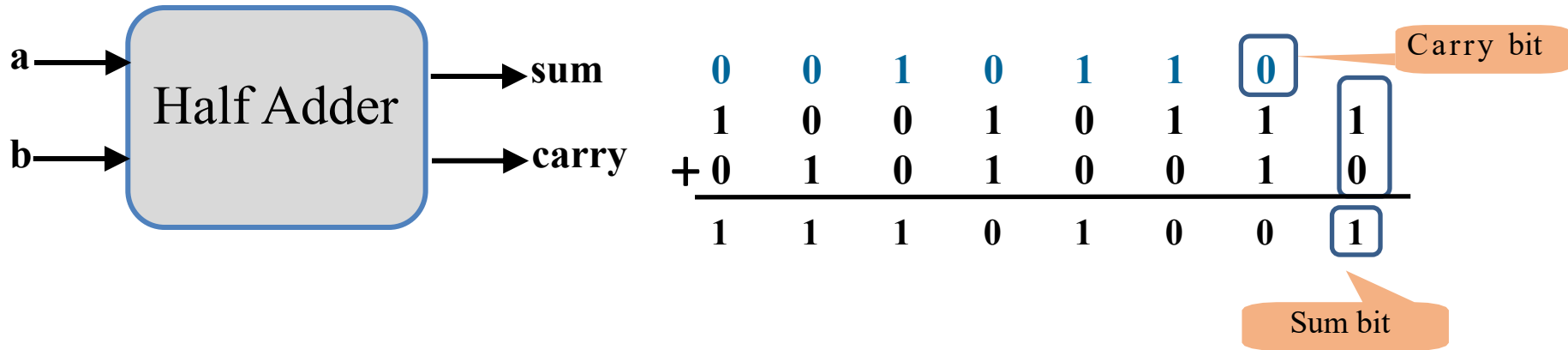
- A half adder is a combinational circuit that accepts two input bits and generates two outputs (a sum bit and a carry bit)



a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$sum(a,b) = a'b + ab' = a \oplus b$$

$$carry(a,b) = ab$$

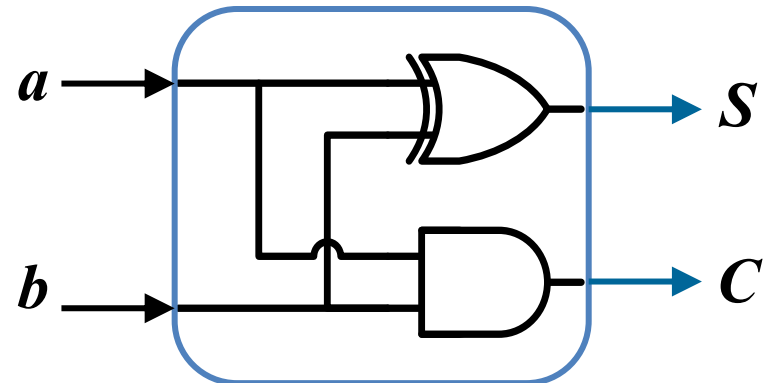




Half Adder Implementation

HalfAdder.hdl
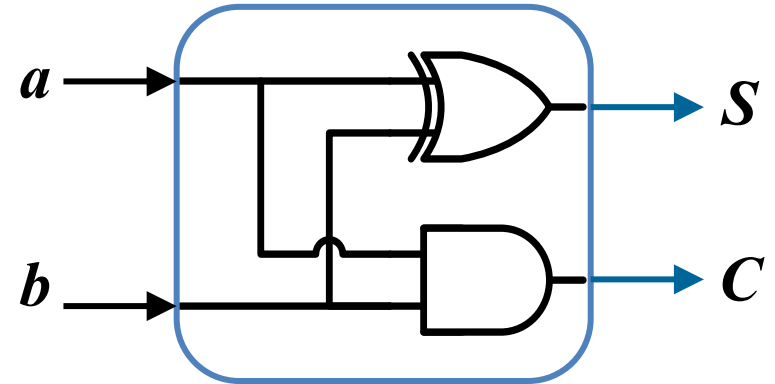
```
/**
 * Computes the sum of two bits.
 */
CHIP HalfAdder {
    IN a, b;    // 1-bit inputs
    OUT sum,    // Right bit of a + b
        carry; // Left bit of a + b
    PARTS:
        XOR(a=a, b=b, out=sum);
        AND(a=a, b=b, out=carry);
}
```






Half Adder Demo





Full Adder

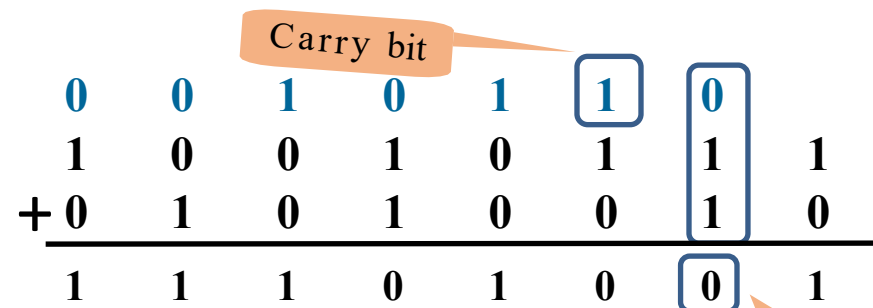- A half adder can add only two bits, it cannot accommodate the carry from the previous two bits addition. A full adder is a combinational circuit that performs the arithmetic sum of three input bits (augend, addend and carry-in) and generates two outputs a sum and a carry-out





$$\begin{aligned}
 \text{sum}(a,b,c) &= a'b'c + a'bc' + ab'c' + abc \\
 &= a \oplus b \oplus c
 \end{aligned}$$

$$\text{carry}(a,b,c) = ab + bc + ac$$

a	b	c	sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1




Full Adder Implementation

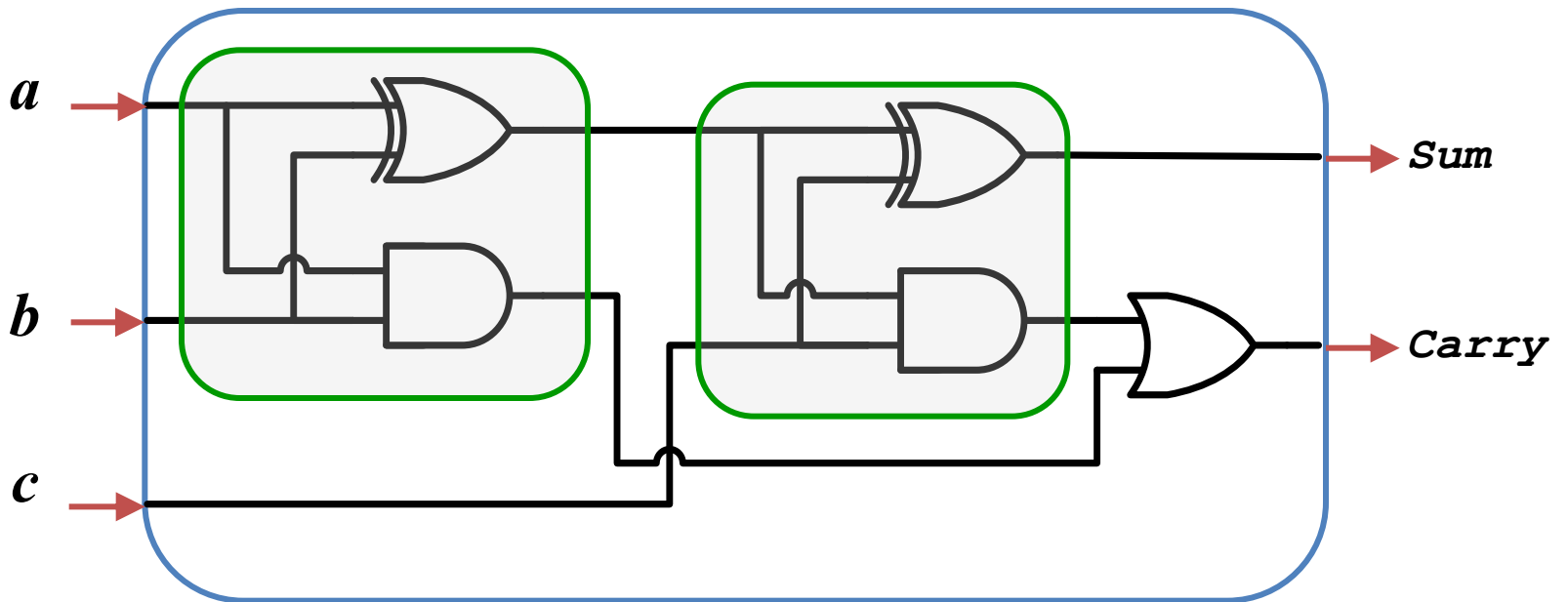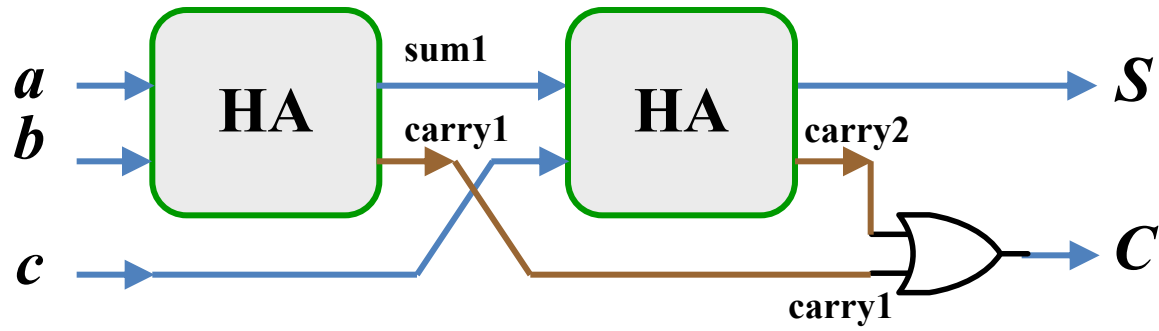



Full Adder Implementation (cont...)

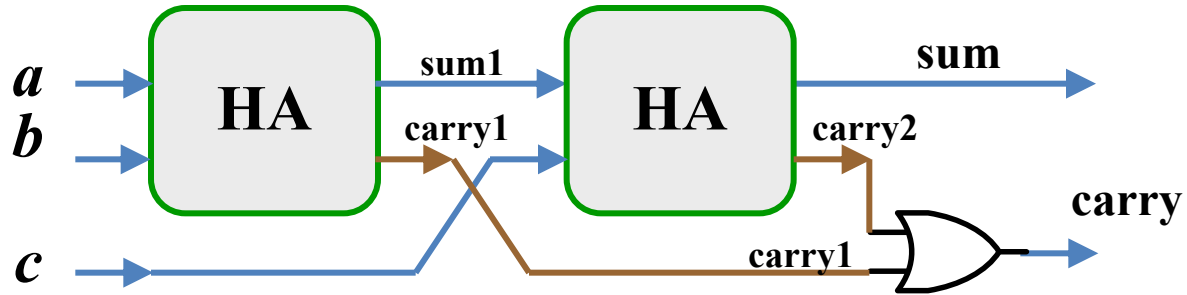

FullAdder.hdl

```
// Computes the sum of three bits
CHIP FullAdder {
    IN a, b, c; // 1-bit inputs
    OUT sum, carry;
    PARTS:
        HalfAdder(a=a, b=b, sum=sum1, carry=carry1);
        HalfAdder(a=sum1, b=c, sum=sum, carry=carry2);
        Or(a=carry1, b=carry2, out=carry);
}
```




Full Adder Demo






Binary Adder


- A digital circuit that produces the sum of two n bit binary numbers is called a n-bit binary adder. It can be designed with full adders connected in cascade. A 4-bit binary adder is shown below:

0	0	1	0	1	1	0	1	
1	0	0	1	0	1	1	1	
0	1	0	1	0	0	1	0	
					+			
1	1	1	0	1	0	0	1	

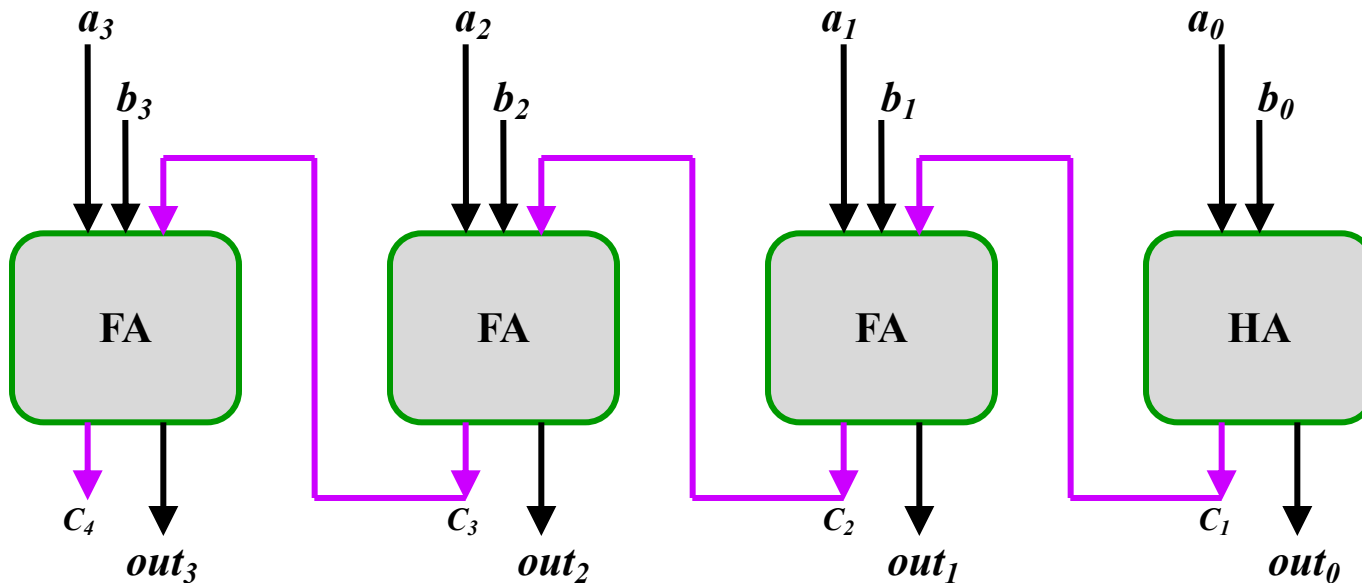



Binary Adder Implementation

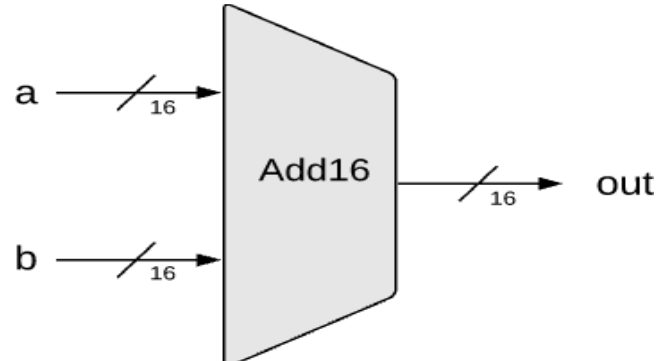

Add16.hdl

```
CHIP Add16 {
  IN a[16], b[16];
  OUT out[16];
  PARTS:
    HalfAdder(a=a[0], b=b[0], sum=out[0], carry=carry0);
    FullAdder(a=a[1], b=b[1], c=carry0, sum=out[1], carry=carry1);
    FullAdder(a=a[2], b=b[2], c=carry1, sum=out[2], carry=carry2);
    FullAdder(a=a[3], b=b[3], c=carry2, sum=out[3], carry=carry3);
    .....
    FullAdder(a=a[14], b=b[14], c=carry13, sum=out[14], carry=carry14);
    FullAdder(a=a[15], b=b[15], c=carry14, sum=out[15], carry=carry15);
}
```




Binary Adder Demo





16 Bit Incrementer Implementation

- A digital circuit that inputs a 16 bit integer and adds 1 to it, ignores the carryout from the MSb (if any)
- The single-bit 0 and 1 values are represented in HDL as false and true


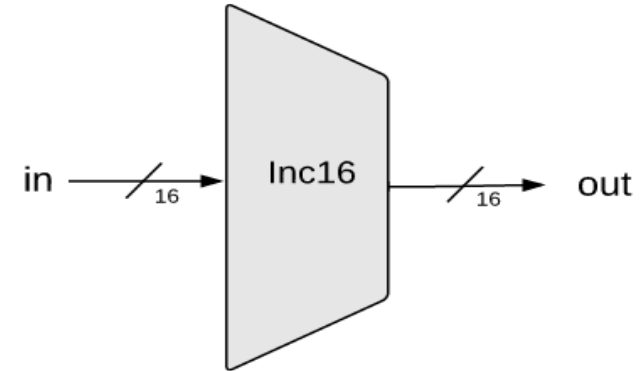


Inc16.hdl

```
/**
 * 16-bit incrementer:
 * out = in + 1 (arithmetic addition)
 */
CHIP Inc16 {
    IN in[16];
    OUT out[16];
    PARTS:
        Add16(a=in, b[0]=true, out=out);
}
```




Half Subtractor Circuit

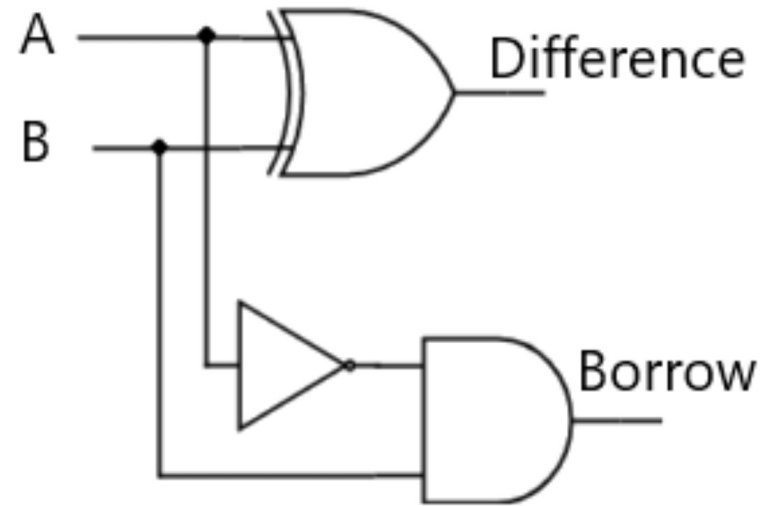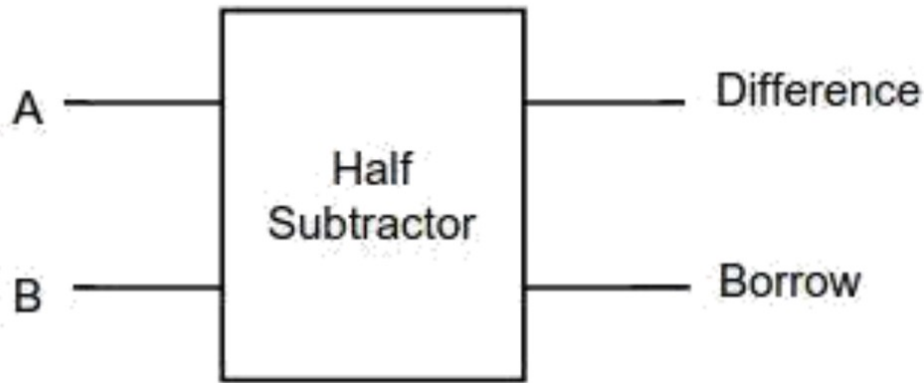



Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Difference} = A \oplus B$$

$$\text{Borrow} = A' B$$



Full Subtractor Circuit

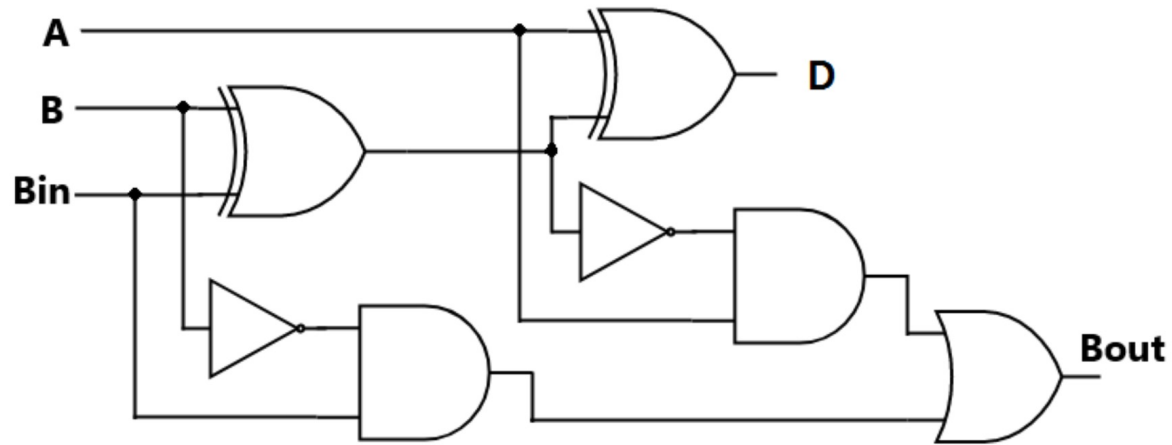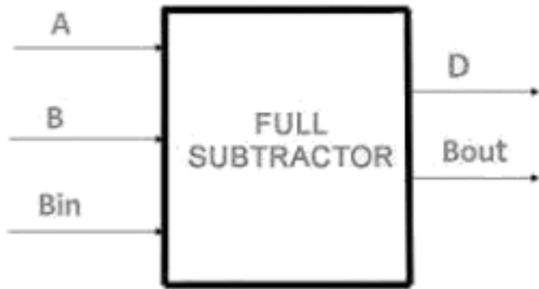


A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = A \oplus B \oplus B_{in}$$
$$B_{out} = A' B_{in} + A' B + B B_{in}$$



4-Bits Binary Subtractor Circuit

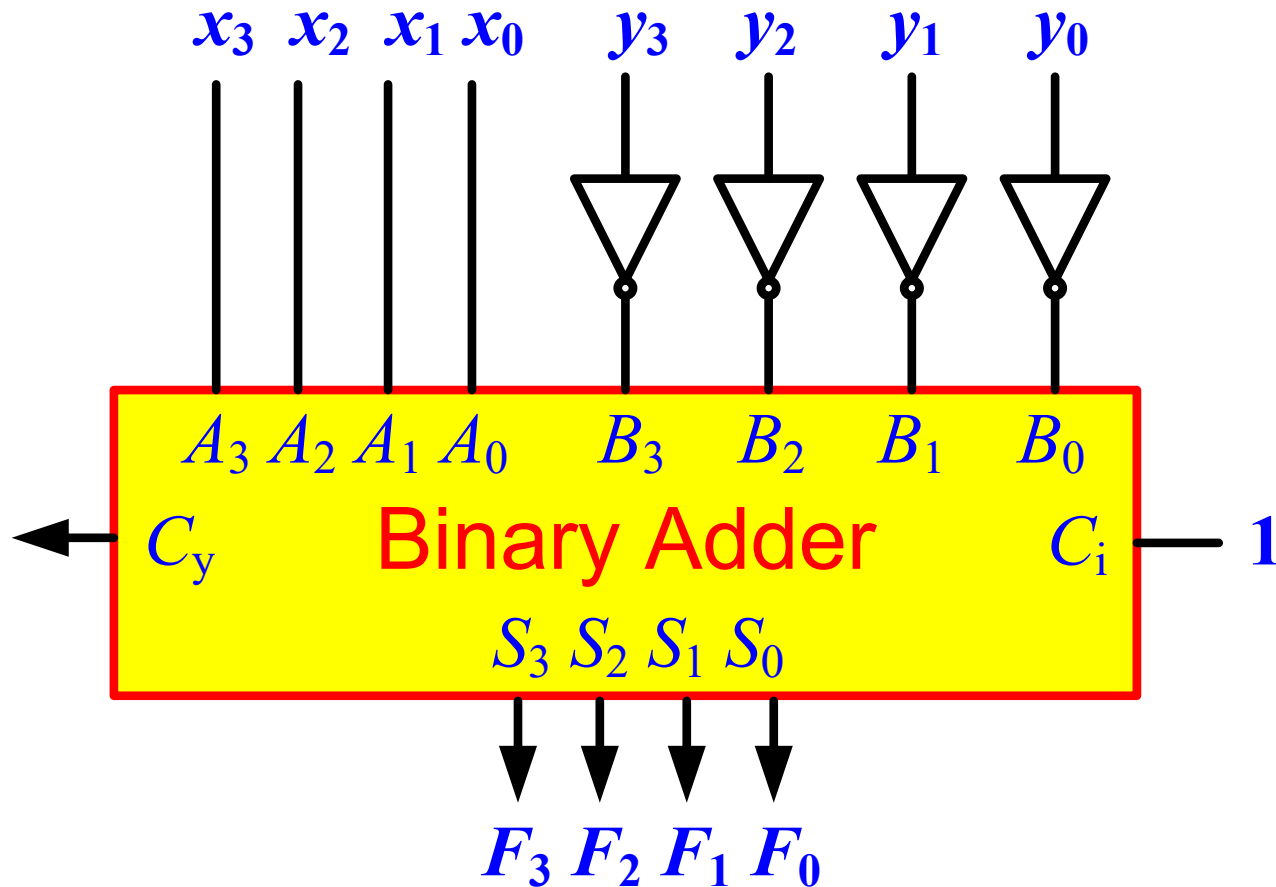




Binary Adder/Subtractor Circuit

- M : Control Signal (Mode)


– $M=0 \rightarrow F = x + y$

– $M=1 \rightarrow F = x - y$

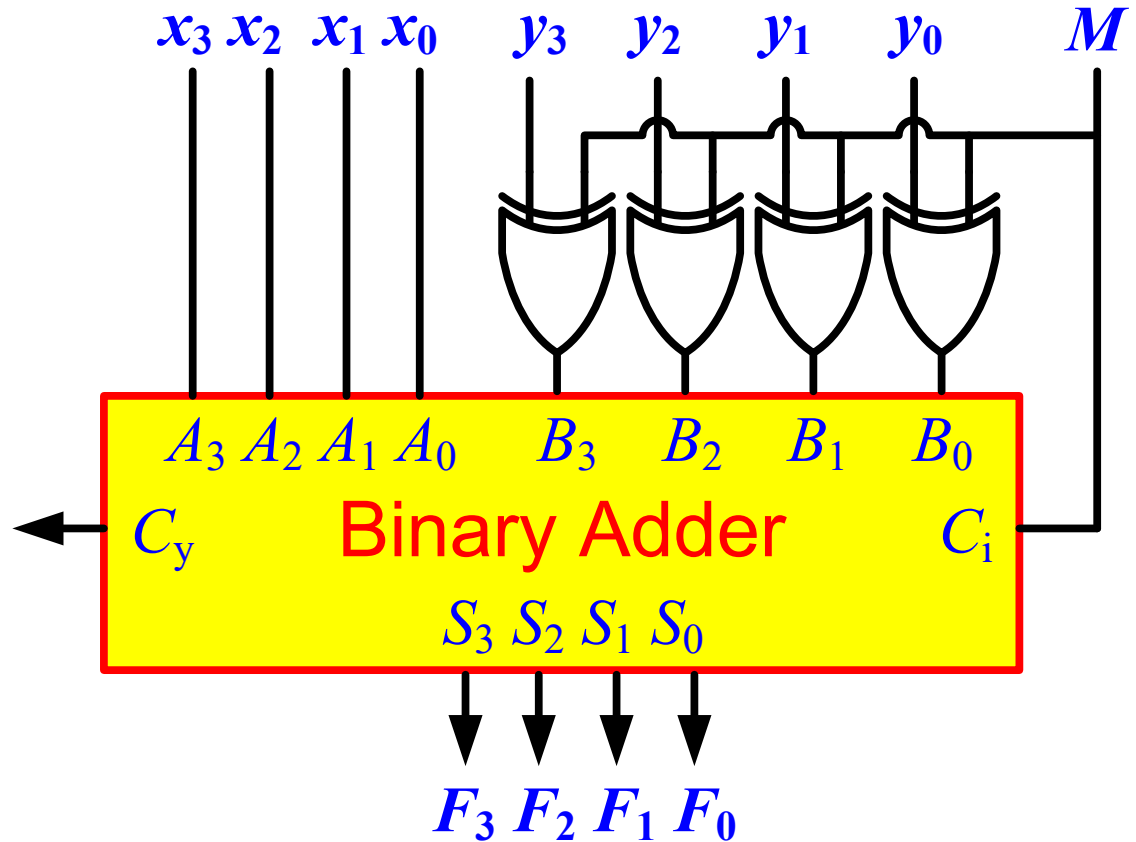


Integer Over Flow Circuit

- Addition of Unsigned Numbers

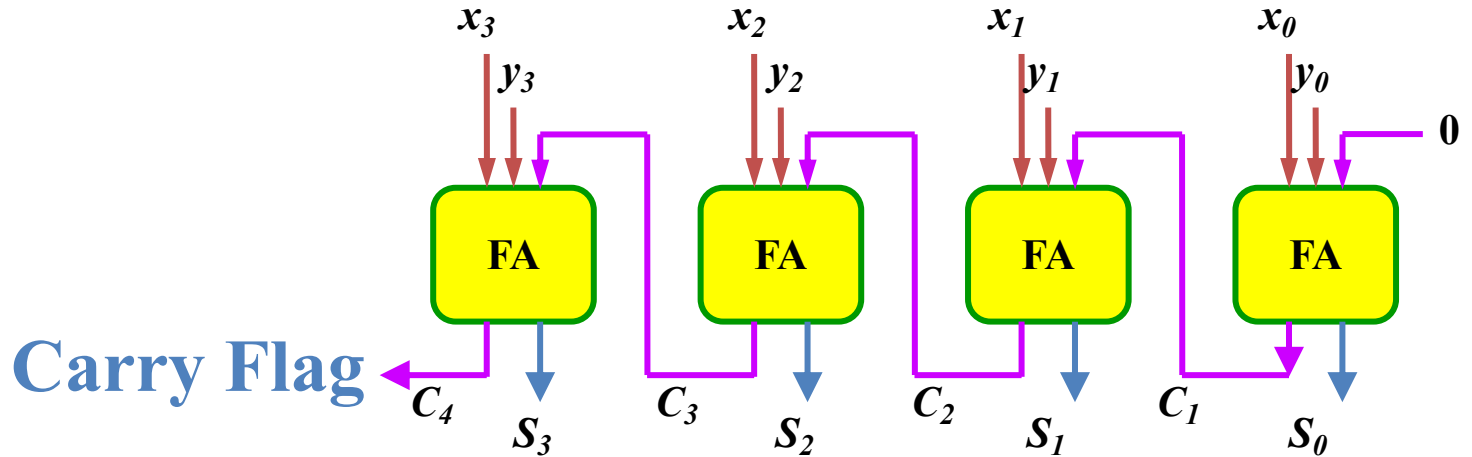

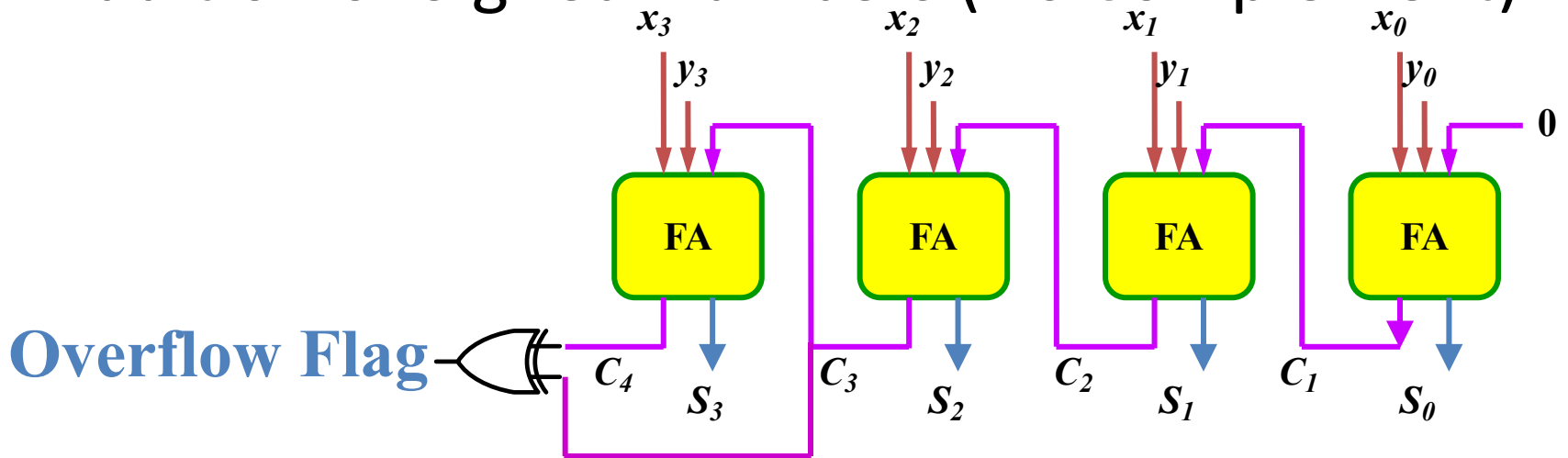- Addition of Signed Numbers (2's Complement)





Things To Do

- Perform interactive and script based testing of the chips designed in today's session on the h/w simulator. You can download the .hdl, .tst and .cmp files of above chips from the course bitbucket repository:

https://github.com/arifpucit/COAL_VLecs



- Interested students should try to design half subtractor, full subtractor and adder-subtractor chips. Also design a 16-bit binary subtractor chip that can subtract one 16 bit number from another 16 bit number

Coming to office hours does NOT mean you are academically week!