
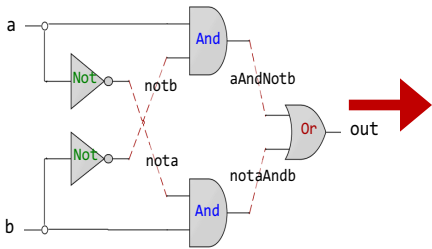


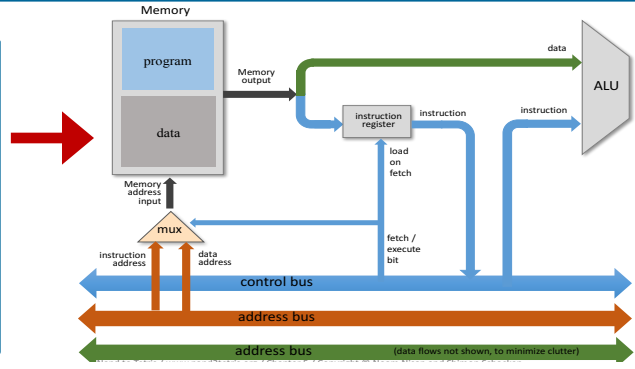

Digital Logic Design



```
CHIP Xor {
  IN a, b;
  OUT out;
  PARTS:
  Not(in=a, out=nota);
  Not(in=b, out=notb);
  And(a=nota, b=b, out=w1);
  And(a=a, b=notb, out=w2);
  Or(a=w1, b=w2, out=out);
}
```



@R1
D=M
@temp
M=D

```
0000000000000001
1111110000010000
0000000000010000
1110001100001000
```

Lecture # 26

Data Path of Hack CPU


```
#include<stdio.h>
#include<stdlib.h>
int main(){
  printf("Learning is fun with Arif\n");
  exit(0);
}
```

```
global main
SECTION .data
  msg: db "Learning is fun with Arif", 0Ah, 0h
  len_msg: equ $ - msg
SECTION .text
main:
  mov rax,1
  mov rdi,1
  mov rsi,msg
  mov rdx,len_msg
  syscall
  mov rax,60
  mov rdi,0
  syscall
```

```
0: b8 01 00 00 00
5: bf 01 00 00 00
a: 48 be 00 00 00 00 00
11: 00 00 00
14: ba 1b 00 00 00
19: 0f 05
1b: b8 3c 00 00 00
20: bf 00 00 00 00
25: 0f 05
```

Slides of first half of the course are adapted from:
<https://www.nand2tetris.org>
 Download s/w tools required for first half of the course from the following link:
<https://drive.google.com/file/d/0B9c0BdDz6XpZUh3X2dPR1o0MUE/view>

Instructor: Muhammad Arif Butt, Ph.D.

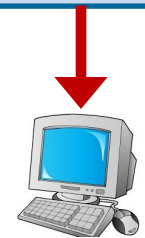



Today's Agenda

- Von Neumann Architecture
- Flow of Information inside Computers
- Buses
 - Data Bus
 - Address Bus
 - Control Bus
- Fetch Execute Cycle
- Fetch Execute Clash
- Harvard Architecture
- Hack CPU Interface
- Hack CPU Implementation
- Input/output and Operations of Hack ALU
- Control Logic of Hack CPU






Von Neumann Architecture



Von Neumann Architecture


The Von Neumann architecture is a computer architecture given by a mathematician and physicist John von Neumann describes the design architecture for an electronic digital computer with these components:

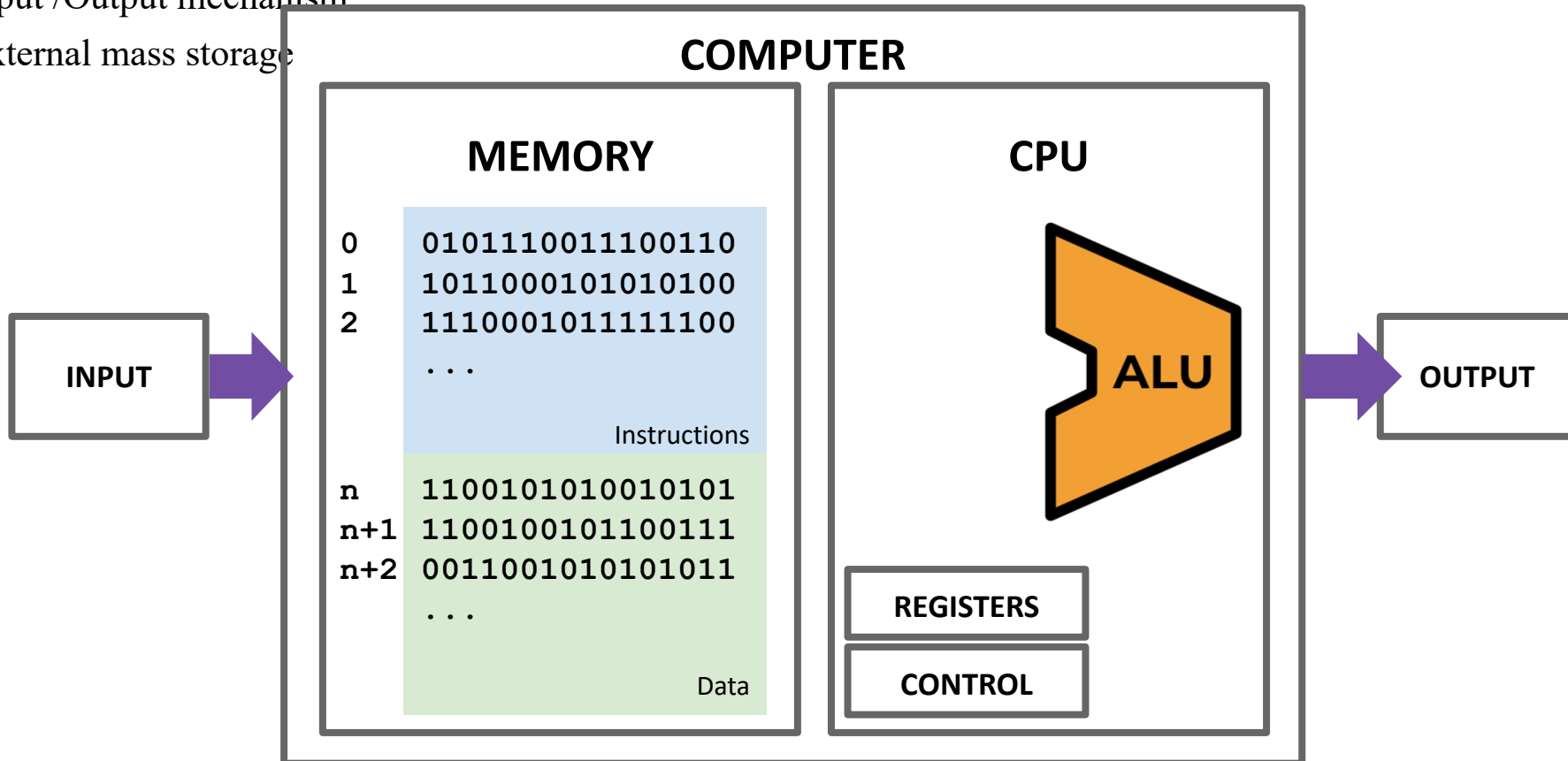- A Processing Unit that contains an ALU and registers
- A Control Unit that contains an instruction register and program counter
- **A Memory unit that stores both data and instructions**
- Input /Output mechanism
- External mass storage





Information Flow / CPU Data Path

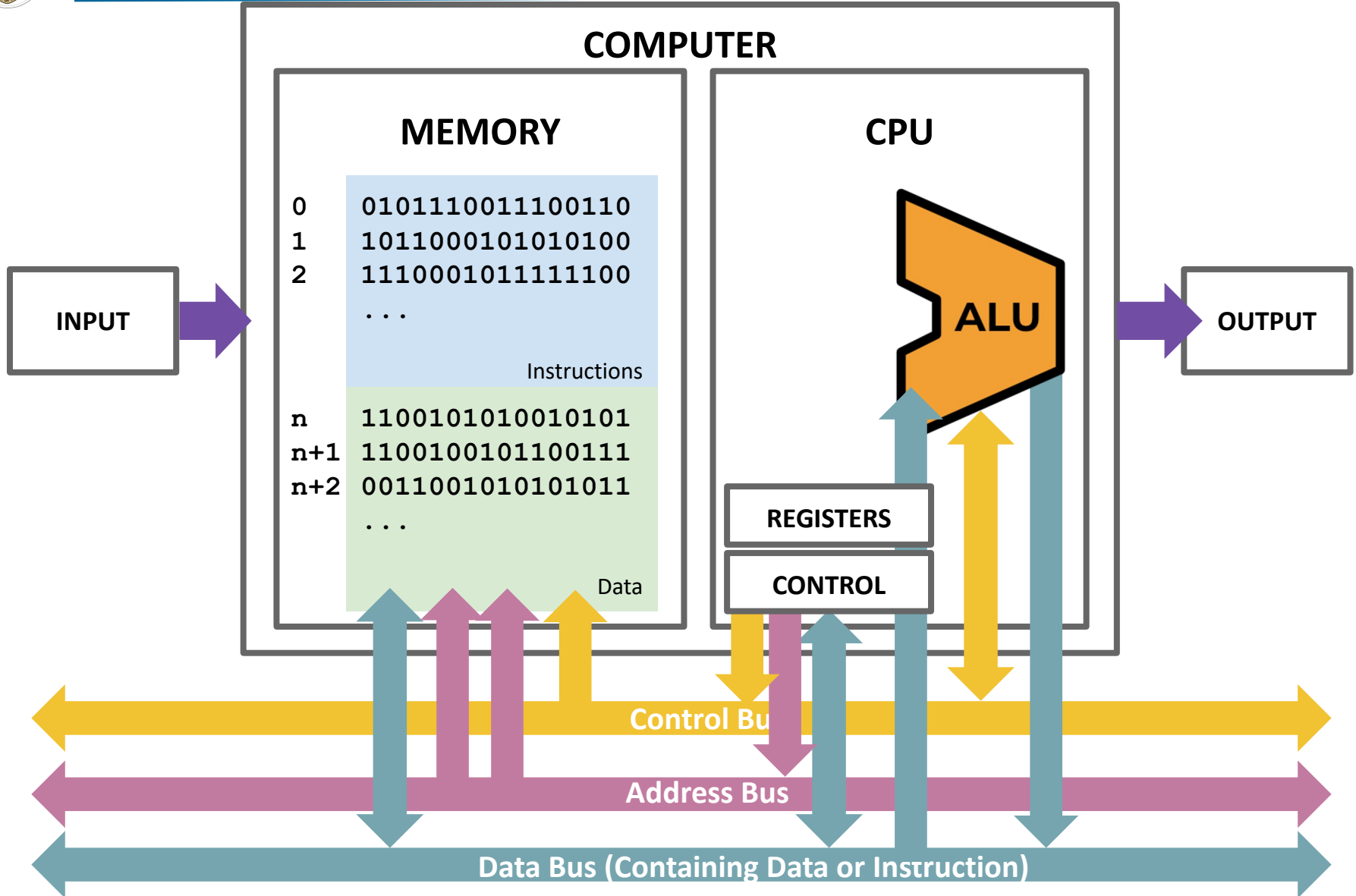



Overview of General Fetch-Execute Cycle



Basic CPU Loop


Repeat:

- **Fetch** an instruction from the program memory
- **Execute** the instruction



Fetching

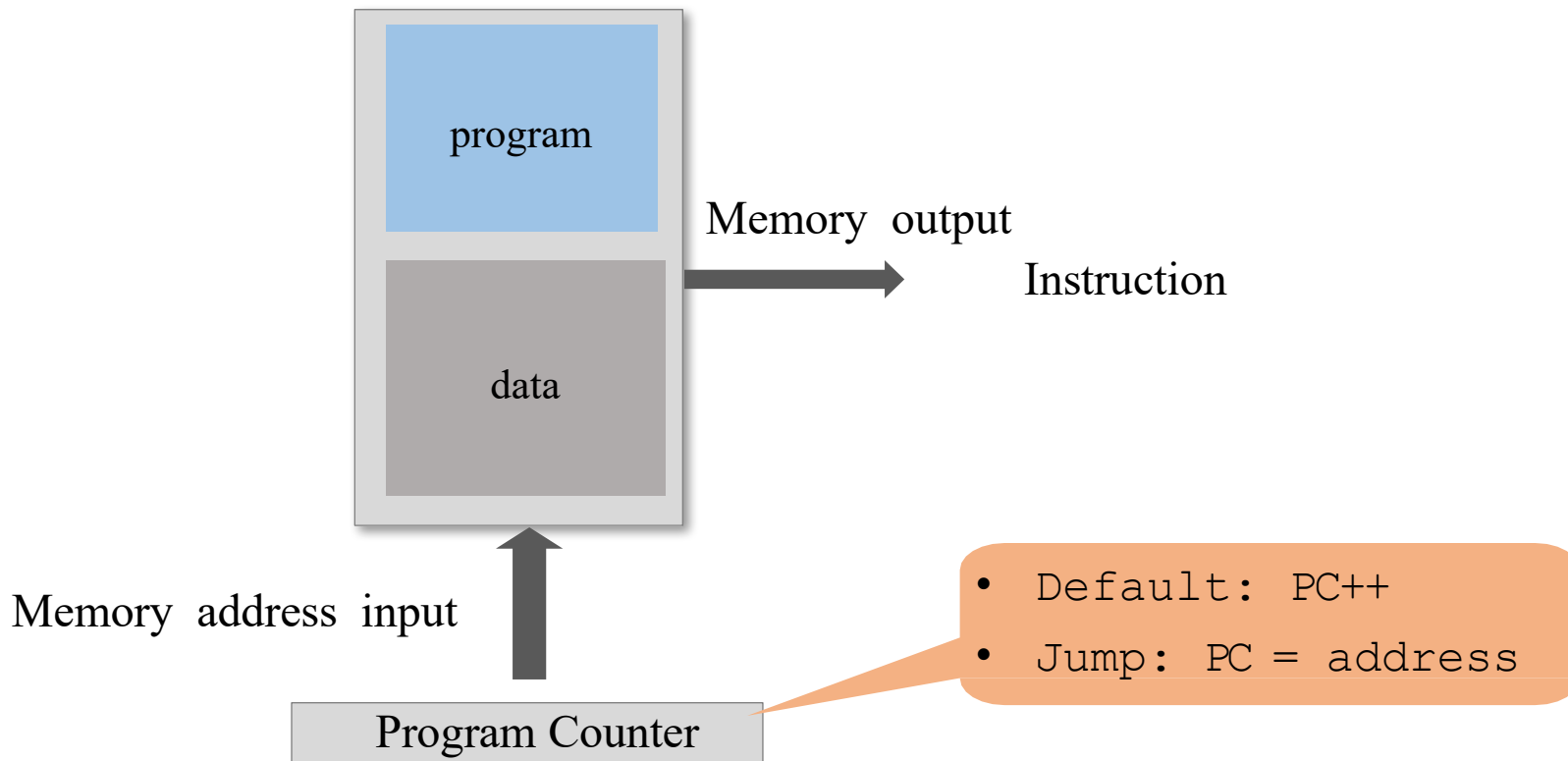- Put the location of the next instruction in the Memory address input
- Read the contents of the memory from that location to get the instruction code





Executing


- The instruction code specifies “what to do”
 - Which arithmetic or logical instruction to execute
 - Which memory address to access (for read / write)
 - If / where to jump
 - ...

Different subset of the instruction bits controls different aspects of the operation

- Executing the instruction involves:
 - accessing registers and / or
 - accessing the data memory




Fetch Execute

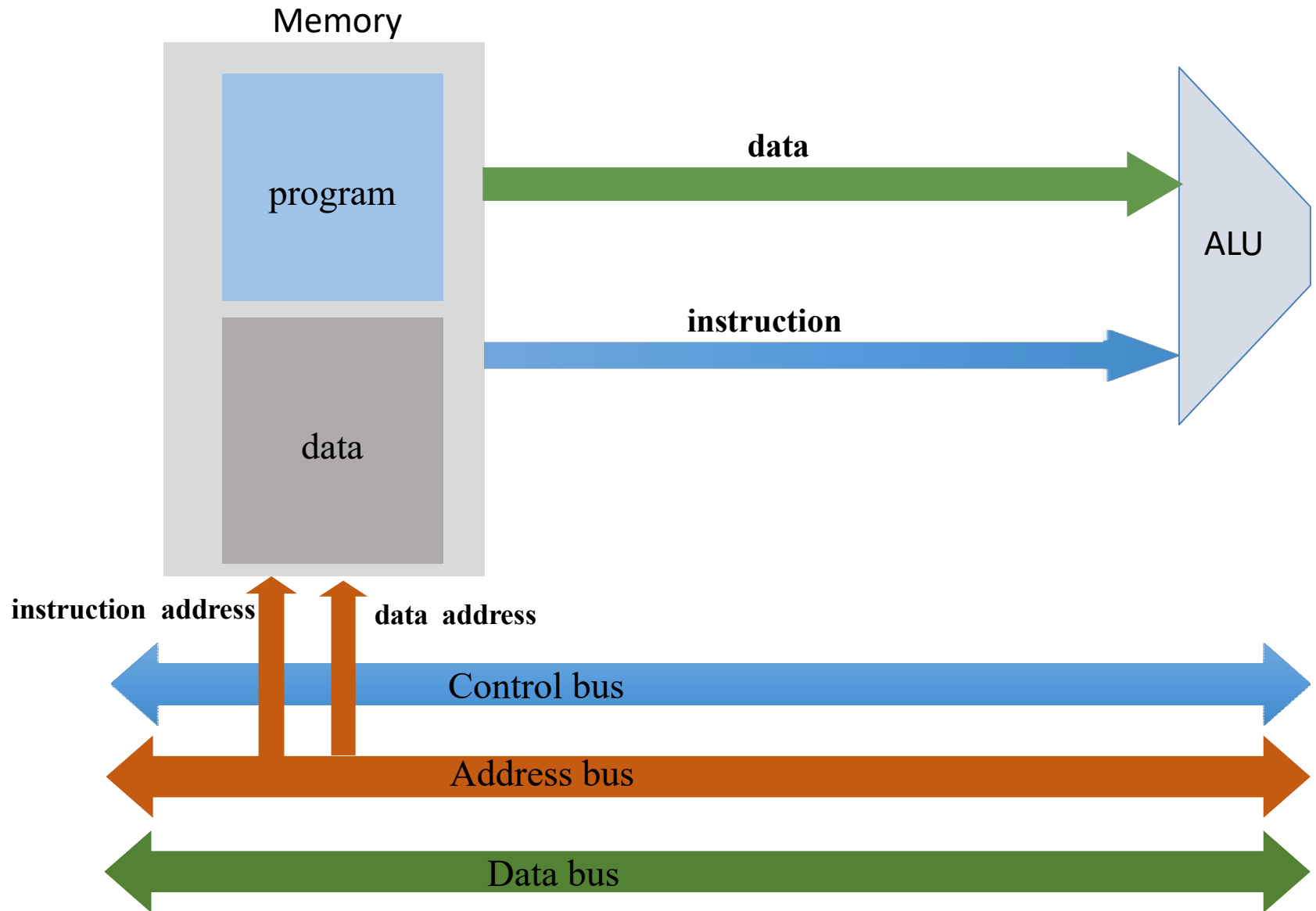



Fetch-Execute Clash

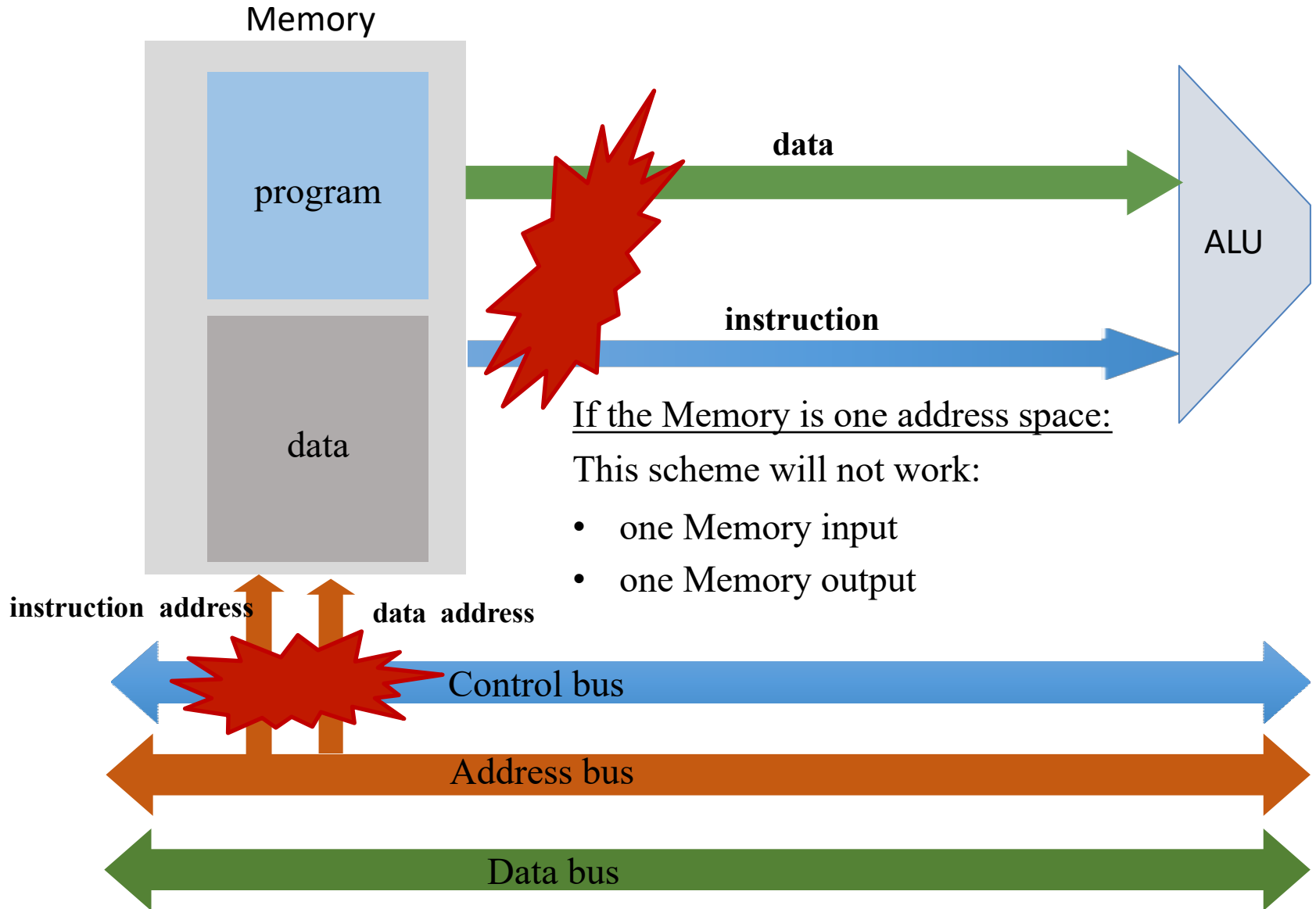


If the Memory is one address space:

This scheme will not work:

- one Memory input
- one Memory output




Fetch-Execute Clash (cont...)

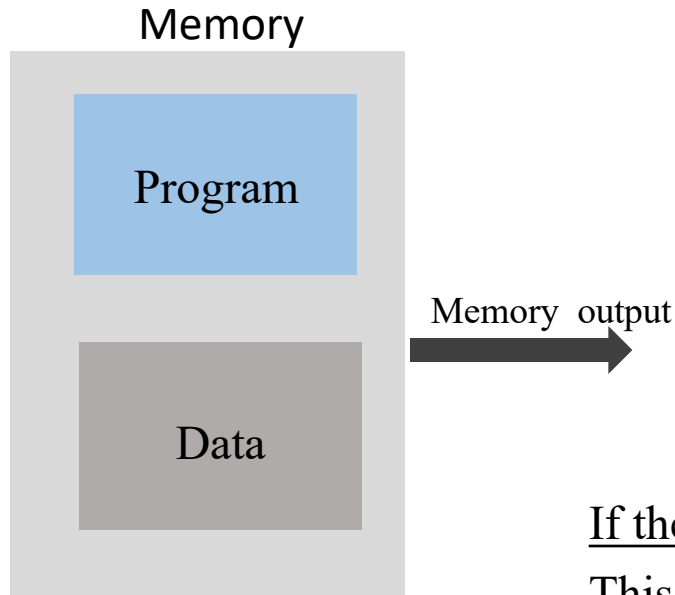

If the Memory is one address space:


This scheme will not work:

- one Memory input
- one Memory output

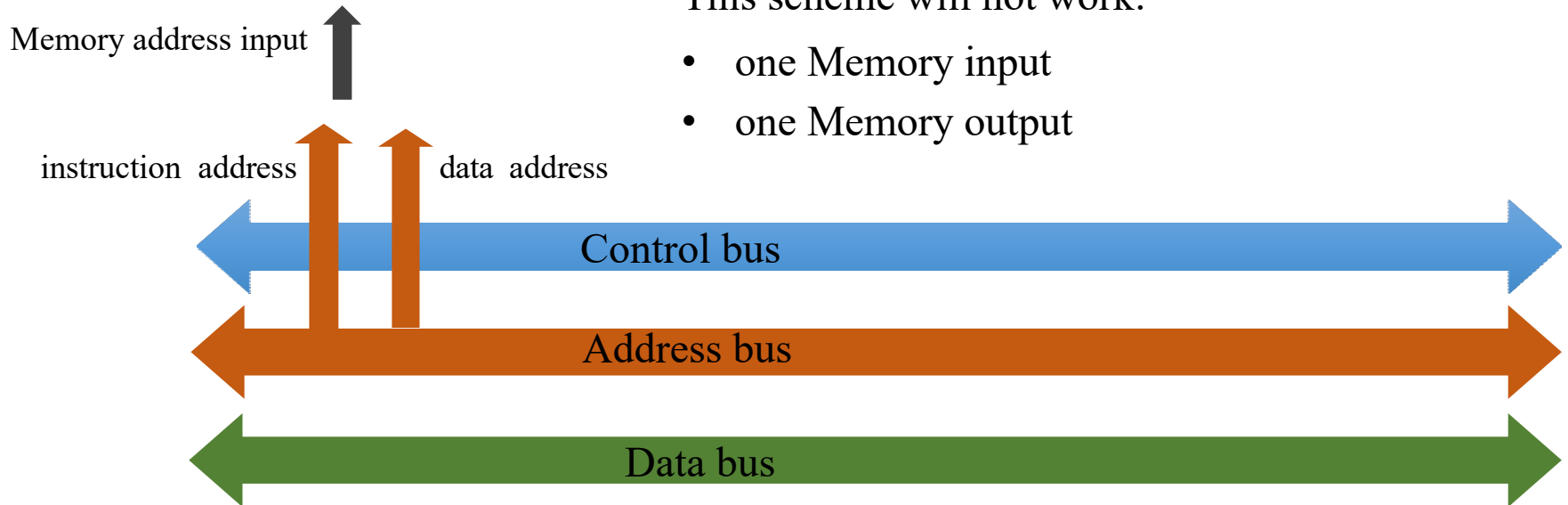




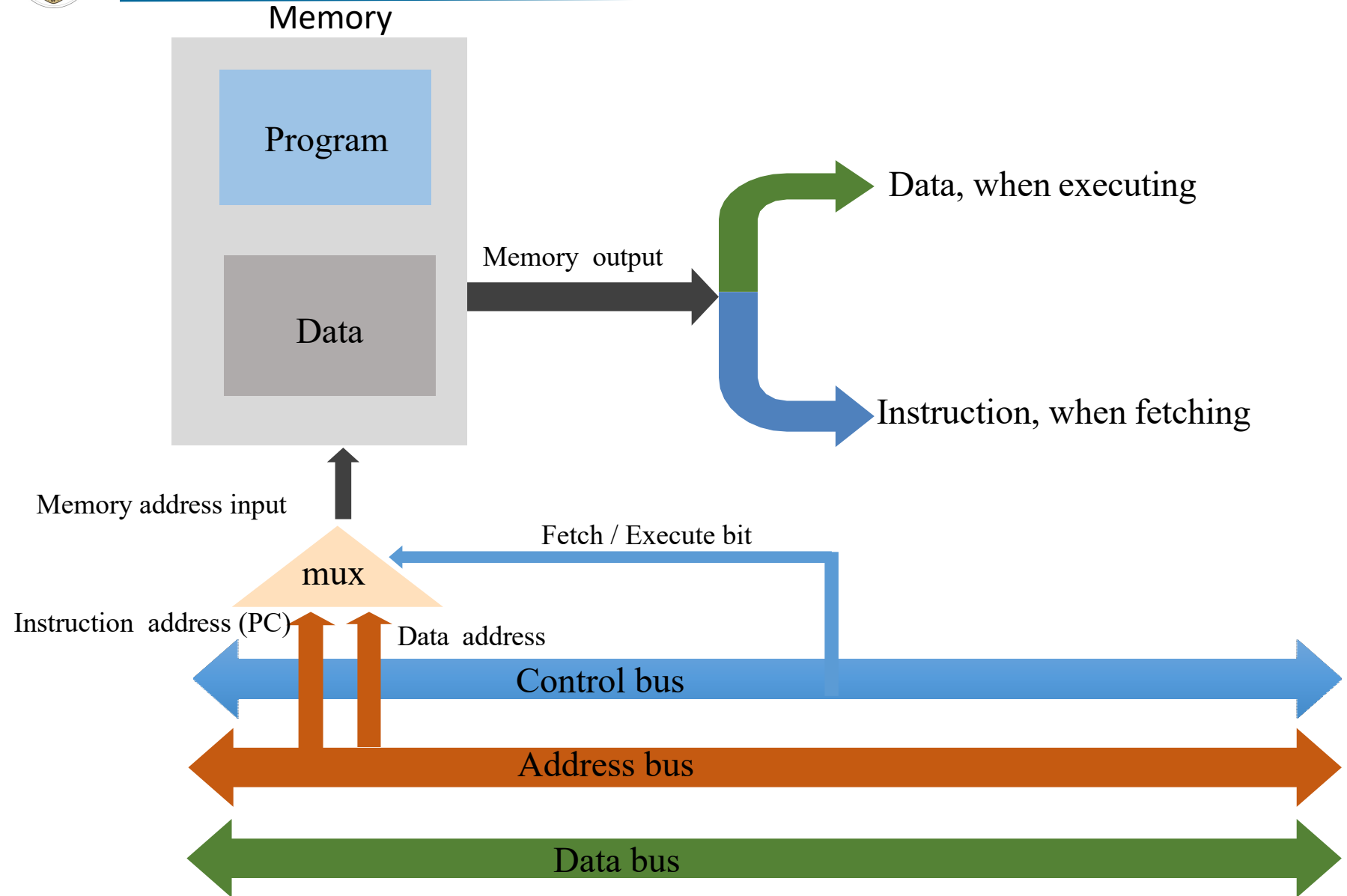Solution: multiplex, using an instruction register





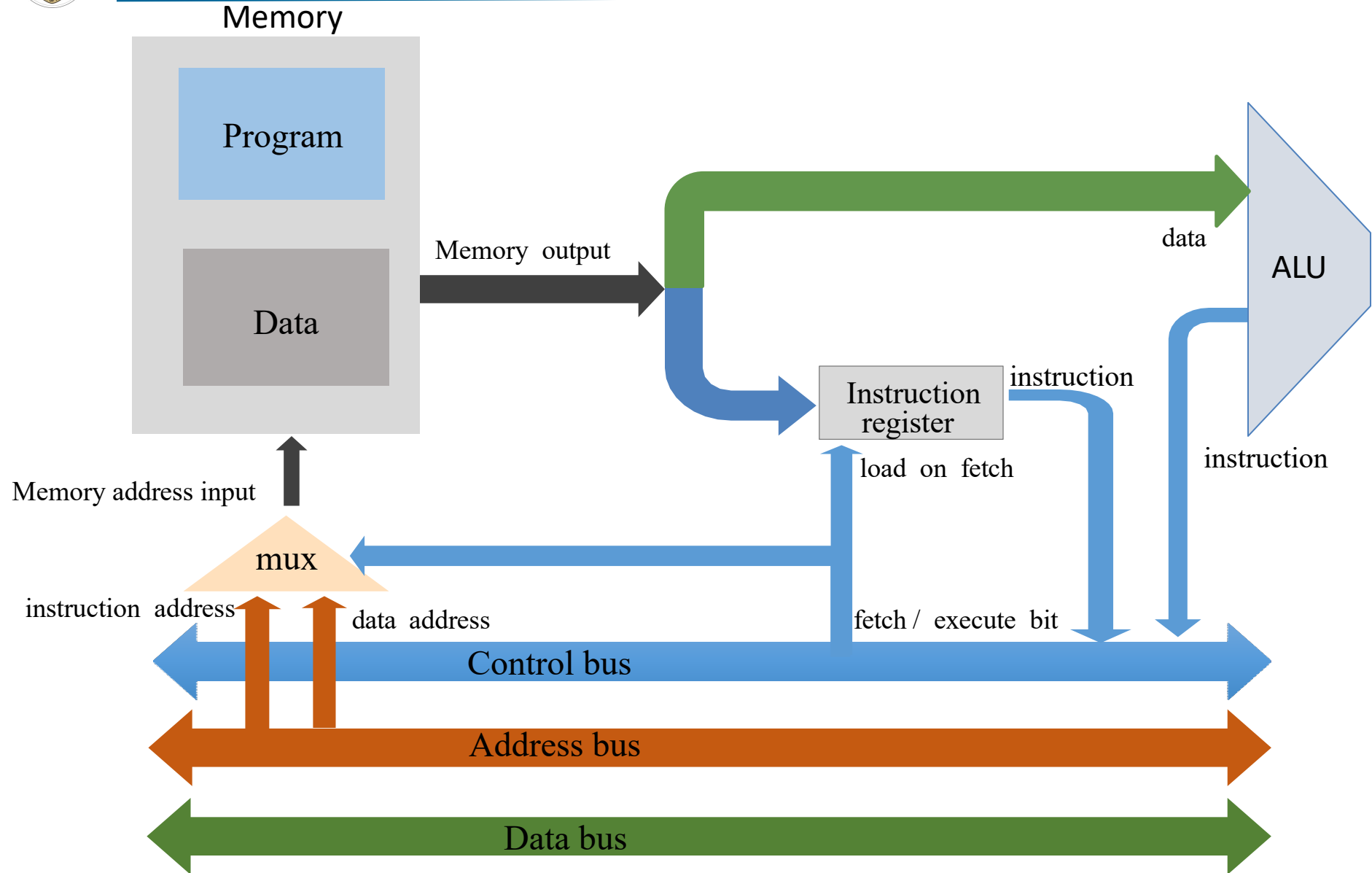Solution: multiplex, using an instruction register





Simpler Solution: Harvard Architecture

Variant of von Neumann Architecture (used by the Hack computer):

Two physically separate memory units:

- Instruction memory
 - Data memory
- } Each can be addressed and manipulated separately, and simultaneously

Advantage:

- Complication avoided

Disadvantage:


- Two memory chips instead of one
- The size of the two chips is fixed



Designing the Data Path of Hack CPU




Hack Computer Architecture

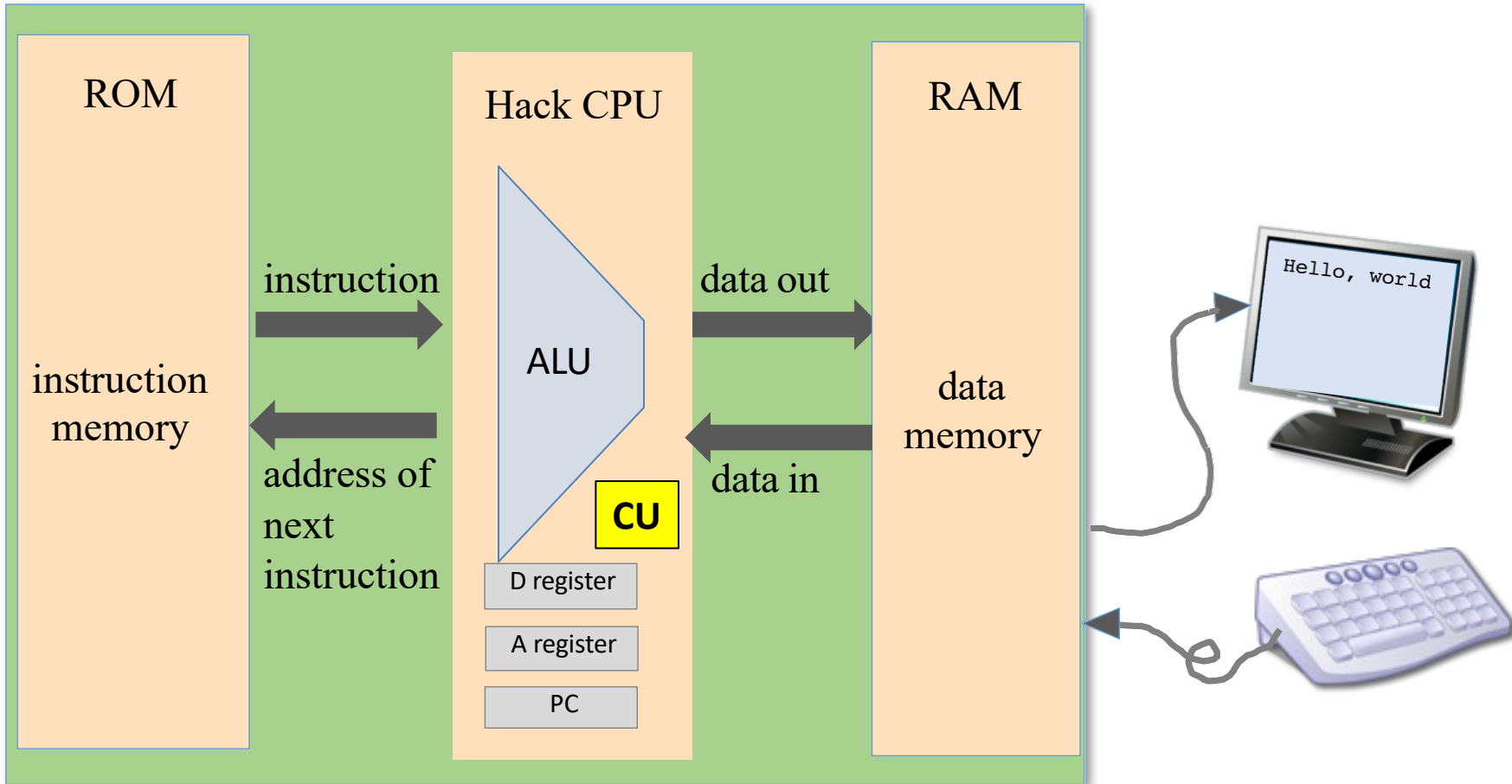




Hack CPU Interface

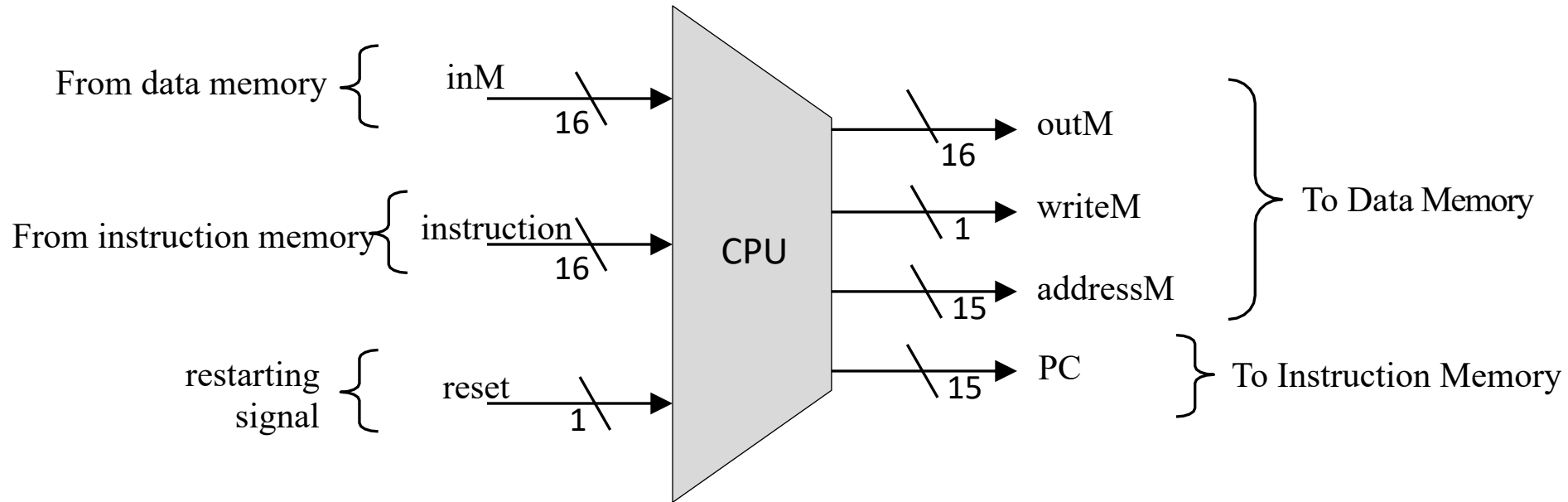


Inputs:

- Data Value
- Instruction
- Reset Bit

 




Hack CPU Interface

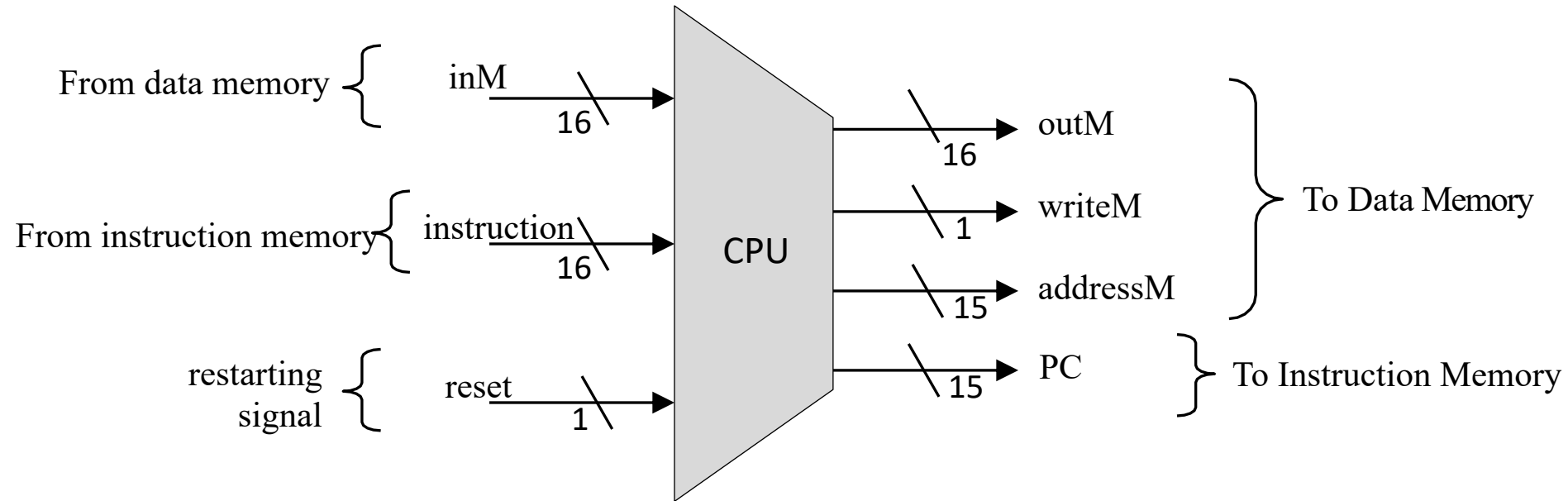

Outputs:

 
- Data Value
- Write to Memory? (yes/no)
- Memory Address
- Address of next instruction





Abstract View of Execution of A and C-Instruction

Hack Instructions:

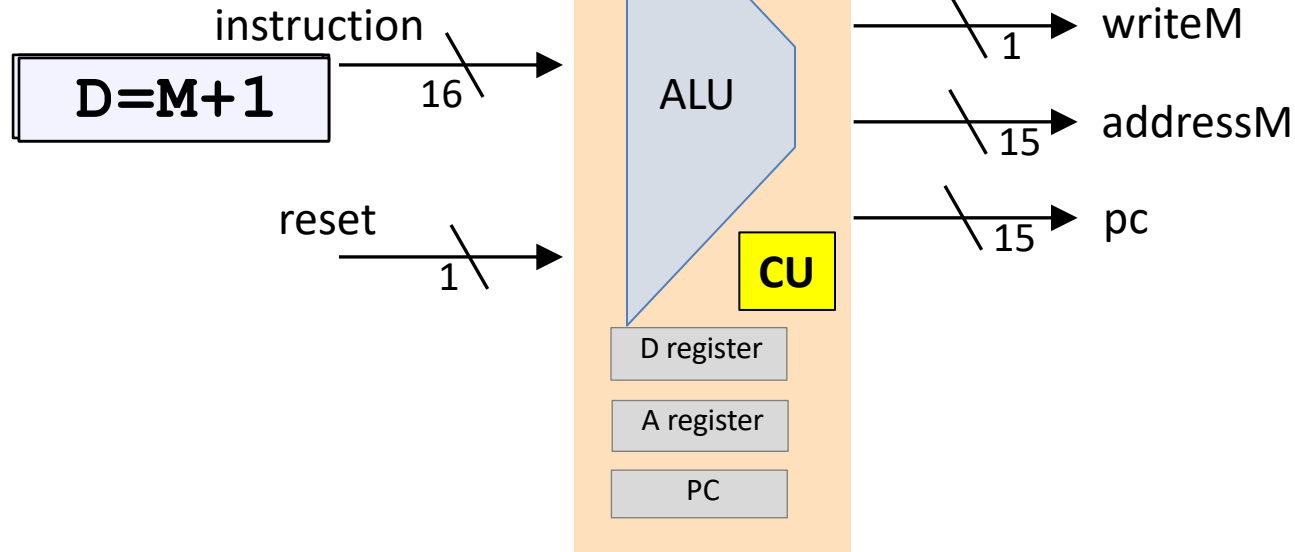



Abstract View of Address of next Instruction

Reset Bit and PC:

If (reset == 1)

The 15 bit output **pc** emits 0, causing the program to restart

If (reset==0)

The CPU logic uses the instruction's jump bits and the ALU's output to decide if there should be a jump. For example:


```
@ 54
D - 1 ; JEQ
```

If (D-1==0)

PC is set to the value of the A-register

else


PC++

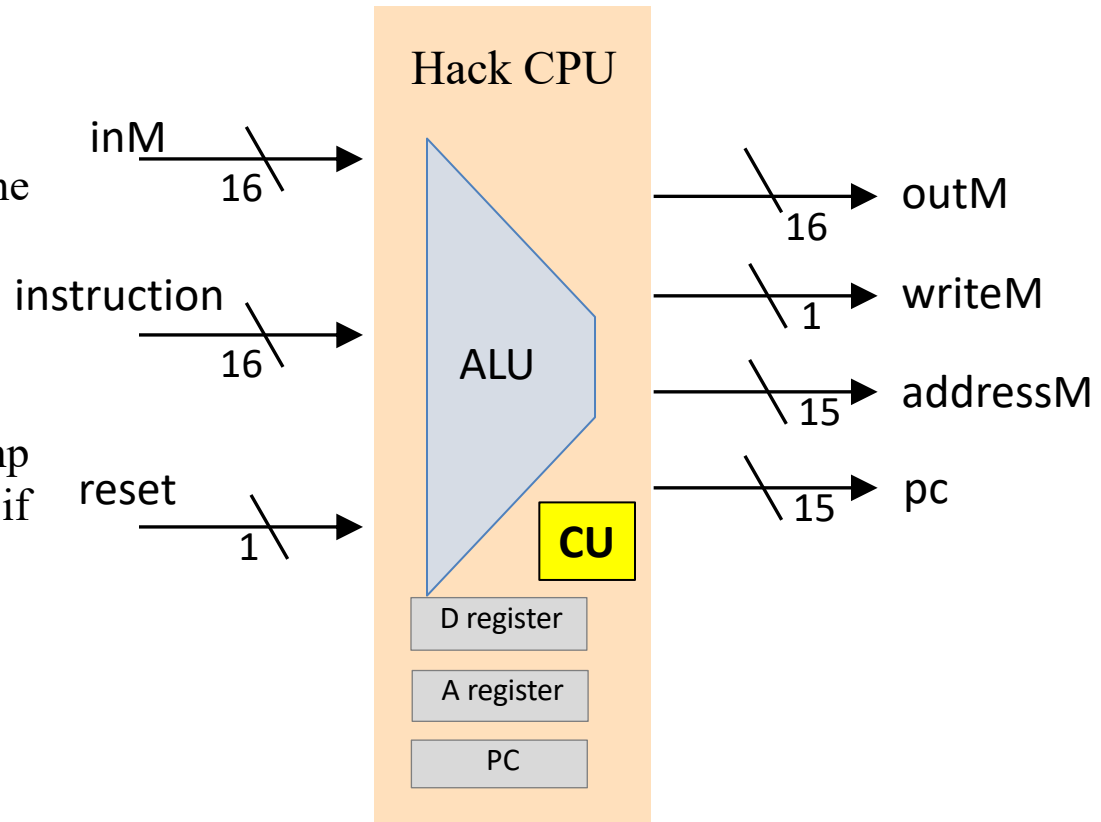

The updated PC value is emitted by 15 bit output named **PC**



Hack CPU Implementation

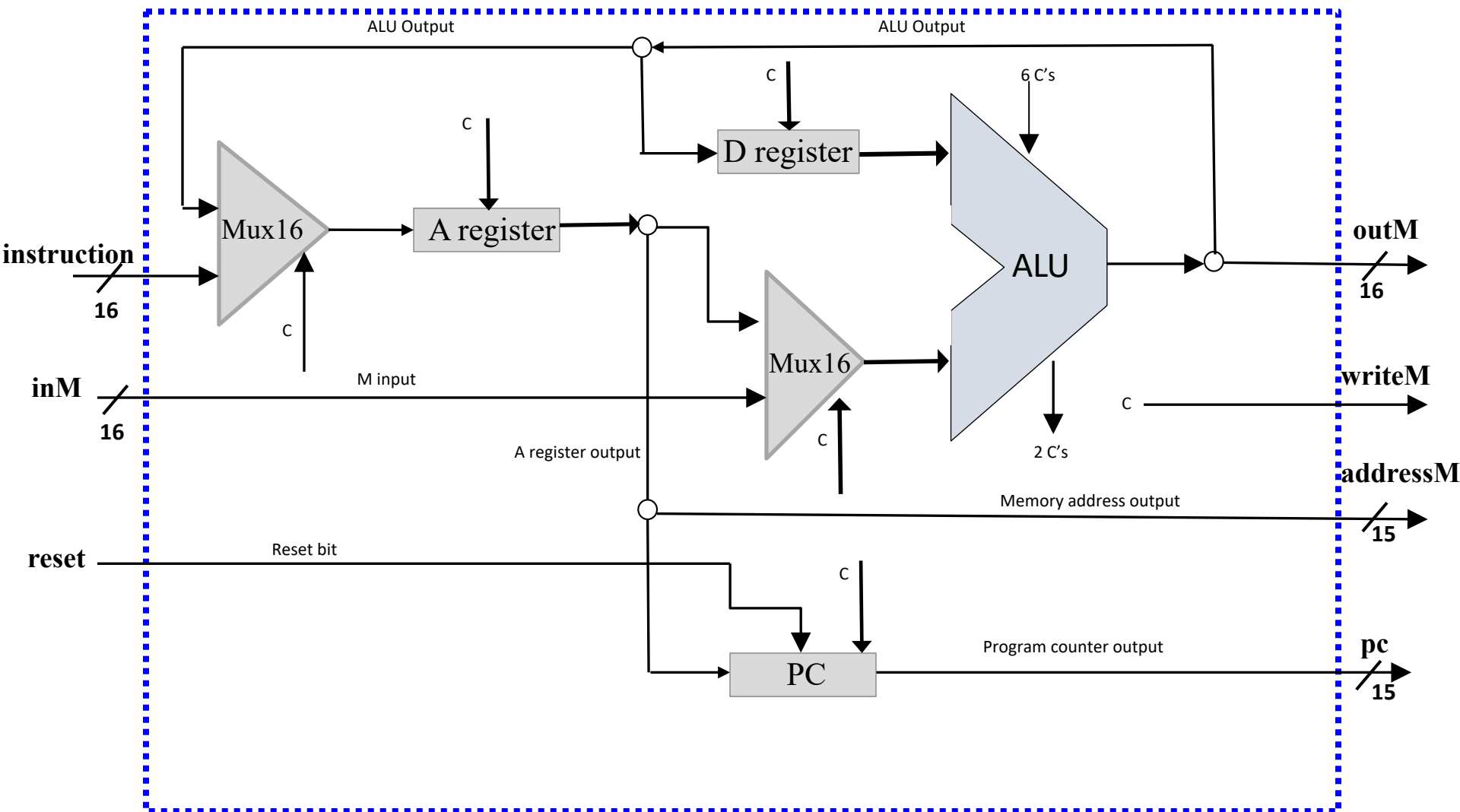


(each "C" symbol represents a control bit)



How A/C-Instructions Execute?




Instruction Handling

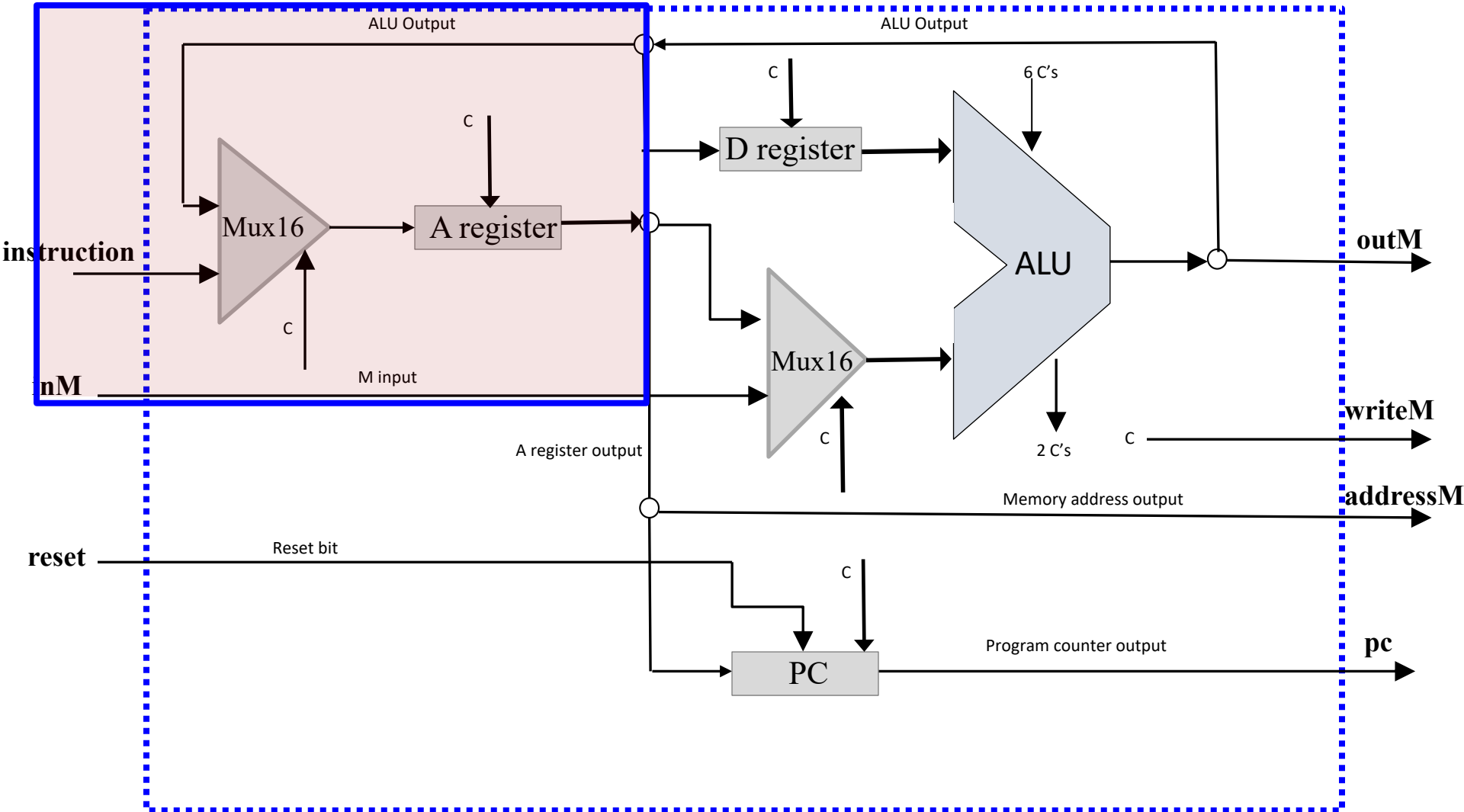



Handling A-Instruction

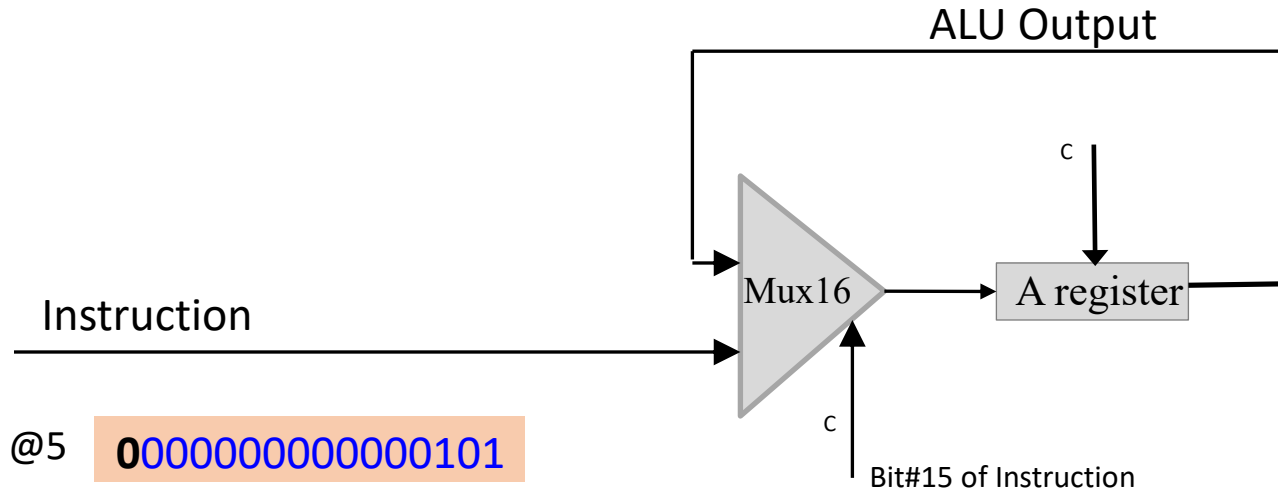

A-instruction

CPU handling of an A-instruction:


- Decodes the instruction into
 - op-code
 - 15-bit value
- Stores the 15 bit value in the A-register
- Outputs the value to ALU via Mux (not shown in this diagram)

Note:

- In case of A-instruction, the A-register get its input from the instruction part
- In case of C-instruction, the A-register get its input from the ALU output



Handling C-Instruction

 

D = D+1 ; JMP 1 11 0011111 010 111

C-instruction

CPU handling of C-instruction:

dest = comp ; jump


- Decodes the instruction bits into:
 - Op-code
 - ALU control bits (D+1)
 - Destination load bits (D-Register)
 - Jump bits (Un-conditional jump)
- Routes these bits to their chip-part destinations
- The chip-parts (most notably, the ALU) execute the instruction



Control Input of two Mux16 Chips




Select Input of First Mux16 Chip

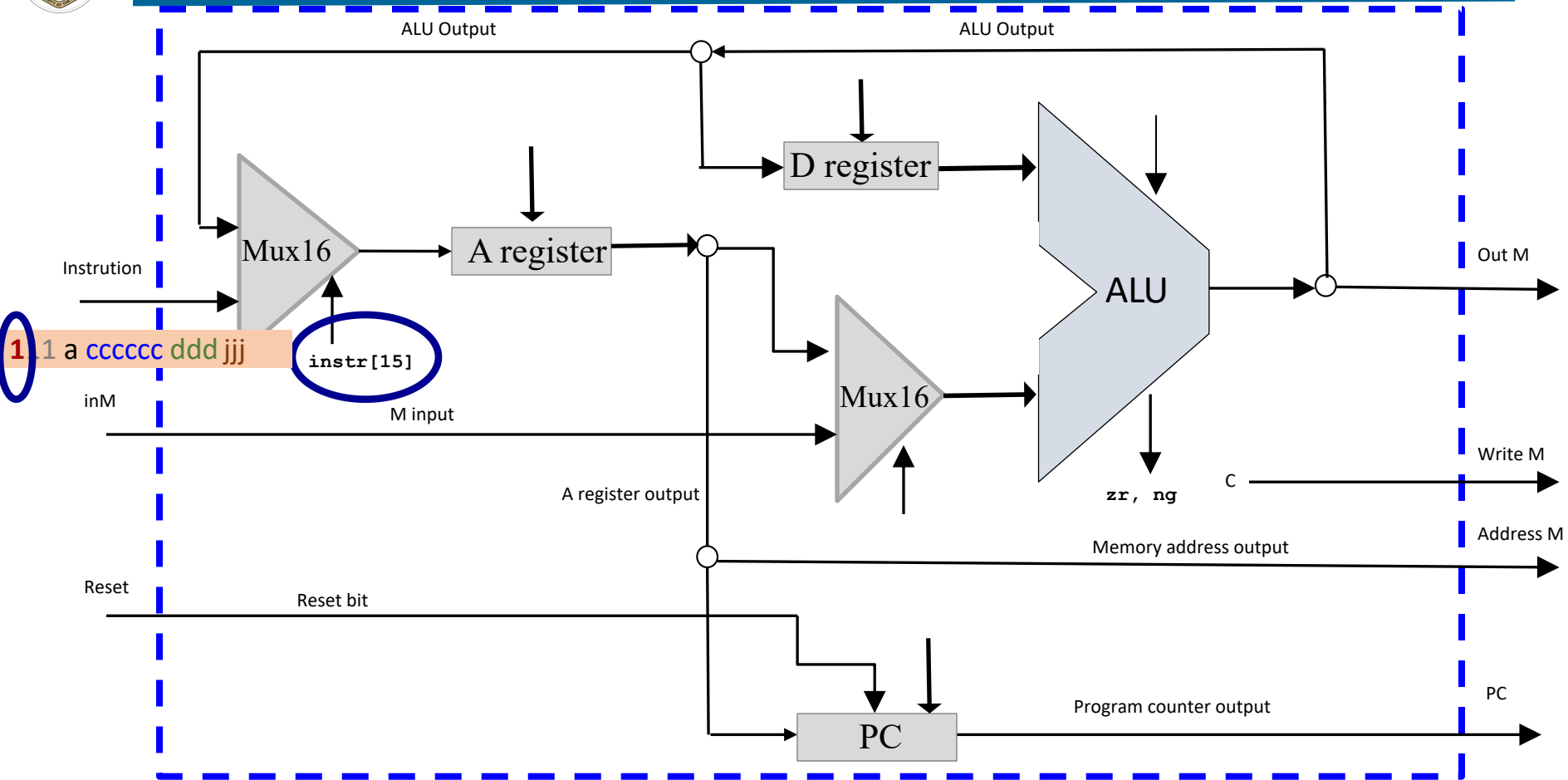



Select Input of Second Mux16 Chip

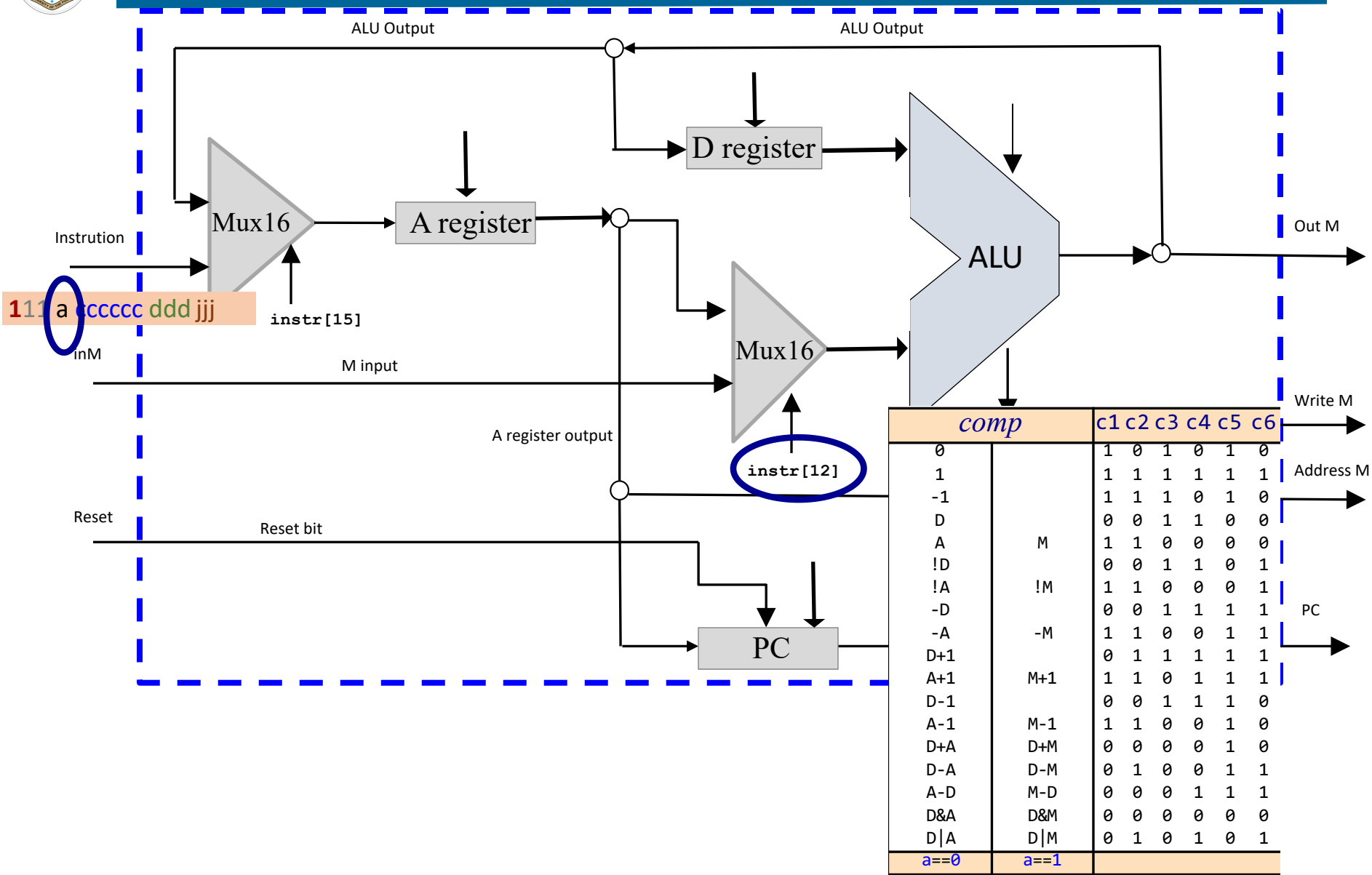




ALU Operations




ALU Operation

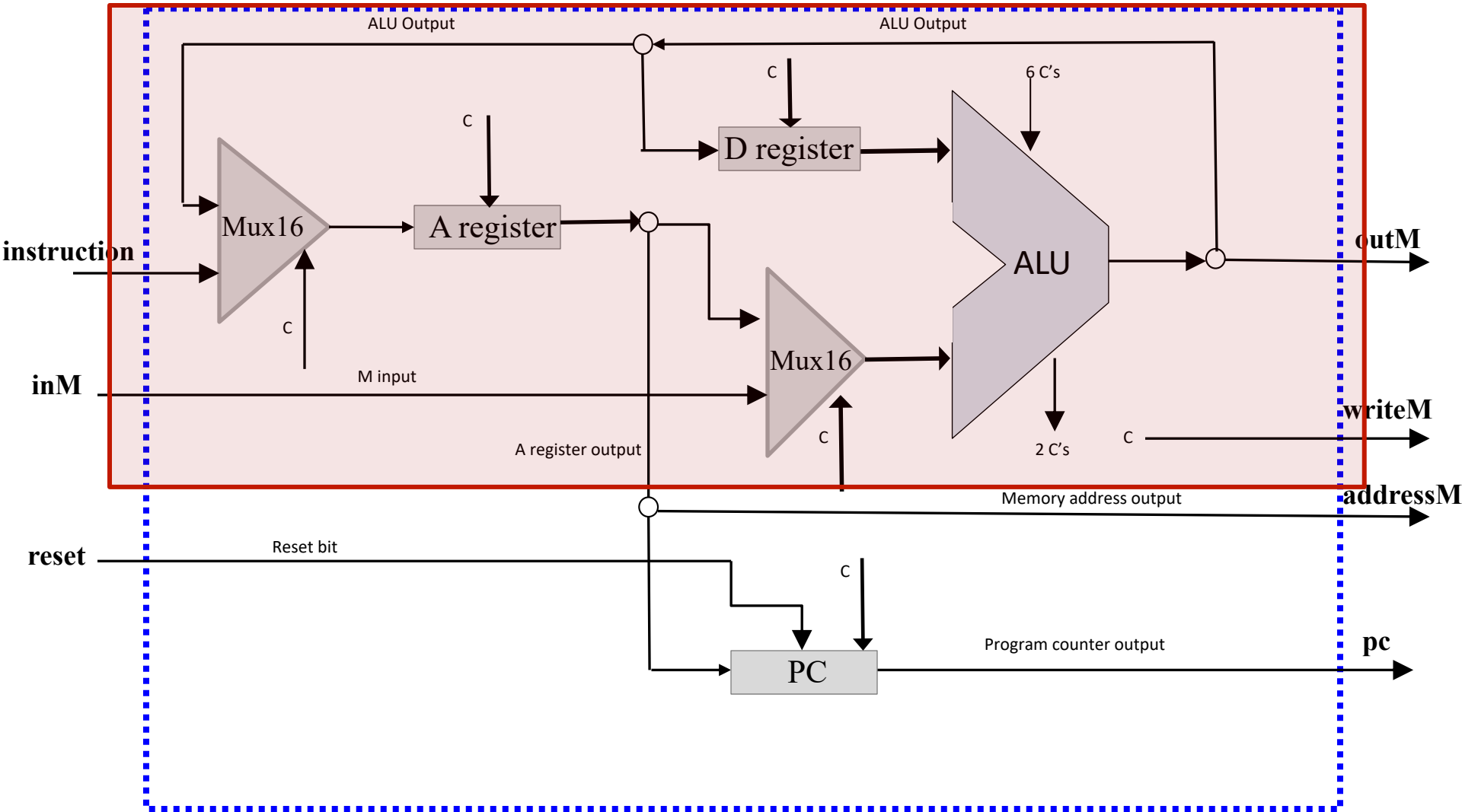



ALU Operation: Inputs

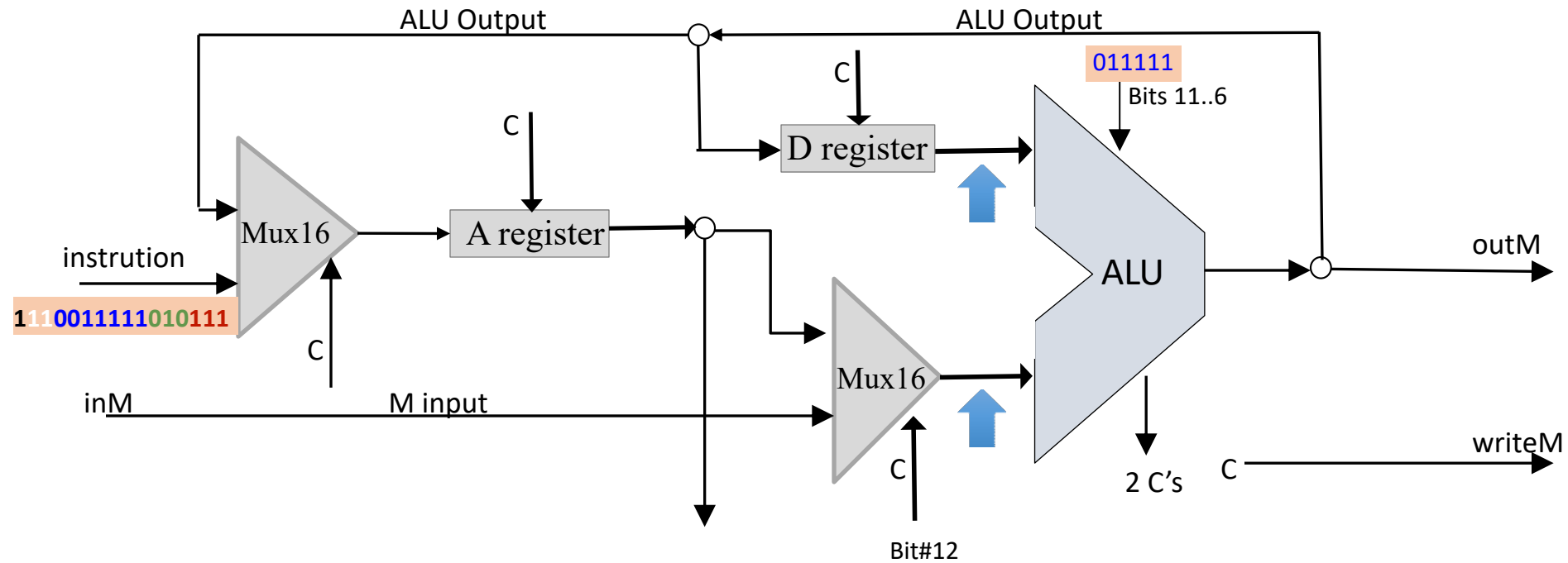

ALU data inputs:

- Input 1: From D-register
- Input 2: From A-register or M-register (decided by bit#12 of Instruction: **a**)


ALU control inputs:

- 6 x Control bits (from bits 6-11 of the instruction: **cccccc**)

`1 11 a cccccc ddd jjj`



ALU Operation: Control Outputs

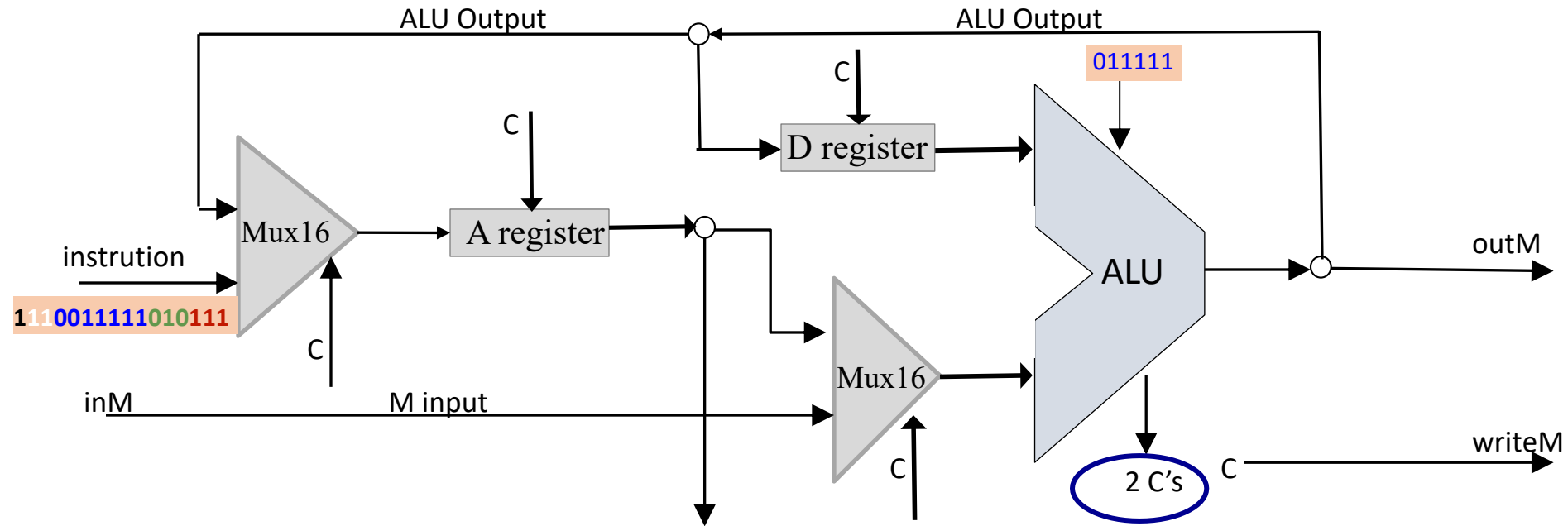

ALU control outputs:


- is the output negative? (ng)
- is the output zero? (zr)



Control Inputs of A-Register and D-Register Chips




Load Input of A-Register Chip

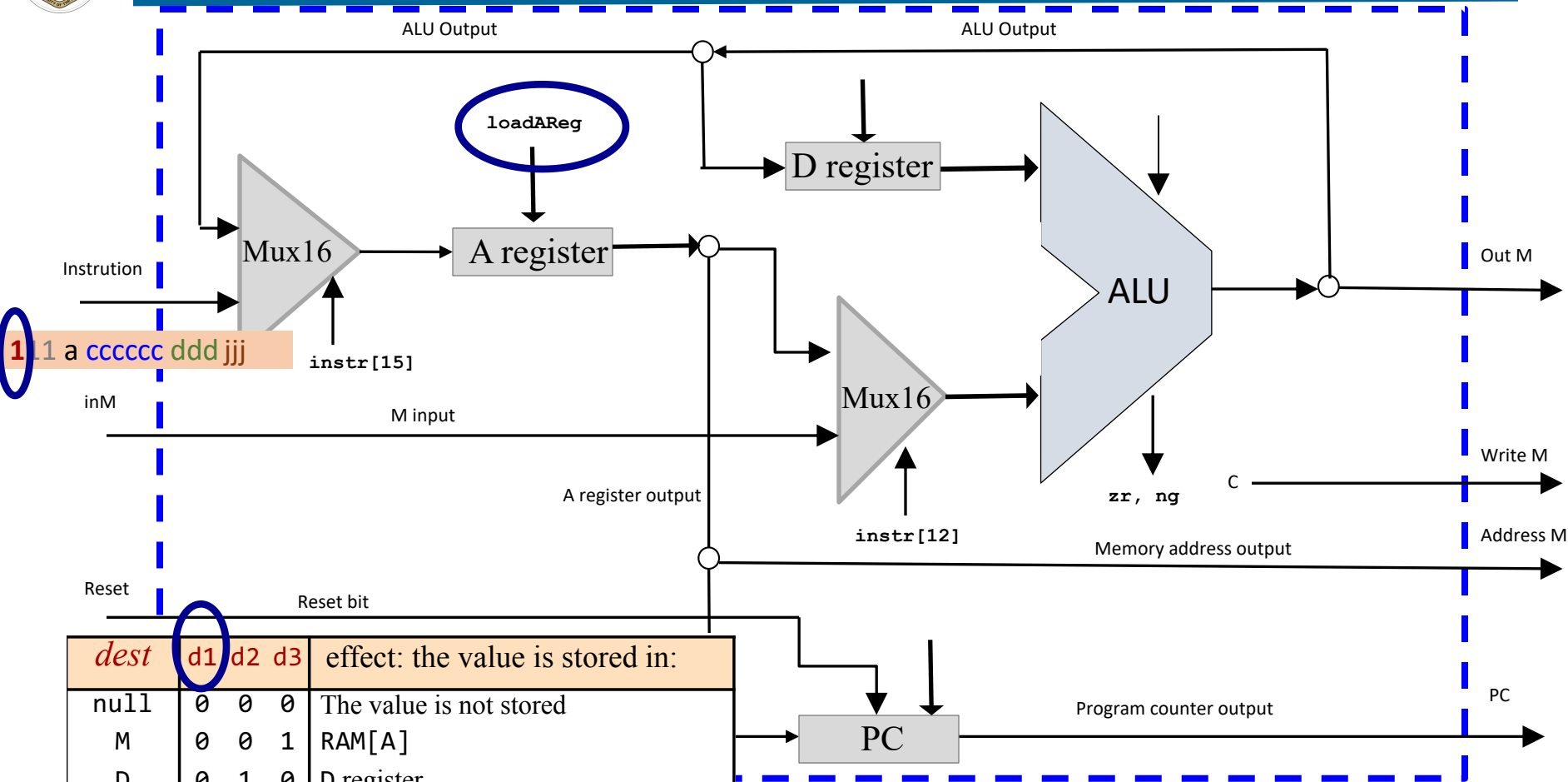

<i>dest</i>	d1	d2	d3	effect: the value is stored in:
null	0	0	0	The value is not stored
M	0	0	1	RAM[A]
D	0	1	0	D register
MD	0	1	1	RAM[A] and D register
A	1	0	0	A register
AM	1	0	1	A register and RAM[A]
AD	1	1	0	A register and D register
AMD	1	1	1	A register, RAM[A], and D register



Load Input of D-Register Chip

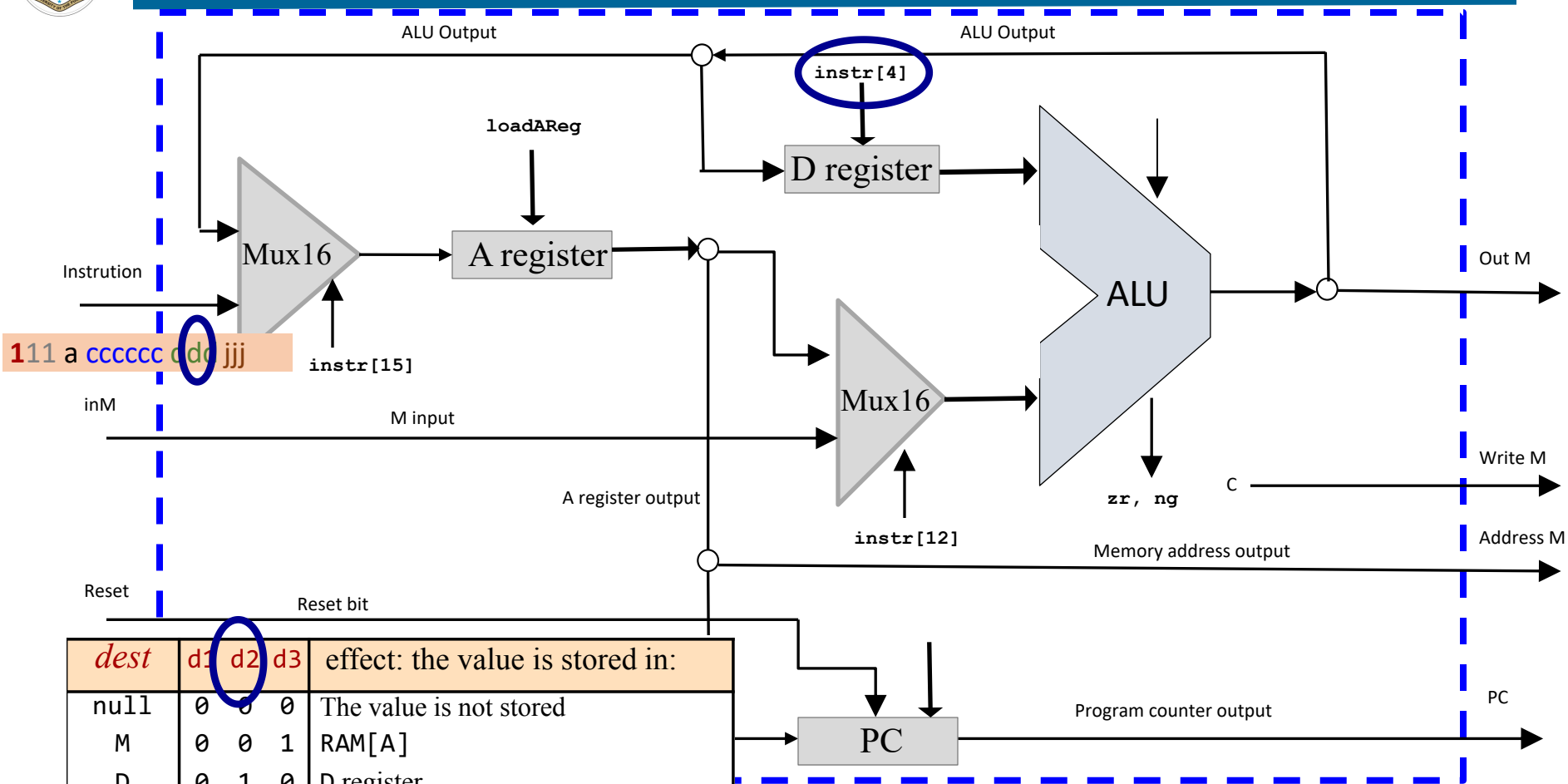


<i>dest</i>	<i>d1</i>	<i>d2</i>	<i>d3</i>	effect: the value is stored in:
null	0	0	0	The value is not stored
M	0	0	1	RAM[A]
D	0	1	0	D register
MD	0	1	1	RAM[A] and D register
A	1	0	0	A register
AM	1	0	1	A register and RAM[A]
AD	1	1	0	A register and D register
AMD	1	1	1	A register, RAM[A], and D register



Control Logic of PC Register




Control Logic of CPU

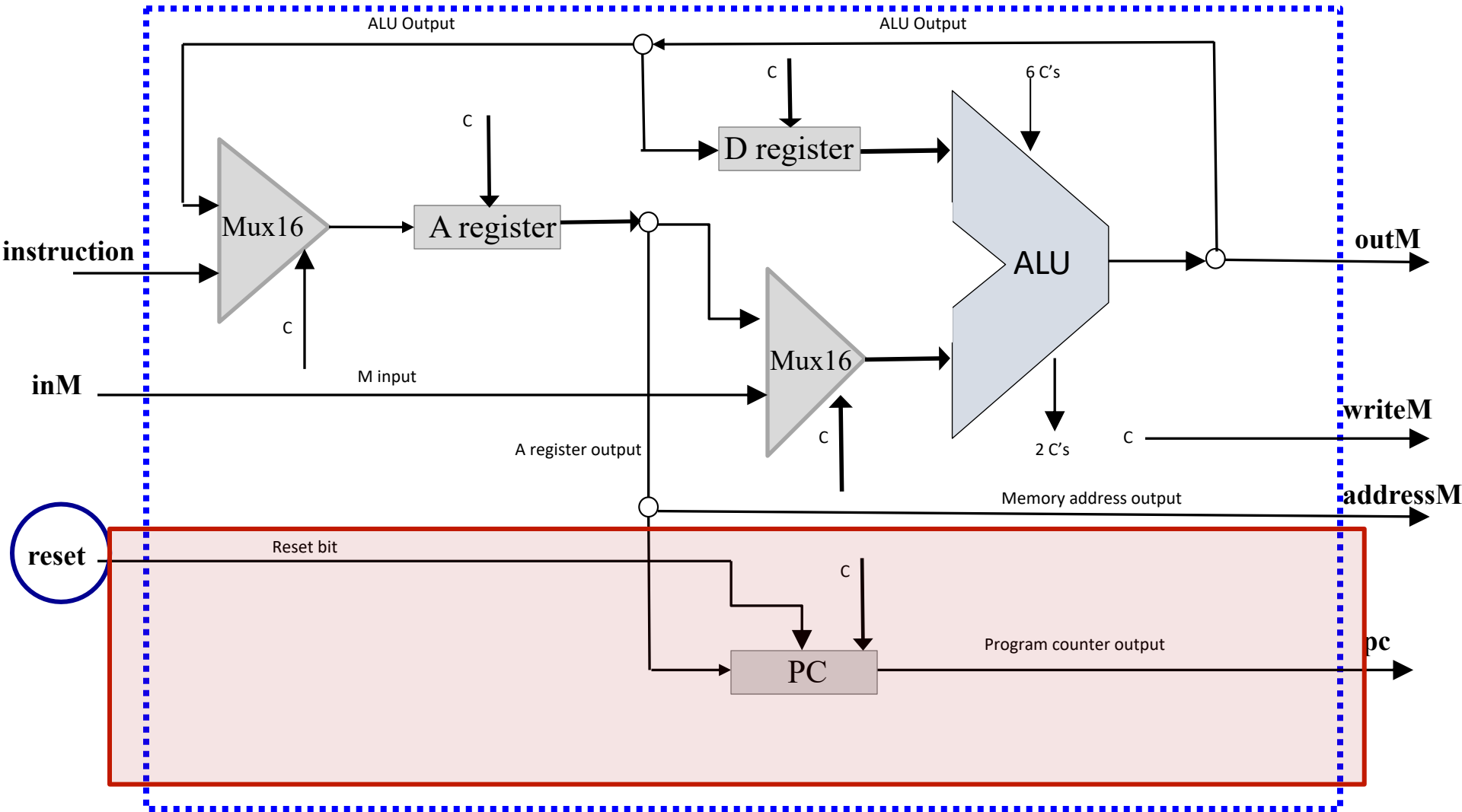

(each "C" symbol represents a control bit)




Possible Outside View of Hack Computer

 

- The computer is loaded with some program
- Pushing reset button causes the program to start running from beginning



Control Abstraction

 


PC operation (abstraction)

- Emits the address of the next instruction
- reset: PC=0
- no jump: **000** PC++
- goto: **111** PC=A
- conditional goto: if (condition) PC= A else PC++



Control Implementation

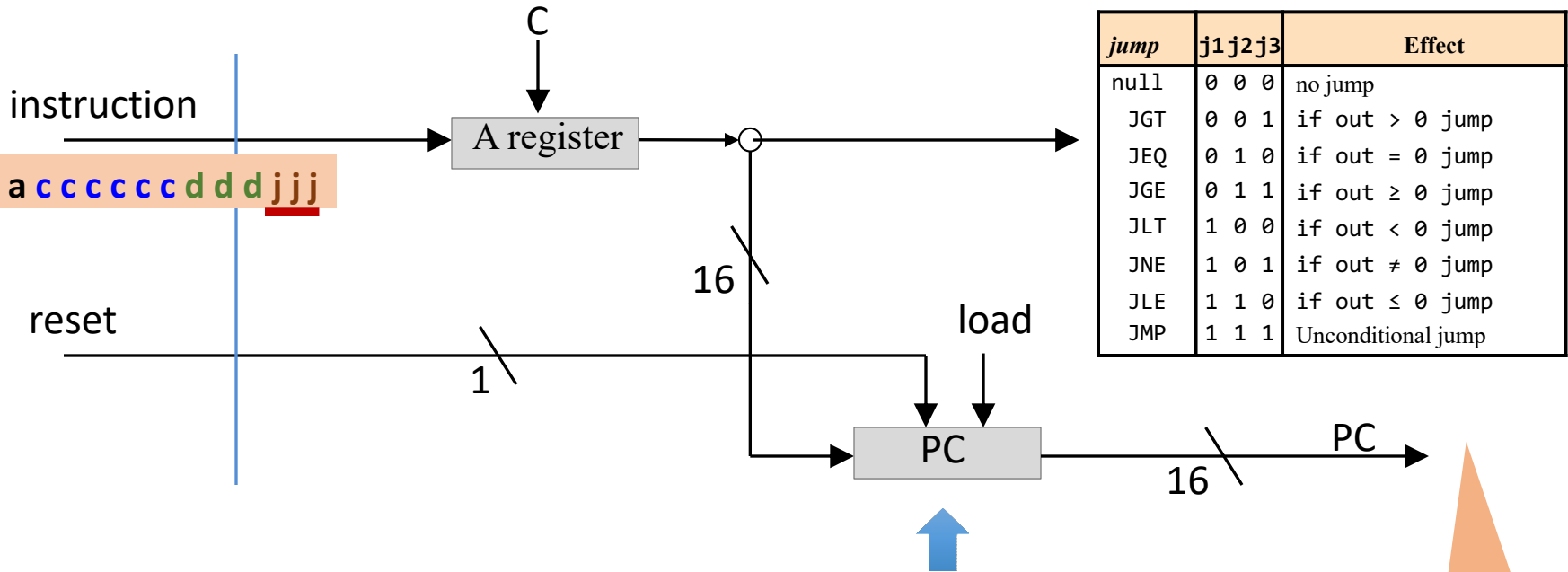

PC operation (implementation)

```
if (reset == 1)
```

```
    PC = 0
```

```
else
```

```
    load = f(jump bits, ALU control outputs (zr,ng))
```


```
    if (load == 1)    PC = A    // jump
```

```
    else            PC++      // next instruction
```

address of next instruction



Hack CPU Implementation

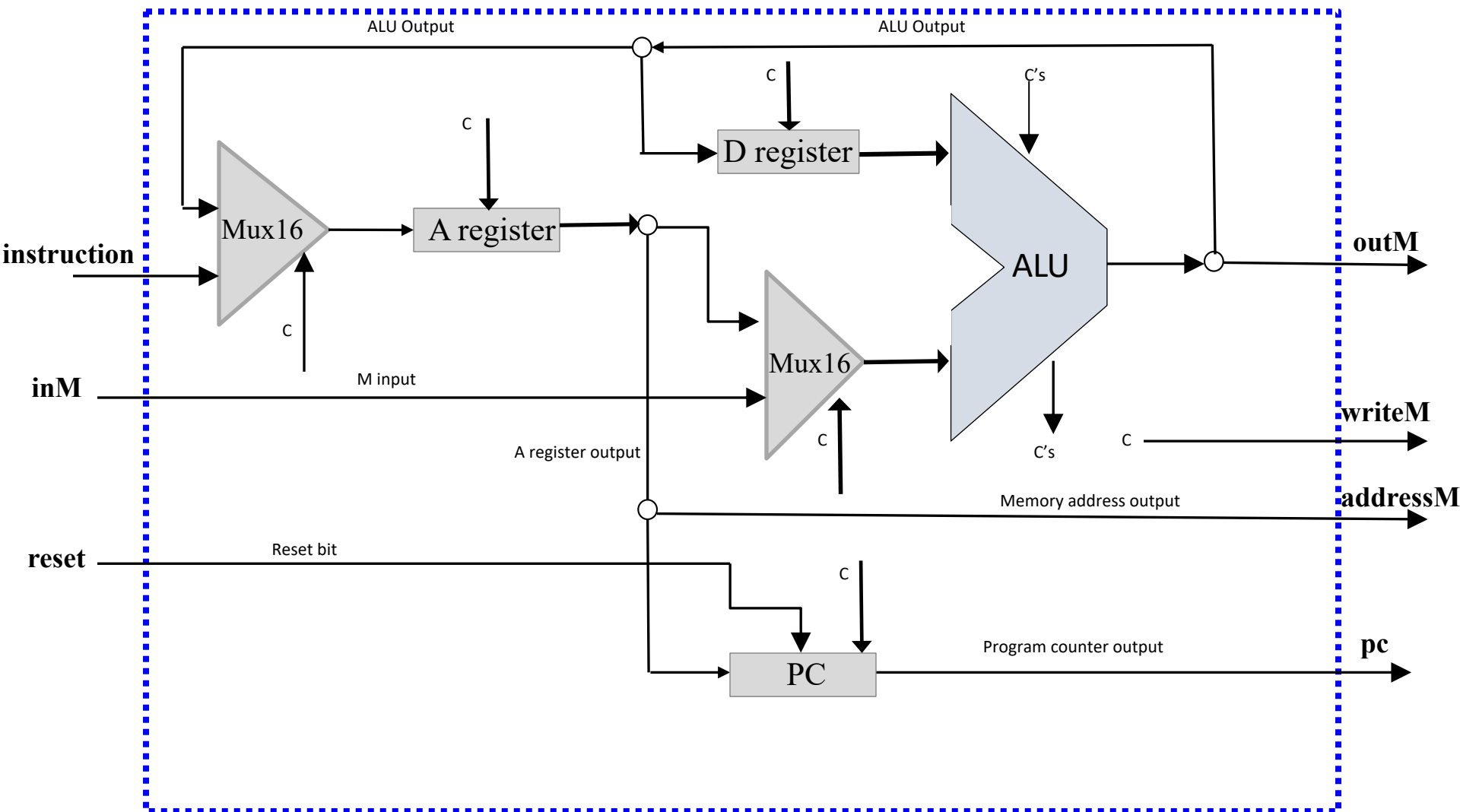

That's It! All that remains is to actually build it 😊



Things To Do

